

A. Conventional number system.

Carry-propagate adders (CPA)

- Switched carry-ripple adder
- Carry-skip adder
- Carry-lookahead adder
- Prefix adder
- Carry-select adder and conditional-sum adder
- Variable-time adder

B. Redundant number system.

Totally-parallel adders (TPA); adders with limited carry propagation

- Carry-save adder
- Signed-digit adder

n-BIT ADDITION

$$x + y + c_{in} = 2^n c_{out} + s$$

The solution:

$$s = (x + y + c_{in}) \bmod 2^n$$

$$c_{out} = \begin{cases} 1 & \text{if } (x + y + c_{in}) \geq 2^n \\ 0 & \text{otherwise} \end{cases}$$

$$= \lfloor (x + y + c_{in}) / 2^n \rfloor$$

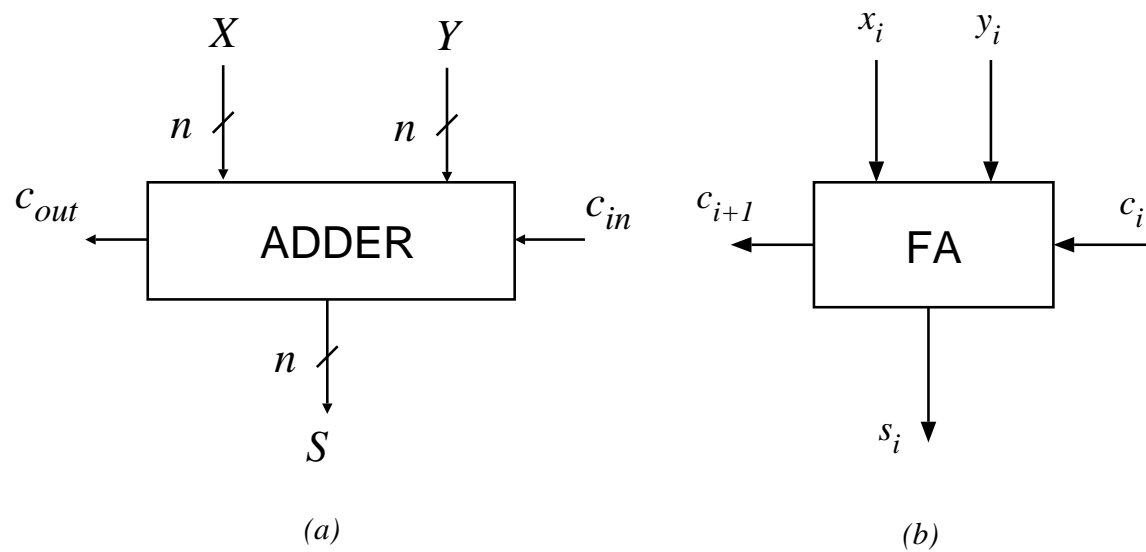


Figure 2.1: (a) An n -bit adder. (b) 1-bit adder (full adder module).

- Primitive module *full adder* (FA)

$$x_i + y_i + c_i = 2c_{i+1} + s_i$$

with solution

$$s_i = (x_i + y_i + c_i) \bmod 2$$

$$c_{i+1} = \lfloor (x_i + y_i + c_i) / 2 \rfloor$$

ADDITION: TWO-STEP PROCESS

1. Obtain carries (carry at i depends on $j \leq i$)
 - non-trivial to do fast
2. Compute sum bits (local function)

 


Figure 2.2: Steps in addition.

CARRY-OUT CASES

Case	x_i	y_i	$x_i + y_i$	c_{i+1}	Comment
1	0	0	0	0	kill (stop) carry-in
2	0	1	1	c_i	propagate carry-in
	1	0	1	c_i	propagate carry-in
3	1	1	2	1	generate carry-out

Case 1 (Kill): $k_i = x_i' y_i' = (x_i + y_i)'$

Case 2 (Propagate): $p_i = x_i \oplus y_i$

Case 3 (Generate): $g_i = x_i y_i$

Then

$$c_{i+1} = g_i + p_i c_i = x_i y_i + (x_i \oplus y_i) c_i$$

Alternative (simpler) expression:

$$c_{i+1} = g_i + a_i c_i$$

Since $a_i = k_i'$ we call it "alive"

CARRY CHAINS

Two types:

1-carry chain consisting of carry=1

0-carry chain consisting of carry=0

i	9	8	7	6	5	4	3	2	1	0	
x_i	1	0	1	0	1	1	1	1	0	0	
y_i	0	0	0	1	0	1	0	0	1	0	
	p	k	p	p	p	g	p	p	p	k	
	a		a	a	a	a	a	a	a		
c_{i+1}	0	← 0	1	← 1	← 1	← 1	← 1	0	← 0	← 0	← 0

Generalization to group of bits

$$c_{j+1} = g_{(j,i)} + p_{(j,i)}c_i = g_{(j,i)} + a_{(j,i)}c_i$$

or, for $i = 0$

$$c_{j+1} = g_{(j,0)} + p_{(j,0)}c_0 = g_{(j,0)} + a_{(j,0)}c_0$$

Recursive combining of subranges of variables:

$$g_{(f,d)} = g_{(f,e)} + p_{(f,e)}g_{(e-1,d)} = g_{(f,e)} + a_{(f,e)}g_{(e-1,d)}$$

$$a_{(f,d)} = a_{(f,e)}a_{(e-1,d)}$$

$$p_{(f,d)} = p_{(f,e)}p_{(e-1,d)}$$

Generalization (cont.)

 


Figure 2.3: Computing $(g_{(f,d)}, a_{(f,d)})$.

BASIC CARRY-RIPPLE ADDER (CRA)

 


Figure 2.4: Carry-ripple adder.

$$T_{CRA} = (n - 1)t_c + \max(t_c, t_s)$$

Implementations of full-adder

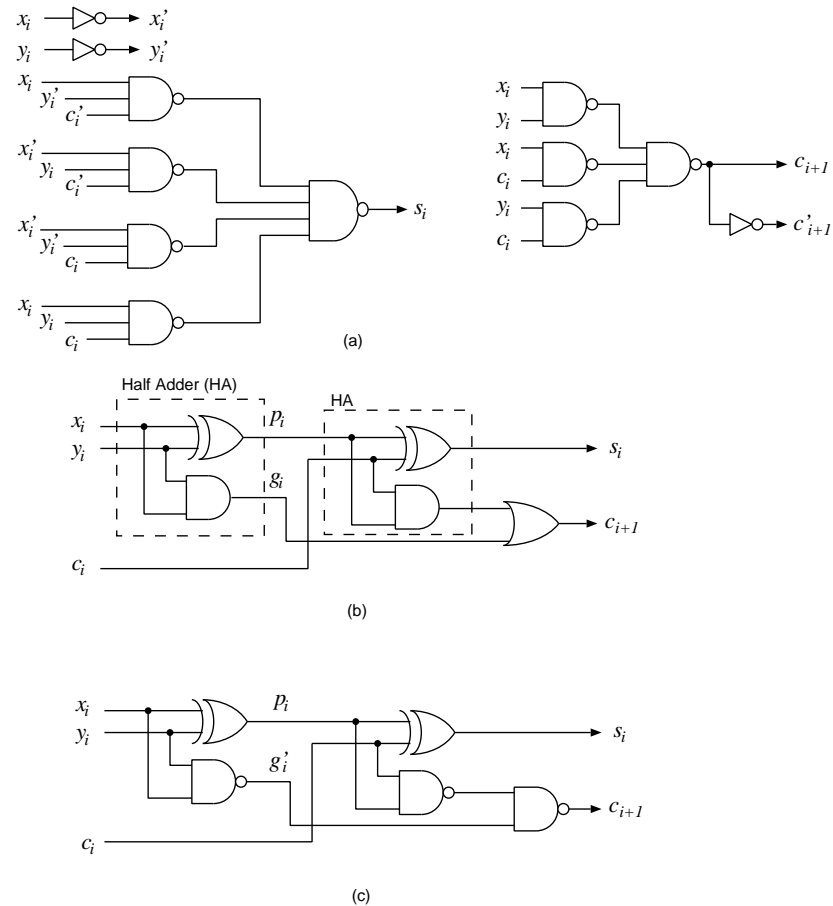


Figure 2.5: Implementation of full-adder. (a) Two-level network. (b) Multilevel network with XOR, AND and OR gates; (c) Multilevel implementation with XOR and NAND gates.

SWITCHED CARRY-RIPPLE (Manchester) ADDER

 


Figure 2.6: Switch carry-ripple network (Manchester circuit)

CARRY-SKIP ADDER

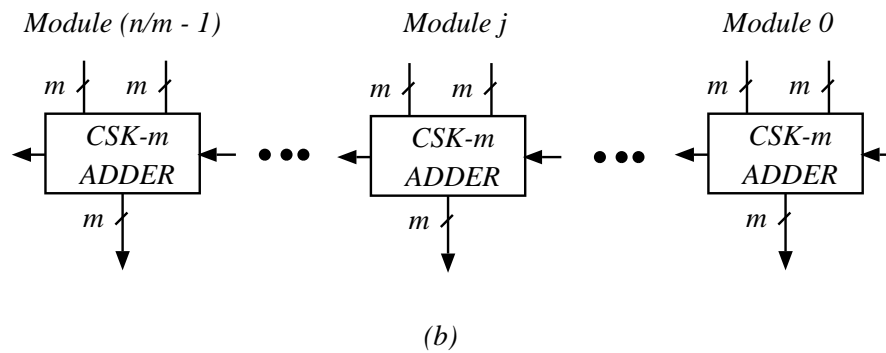
 


Figure 2.7: Carry-skip adder: (a) A group with carry bypass. (b) n-bit CSK adder.

CARRY CHAINS IN CARRY-SKIP ADDER

 


Figure 2.8: Carry chains in carry-skip adder: A case with several carry chains.

 
 


Figure 2.9: (a) Critical path in carry-skip adder. (b) The worst-case situation for $n = 16$.

$$\begin{aligned}
 T_{CSK} &= mt_c + t_{mux} + \left(\frac{n}{m} - 2\right)t_{mux} + (m - 1)t_c + t_s \\
 &= (2m - 1)t_c + \left(\frac{n}{m} - 1\right)t_{mux} + t_s
 \end{aligned}$$

PROBLEM WITH CLEARING OF CARRIES

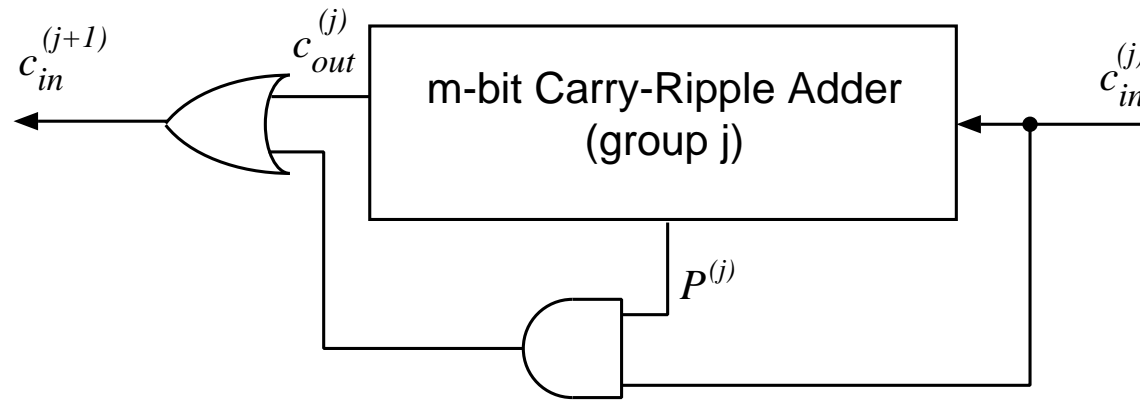


Figure 2.10: Carry-skip adder using AND-OR for bypass

Fixed-size:

$$m_{opt} = \left(\frac{t_{mux}n}{2t_c}\right)^{1/2} \text{ (minimum delay)}$$

$$T_{opt} \approx (8t_{mux}t_cn)^{1/2}$$

Variable-size:

 


Figure 2.11: Optimal distribution of group sizes in carry-skip adder.

CARRY-LOOKAHEAD ADDER(CLA)

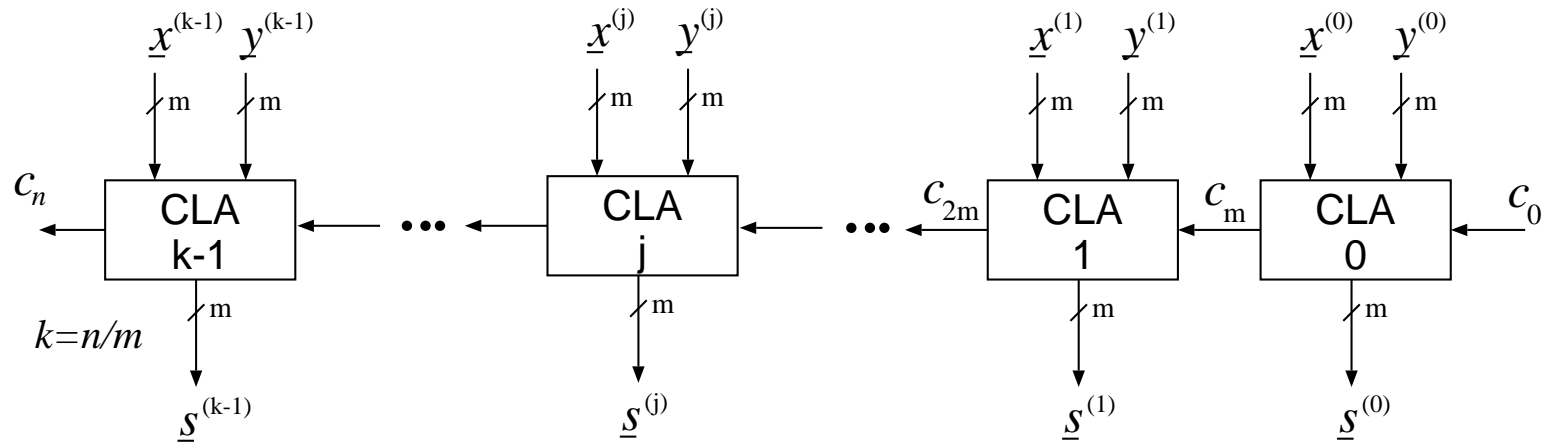


Figure 2.12: One-level carry-lookahead adder

CARRY-LOOKAHEAD MODULE

 


Figure 2.13: Carry-lookahead adder module ($m = 4$).

CARRY-LOOKAHEAD GENERATOR

 


Figure 2.14: 4-bit carry-lookahead generator CLG-4.

TWO-LEVEL CARRY-LOOKAHEAD ADDER

 
 


Figure 2.15: Two-level carry-lookahead adder ($n = 32$)

Figure 2.16: Three-level carry-lookahead adder ($n = 8$, $m = 2$).

Prefix adders

 


Figure 2.17: Composition of spans in computing (g, a) signals.

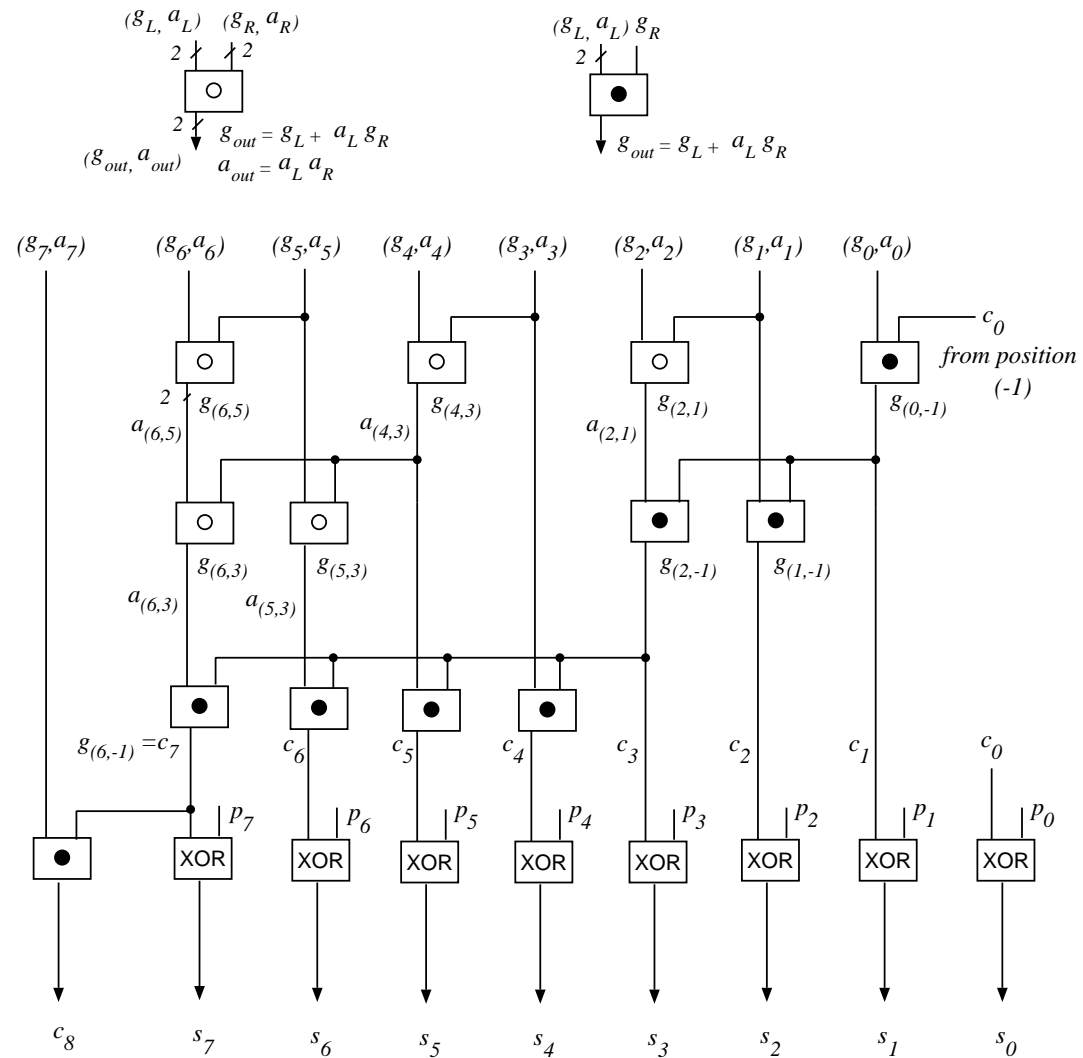


Figure 2.18: 8-bit prefix adder. (Modules to obtain p_i , g_i , and a_i signals not shown.)

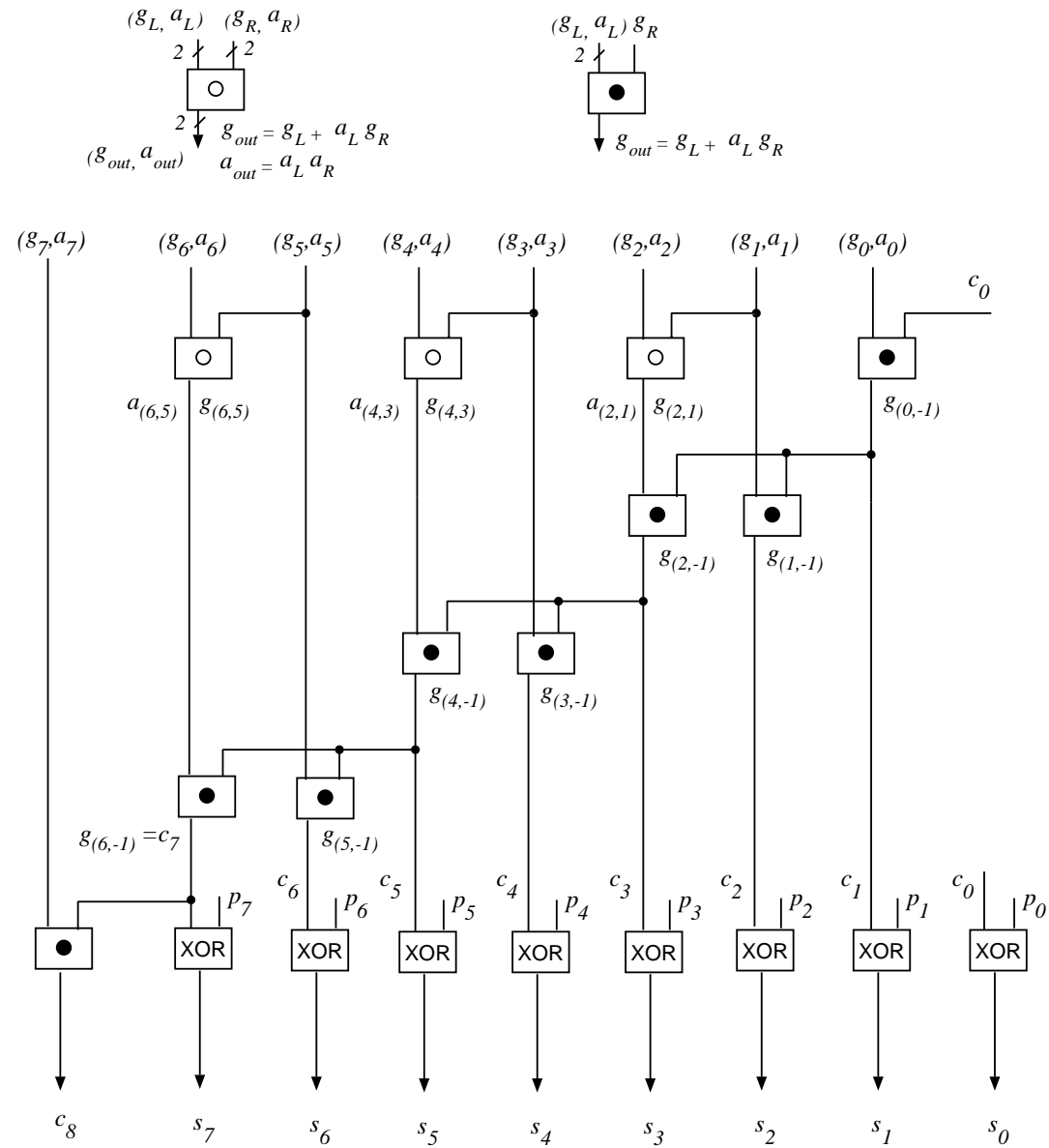


Figure 2.19: 8-bit prefix adder with maximum fanout of three and five levels. (Modules to obtain p_i , g_i , and a_i signals not shown.)

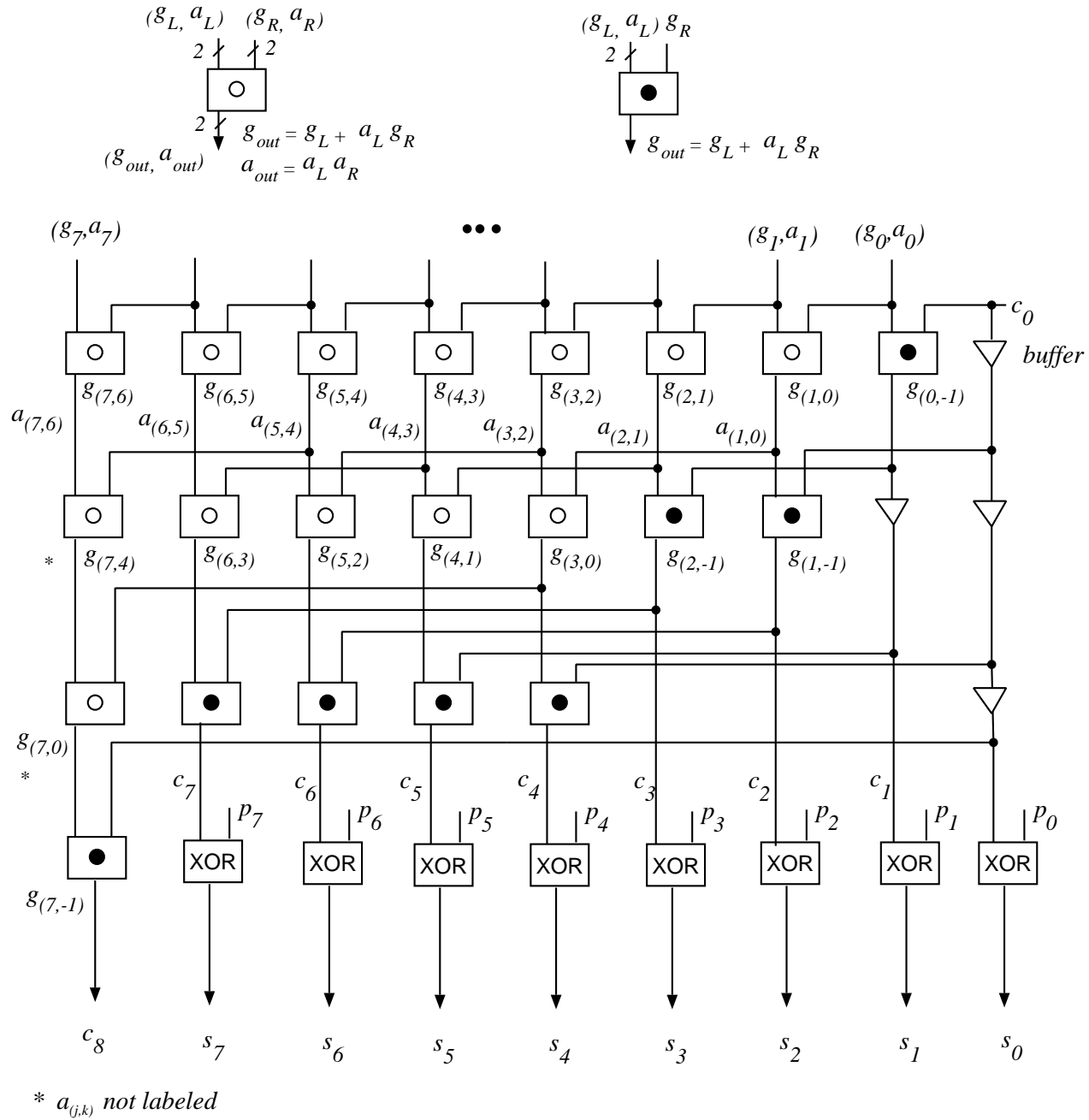


Figure 2.20: 8-bit prefix adder with minimum number of levels and fanout of two. (Modules to obtain p_i , g_i , and a_i signals not shown.)

CONDITIONAL ADDER (COND ADDER)

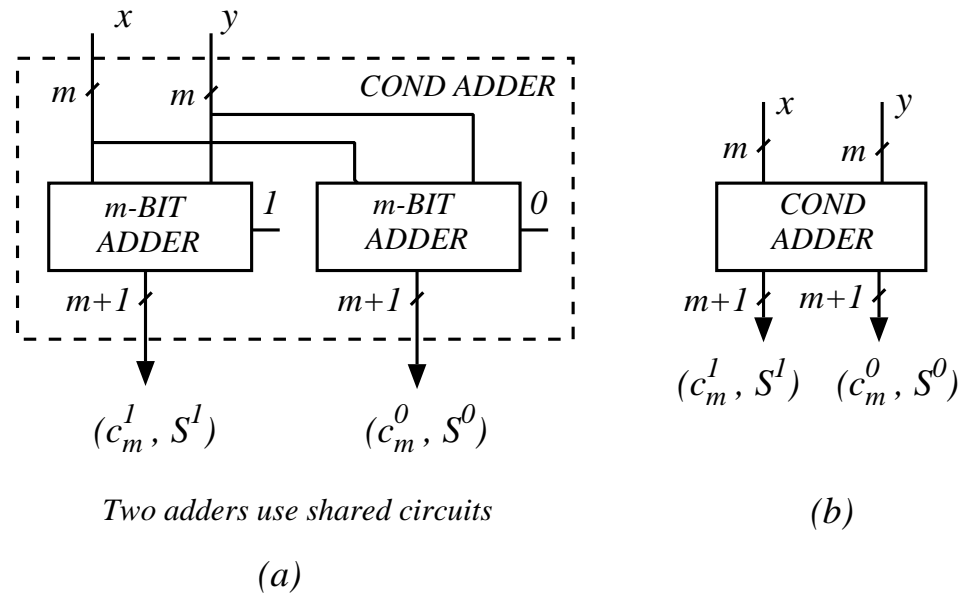


Figure 2.21: (a) Obtaining conditional outputs. (b) Combined conditional adder.

CARRY-SELECT ADDER

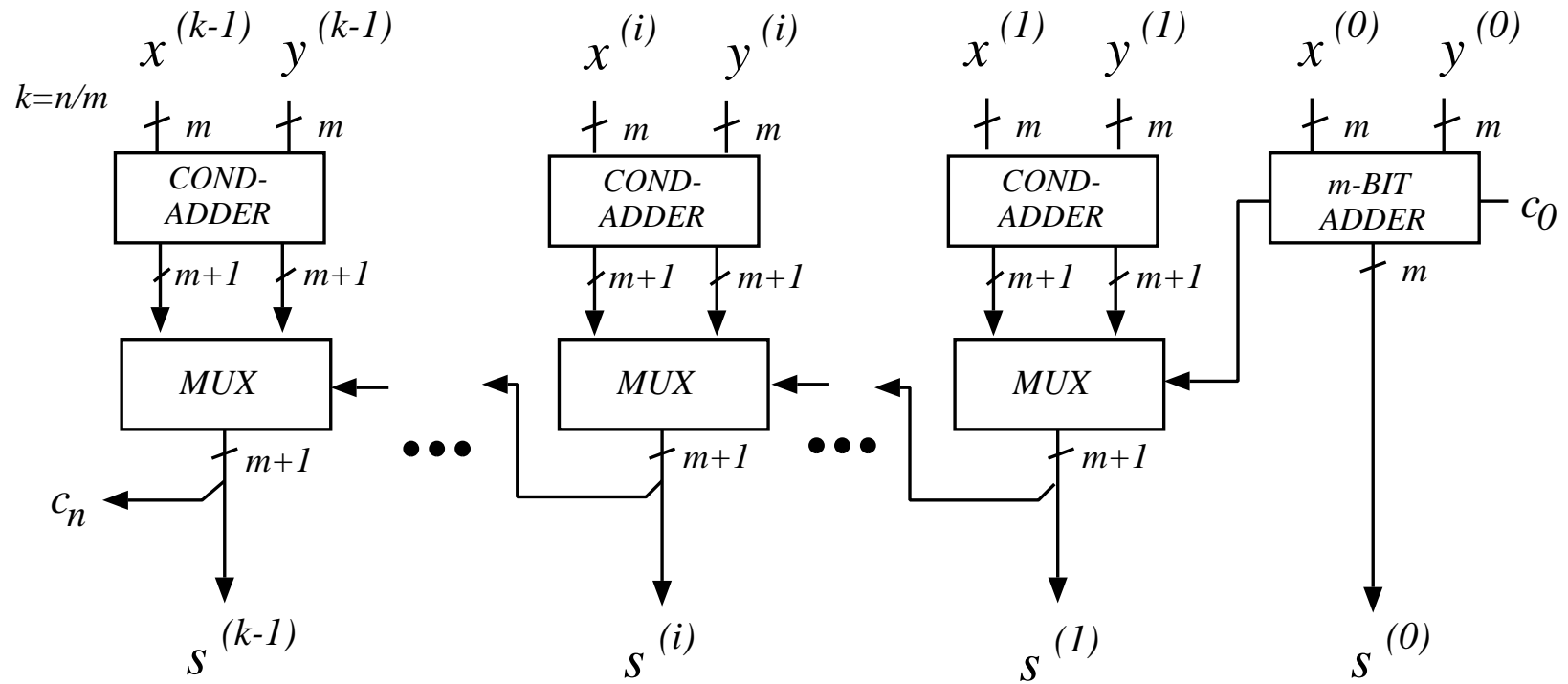


Figure 2.22: Carry-select adder.

CONDITIONAL-SUM ADDER

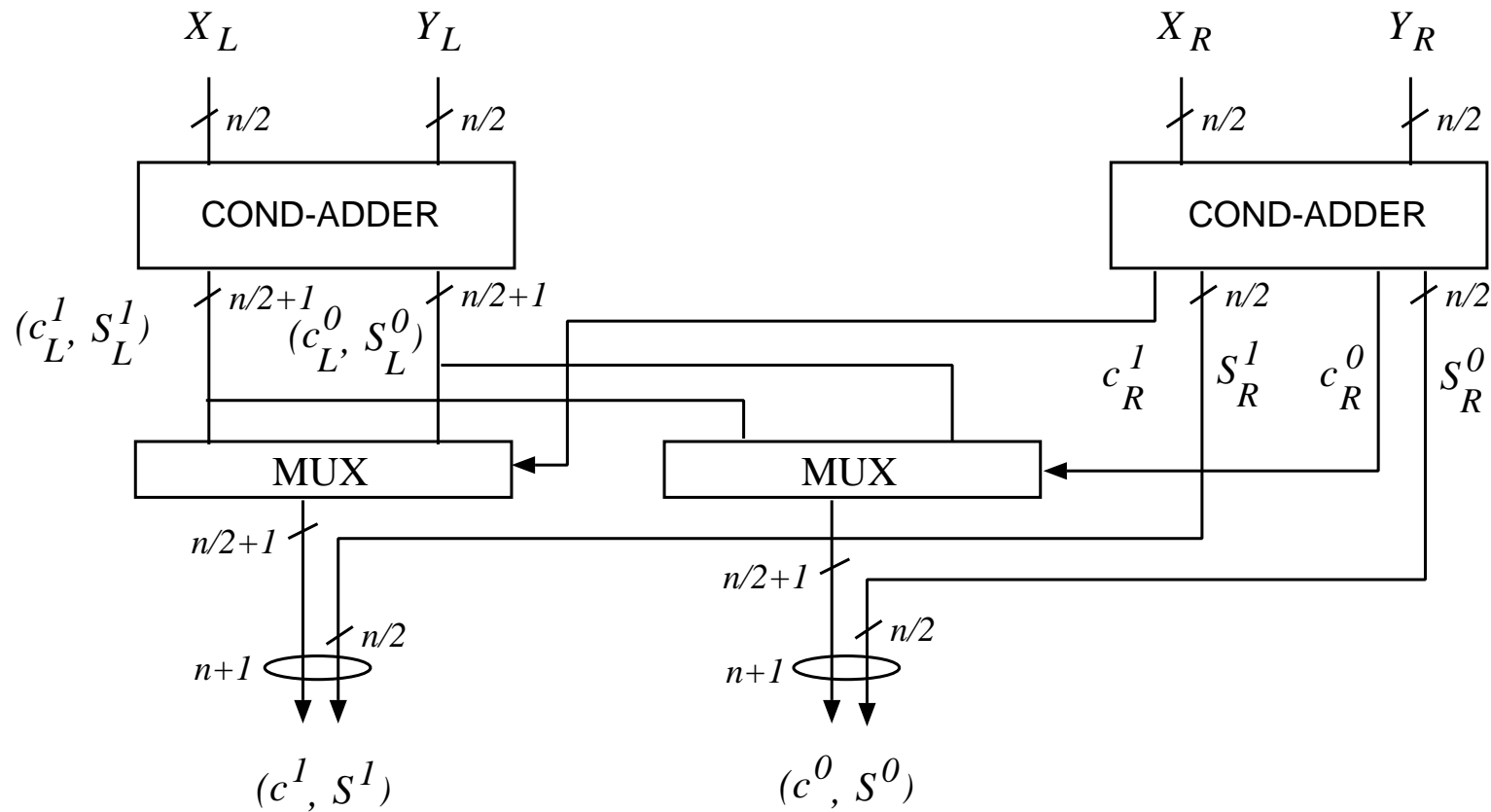


Figure 2.23: Doubling the number of bits of the conditional sum.

16-bit CONDITIONAL-SUM ADDER

 


Figure 2.24: 16-bit conditional-sum adder ($m = 4$).

TEMPLATE

s_3^0	s_2^0	s_1^0	s_0^0	Step 2
c_4^0		c_2^0		
s_3^1	s_2^1	s_1^1	s_0^1	
c_4^1		c_2^1		
s_3^0	s_2^0	s_1^0	s_0^0	Step 3
c_4^0				
s_3^1	s_2^1	s_1^1	s_0^1	
c_4^1				

Figure 2.25: Conditional-sum addition for eight bits with $m = 1$: (a) Template. (b) Example.

$$\begin{array}{rcccccccc}
 & 7 & 6 & 5 & 4 & 3 & 2 & 1 & 0 \\
 x & 0 & 1 & 0 & 1 & 1 & 0 & 1 & 1 & c_0 = 0 \\
 y & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \\
 \hline
 s^0 & 0 & 0 & 0 & 0 & 1 & 1 & 1 & 0 \\
 c^0 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1
 \end{array}$$

Step 1

$$\begin{array}{rcccccccc}
 s^1 & 1 & 1 & 1 & 1 & 0 & 0 & 0 \\
 c^1 & 0 & 1 & 0 & 1 & 1 & 1 & 1 \\
 \hline
 s^0 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 0 \\
 c^0 & 0 & & 0 & & 0 & & 1
 \end{array}$$

Step 2

$$\begin{array}{rcccccccc}
 s^1 & 1 & 1 & 1 & 1 & 0 & 0 \\
 c^1 & 0 & & 0 & & 1 \\
 \hline
 s^0 & 1 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 c^0 & 0 & & & & 1
 \end{array}$$

Step 3

$$\begin{array}{rcccccccc}
 s^1 & 1 & 0 & 1 & 1 \\
 c^1 & 0 \\
 \hline
 s & 1 & 0 & 1 & 1 & 0 & 0 & 0 & 0
 \end{array}$$

Increase throughput

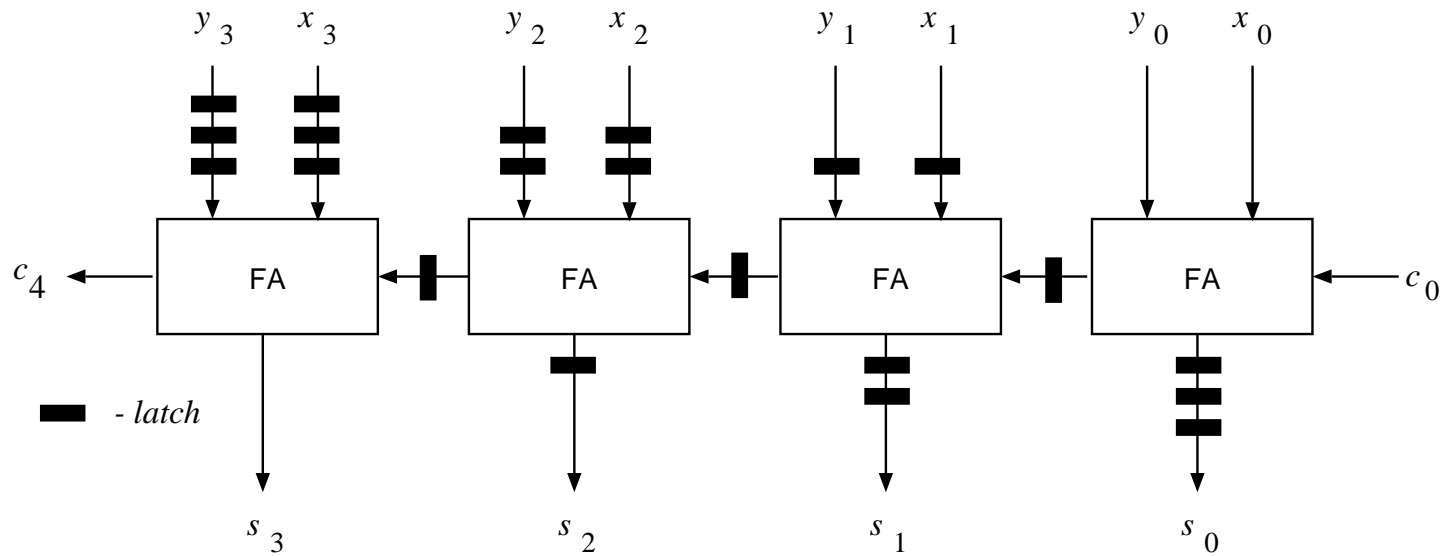


Figure 2.26: Pipelined carry-ripple adder (for group size of 1 and $n = 4$)

VARIABLE-TIME ADDER: Type 1

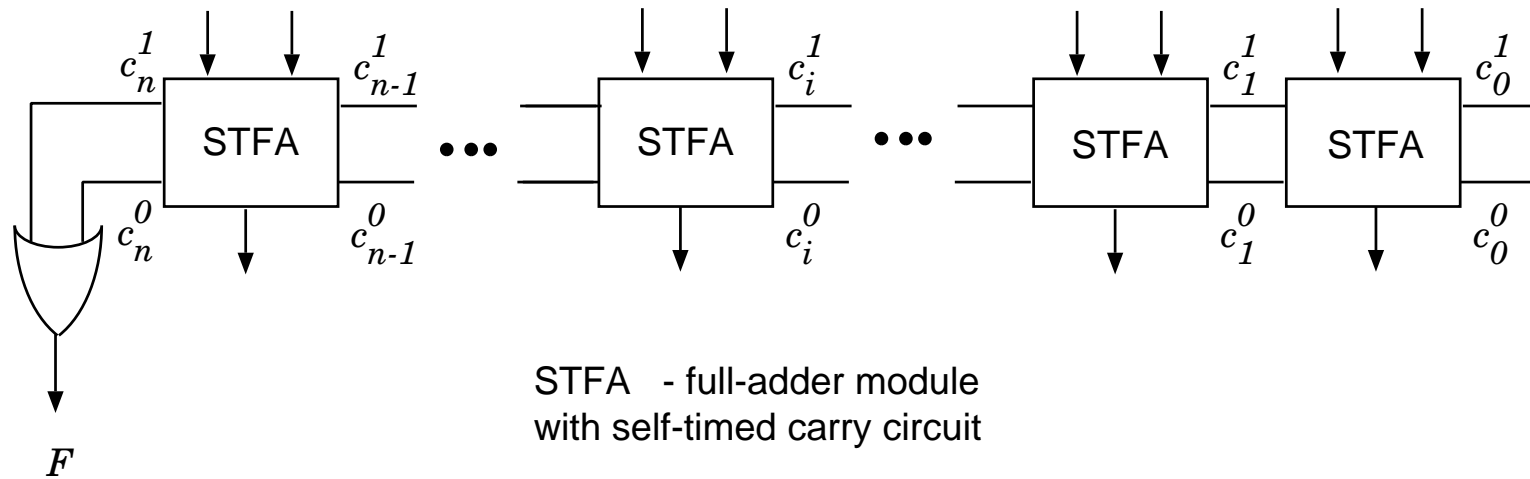


Figure 2.27: Variable-time adder: Type 1.

Two carry signals:

c_i^0 zero carry c_i^1 one carry

with coding:

c_i^0	c_i^1	c_i
0	0	not determined (yet)
0	1	1
1	0	0
1	1	does not occur

VARIABLE-TIME ADDER: Type 1 cont.

STFA module expressions:

$$\begin{aligned}c_{i+1}^0 &= k_i(c_i^0 + c_i^1) + p_i c_i^0 = k_i c_i^1 + (p_i + k_i) c_i^0 \\c_{i+1}^1 &= g_i(c_i^0 + c_i^1) + p_i c_i^1 = g_i c_i^0 + (p_i + g_i) c_i^1 \\s_i &= p_i \oplus c_i^1\end{aligned}$$

$$k_i = x_i' y_i', \quad g_i = x_i y_i, \quad p_i = x_i \oplus y_i$$

Addition time: based on *actual* delays, not worst-case

$$T_{var-1} = \sum_{i=0}^{n-1} t_{c,i}$$

VARIABLE-TIME ADDER: Type 2

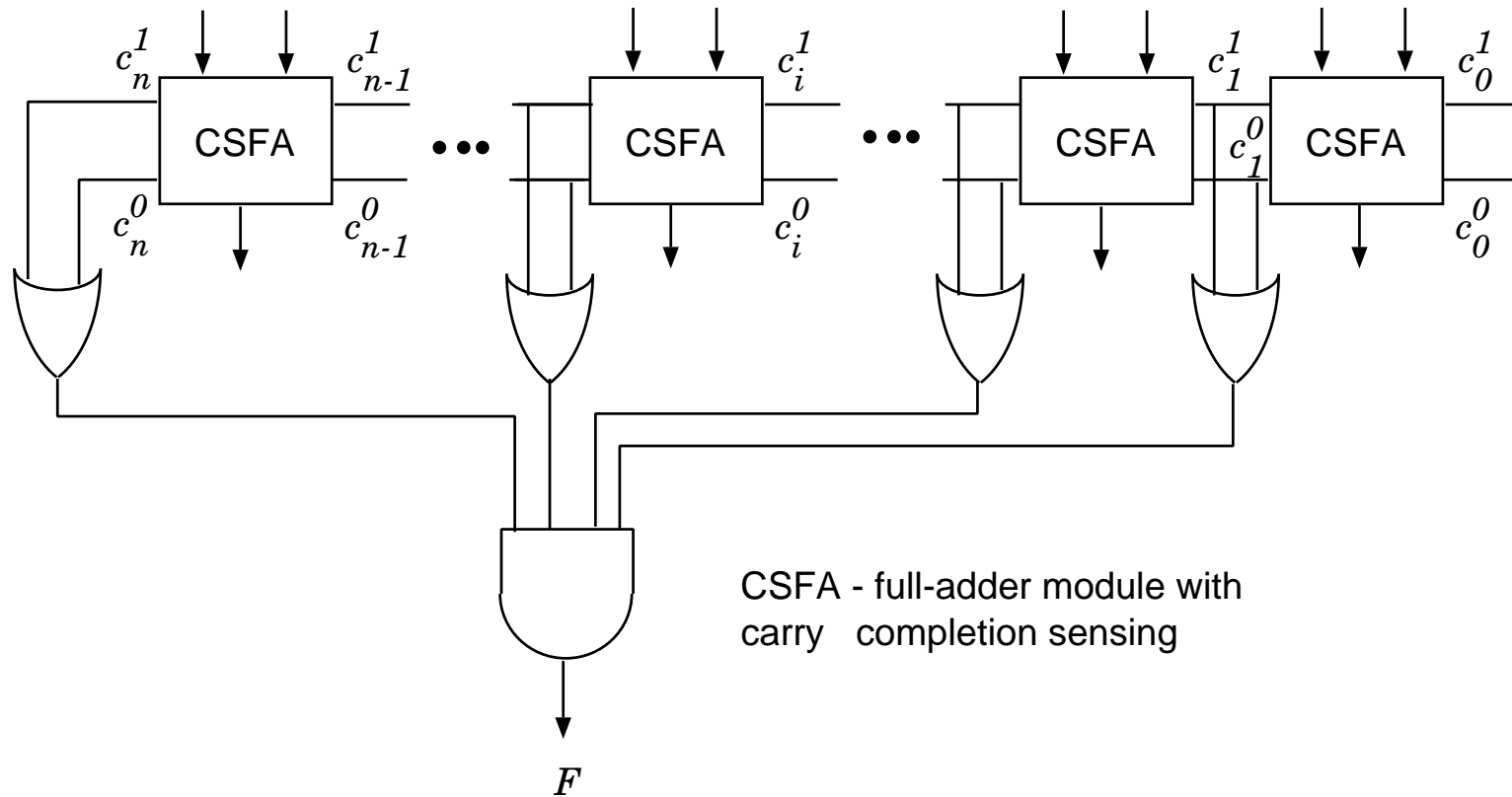


Figure 2.28: Variable-time adder: Type 2.

Carry chains initiated simultaneously
 CSFA module expressions:

$$c_{i+1}^0 = k_i + p_i c_i^0, \quad c_{i+1}^1 = g_i + p_i c_i^1$$

Example

X	0	1	1	0	0	0	1	1	1	0	0	1	1	0	1	0	
Y	1	0	1	0	1	1	0	0	1	1	1	0	0	1	1	0	
+	a	a	a	b	c	c	c	c	c	d	d	d	d	d	d	e	Prop.chains

Completion signal:

$$F = \prod_{i=0}^{n-1} (c_i^0 + c_i^1)$$

Addition time: proportional to $\log_2(n)$

2's COMPLEMENT AND 1s' COMPLEMENT ADDERS

 


Figure 2.29: Implementing ones' complement adder with prefix network. (Modules to obtain p_i , g_i , and a_i signals not shown.)

ADDERS WITH REDUNDANT DIGIT-SET

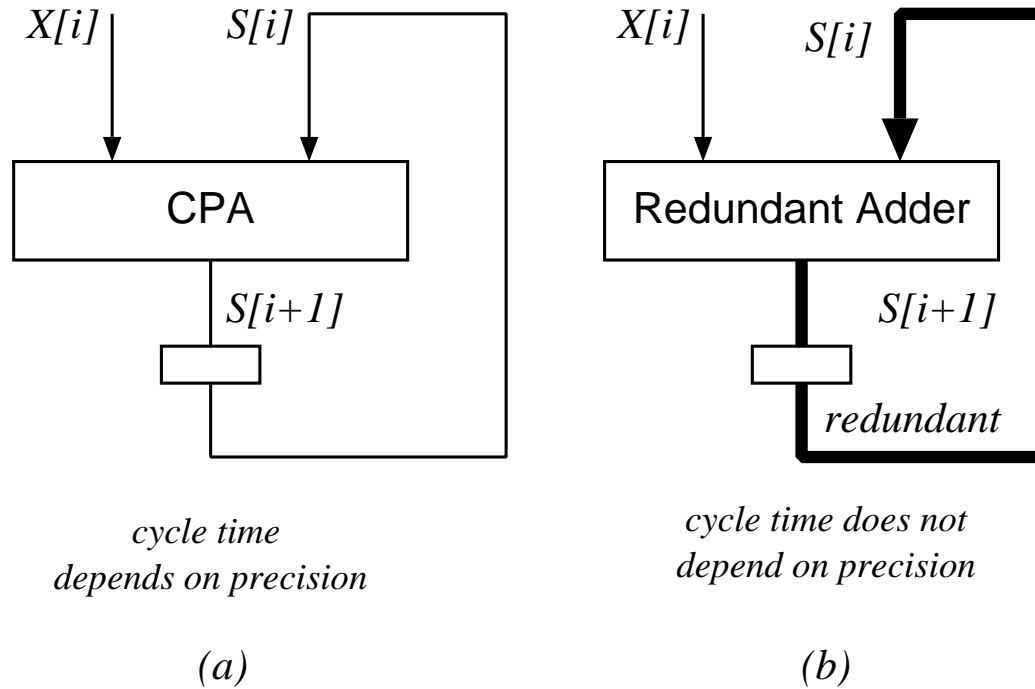


Figure 2.30: Accumulation with (a) non-redundant, and (b) redundant representation of sum.

CARRY-SAVE ADDER

 


Figure 2.31: Carry-save adder: (a) Bit level. (b) Bit-vector level.

EXAMPLE OF CARRY-SAVE OPERATION

X	0	1	1	1	0	1	0	0
Y	0	0	1	1	1	0	1	1
Z	1	0	1	0	1	0	1	0
VS	1	1	1	0	0	1	0	1
(c_{out}, VC)	0	0	1	1	1	0	1	0
digit value	0	1	2	2	1	0	2	0

[4:2] ADDER

 


Figure 2.32: [4:2] adder.

HIGH RADIX CARRY-SAVE REPRESENTATION

XS	1 0 1	1 0 1	1 0 0
XC		1	0
Y	0 1 0	0 0 1	1 1 1
VS	0 0 0	1 1 1	0 1 1
(c_{out}, VC)	1	0	1

 


Figure 2.33: Radix-8 carry-save adder.

SIGNED-DIGIT ADDITION

- Uses signed-digit representation (redundant)

$$x = \sum_0^{n-1} x_i r^i$$

with digit set

$$D = \{-a, \dots, -1, 0, 1, \dots, a\}$$

- Limits carry propagation to next position
- Addition algorithm:

$$\begin{aligned} \text{Step 1: } x + y &= w + t \\ x_i + y_i &= w_i + r t_{i+1} \end{aligned}$$

$$\begin{aligned} \text{Step 2: } s &= w + t \\ s_i &= w_i + t_i \end{aligned}$$

- No carry produced in Step 2

SD ADDER

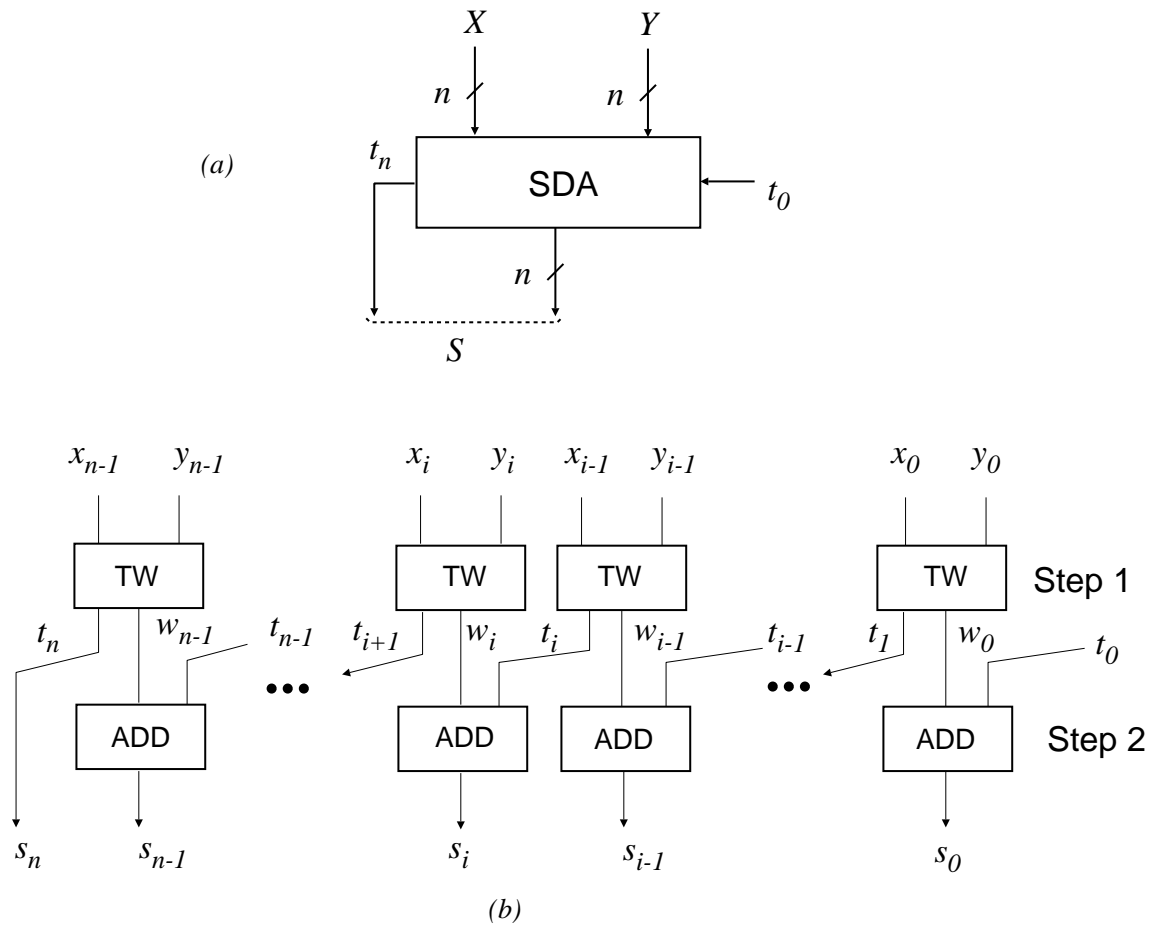


Figure 2.34: Signed-digit addition.

CASES CONSIDERED

Case A : two SD operands; result SD

Step 1:

$$(t_{i+1}, w_i) = \begin{cases} (0, x_i + y_i) & \mathbf{if} \ -a + 1 \leq x_i + y_i \leq a - 1 \\ (1, x_i + y_i - r) & \mathbf{if} \ x_i + y_i \geq a \\ (-1, x_i + y_i + r) & \mathbf{if} \ x_i + y_i \leq -a \end{cases}$$

- algorithm modified for $r = 2$

Case B : two conventional operands; result SD

Case C : one conventional, one SD; result SD

RECODING 1:

$$\begin{aligned}x_i + y_i &= 2h_{i+1} + z_i \in \{-2, -1, 0, 1, 2\} \\h_i &\in \{0, 1\}, z_i \in \{-2, -1, 0\} \\q_i &= z_i + h_i \in \{-2, -1, 0, 1\}\end{aligned}$$

RECODING 2:

$$\begin{aligned}q_i = z_i + h_i &= 2t_{i+1} + w_i \in \{-2, -1, 0, 1\} \\t_i &\in \{-1, 0\}, w_i \in \{0, 1\}\end{aligned}$$

THE RESULT: $s_i = w_i + t_i \in \{-1, 0, 1\}$

METHOD 1 SD ADDER

 


Figure 2.35: Double recoding method for signed-bit addition

SIGNED BINARY ADDITION: METHOD 2 (Using Previous Digit)

$$P_i = \begin{cases} 0 & \text{if } (x_i, y_i) \text{ both nonnegative} \\ & \text{(which implies } t_{i+1} \geq 0) \\ 1 & \text{otherwise } (t_{i+1} \leq 0) \end{cases}$$

$x_i + y_i$	P_{i-1}	t_{i+1}	w_i
2	-	1	0
1	$0(t_i \geq 0)$	1	-1
1	$1(t_i \leq 0)$	0	1
0	-	0	0
-1	$0(t_i \geq 0)$	0	-1
-1	$1(t_i \leq 0)$	-1	1
-2	-	-1	0

METHOD 2 SD ADDER

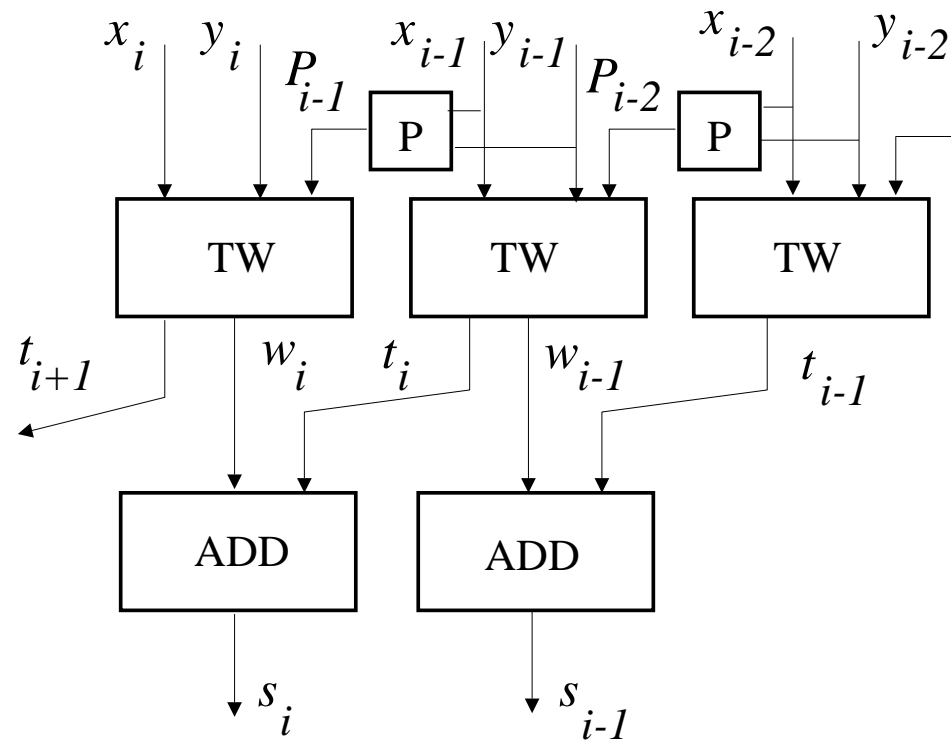


Figure 2.36: Signed-bit addition using the information from previous digit

Example

X 0 1 1 1 $\bar{1}$ 1 0 $\bar{1}$ 1

Y 0 1 1 0 $\bar{1}$ 0 1 0 1

P 0 0 0 0 1 0 0 1 0

W 0 0 0 1 0 $\bar{1}$ 1 $\bar{1}$ 0

T 0 1 1 0 $\bar{1}$ 1 0 0 1 0

S 1 1 0 0 1 $\bar{1}$ 1 0 0

- Case C: $x_i \in \{0, 1\}$, $y_i, s_i \in \{-1, 0, 1\}$
- Code: borrow-save $y_i = y_i^+ - y_i^-$, $y_i^+, y_i^- \in \{0, 1\}$, sim. for s_i
- $x_i + y_i \in \{-1, 0, 1, 2\}$: recode to (t_{i+1}, w_i) , $t_{i+1} \in \{0, 1\}$, $w_i \in \{-1, 0\}$

$$x_i + y_i^+ - y_i^- = 2t_{i+1} + w_i$$

$x_i + y_i$	-1	0	1	2
w_i	-1	0	-1	0
t_{i+1}	0	0	1	1

SWITCHING FUNCTIONS FOR t_{i+1} AND w_i

x_i	y_i^+	y_i^-	$x_i + y_i$	t_{i+1}	$-w_i$
0	0	0	0	0	0
0	0	1	-1	0	1
0	1	0	1	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	2	1	0
1	1	1	1	1	1

$$w_i = (x_i \oplus y_i^+ \oplus (y_i^-)')'$$

$$t_{i+1} = x_i y_i^+ + x_i (y_i^-)' + y_i^+ (y_i^-)'$$

\implies implemented using a full-adder and inverters (for variables subtracted)

 


Figure 2.37: Redundant adder: one operand conventional, one operand redundant, result redundant.

SUMMARY

Scheme	Delay proportional to	Area proportional to
Linear structures:		
Carry ripple	n	n
Carry lookahead (one level)	n/m	$(k_m m)(n/m) = k_m n$
Carry select (one level)	n/m	$(k_m m)(n/m) = k_m n$
Carry skip (one level)	\sqrt{n}	n
Logarithmic structures:		
Carry lookahead (max. levels)	$2 \log_m n$	$(k_m m)(n/m) = k_m n$
Prefix	$\log_m n$	$((k_m m) \log_m n)n$
Conditional sum	$\log_2(n/m)$	$(k_m + \log_2(n/m))n$
Completion signal (avg. delay)	$(\log_2 n)/m$	$k_m m(n/m) = k_m n$
Redundant	<i>const.</i>	n