

- 
- Bit-arrays for unsigned and signed operands
    - simplification of sign extension
  - Reduction by rows and by columns
    - $[p:2]$  modules and  $[p:2]$  adders for reduction by rows
    - $(p:q)$  counters and multicolumn counters for reduction by columns
  - Sequential implementation
  - Combinational implementation
    - Reduction by rows: arrays of adders (linear arrays, adder trees)
    - Reduction by columns:  $(p:q)$  counters
    - systematic design method for reduction by columns with  $(3:2)$  and  $(2:2)$  counters
  - Pipelined adder arrays
  - Partially combinational implementation

## BIT ARRAYS FOR UNSIGNED AND SIGNED OPERANDS

---

2

$$\begin{array}{l} a_0 a_0 a_0 a_0 \cdot a_1 a_2 \cdots a_n \\ b_0 b_0 b_0 b_0 \cdot b_1 b_2 \cdots b_n \\ c_0 c_0 c_0 c_0 \cdot c_1 c_2 \cdots c_n \\ d_0 d_0 d_0 d_0 \cdot d_1 d_2 \cdots d_n \\ \underbrace{e_0 e_0 e_0 e_0}_{\text{sign extension}} \cdot e_1 e_2 \cdots e_n \end{array}$$

sign extension

Figure 3.1: SIGN-EXTENDED ARRAY FOR  $m = 5$ .

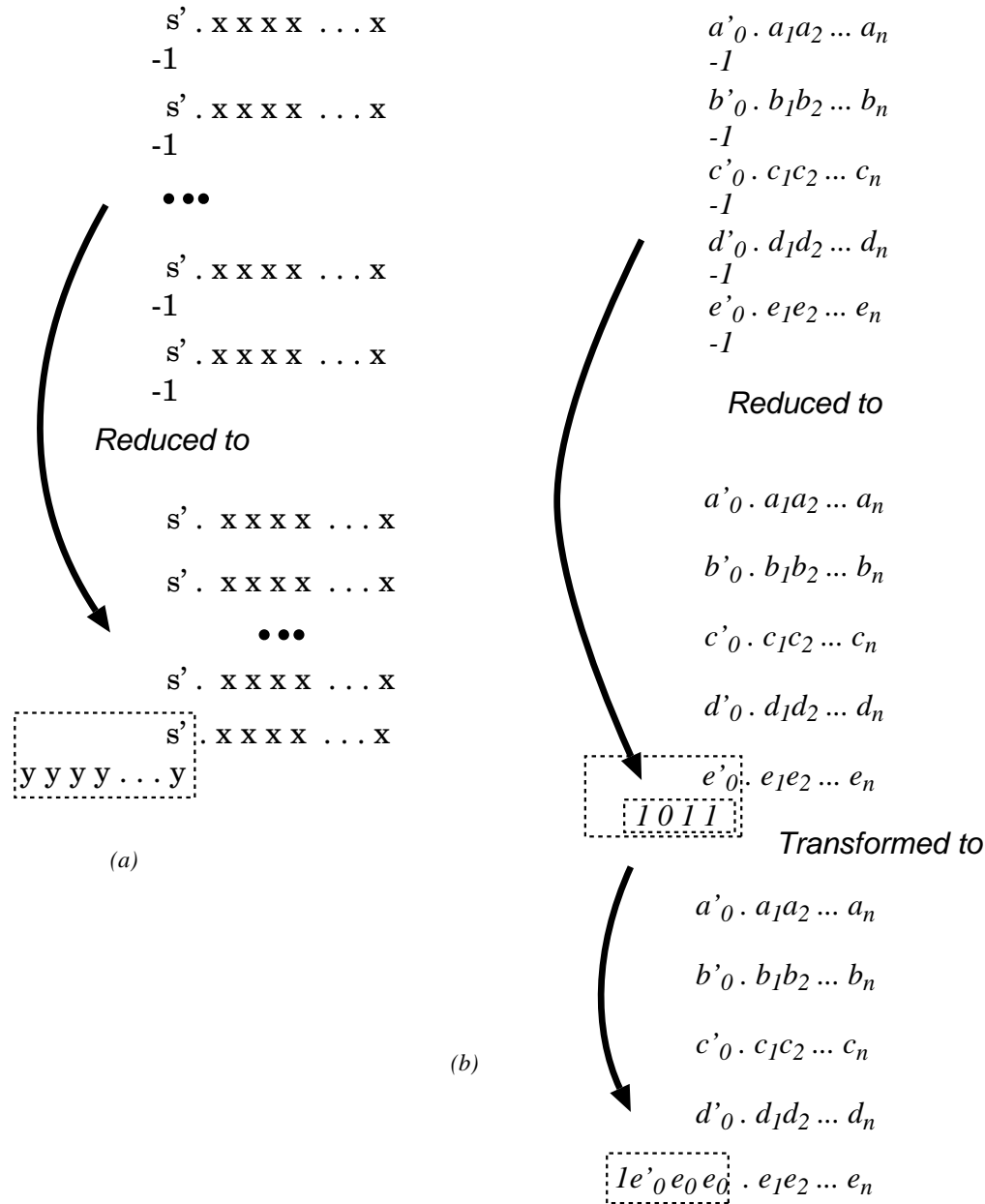


Figure 3.2: SIMPLIFYING SIGN-EXTENSION: (a) GENERAL CASE. (b) EXAMPLE OF SIMPLIFYING ARRAY WITH  $m = 5$ .

# REDUCTION

---

- By rows
- By columns

# $[p:2]$ ADDERS FOR REDUCTION BY ROWS

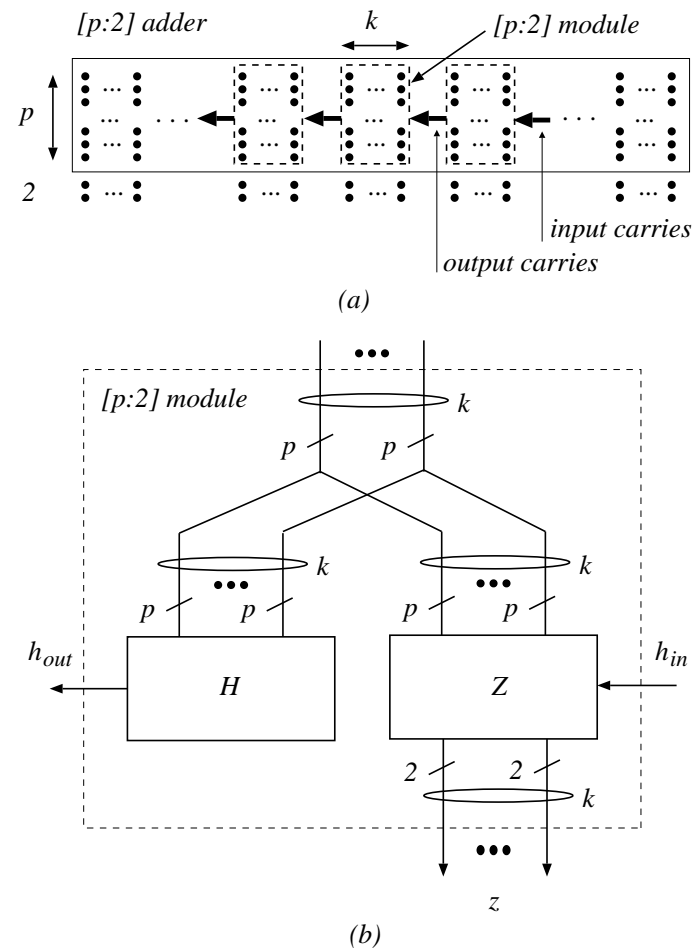


Figure 3.3: A  $[p:2]$  adder: (a) Input-output bit-matrix. (b)  $k$ -column  $[p:2]$  module decomposition.

# MODEL OF $[p:2]$ MODULE

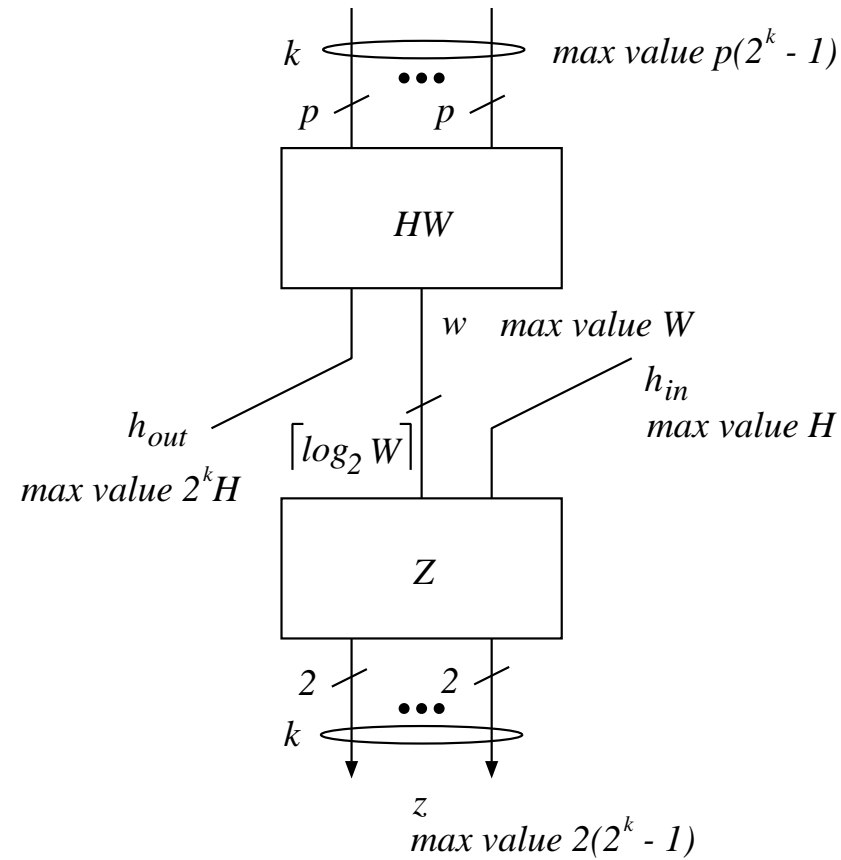


Figure 3.4: A model of a  $[p:2]$  module.

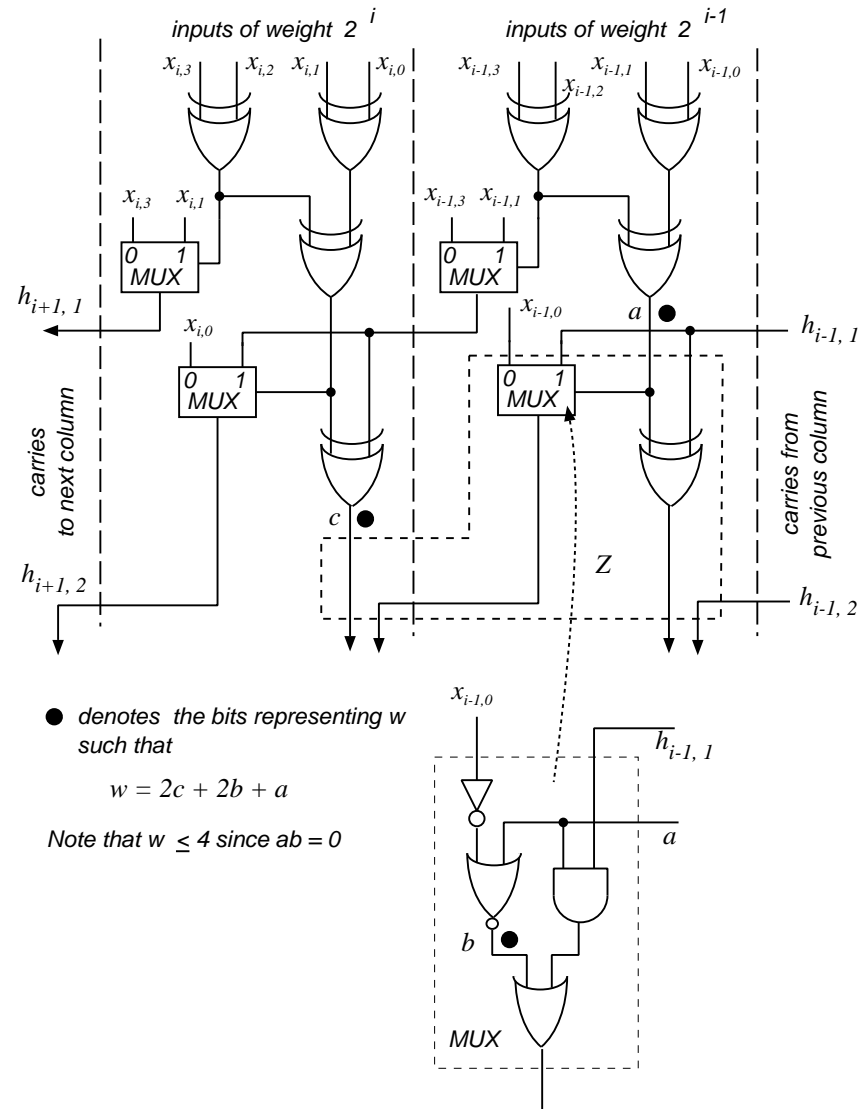


Figure 3.5: Gate network implementation of [4:2] module.

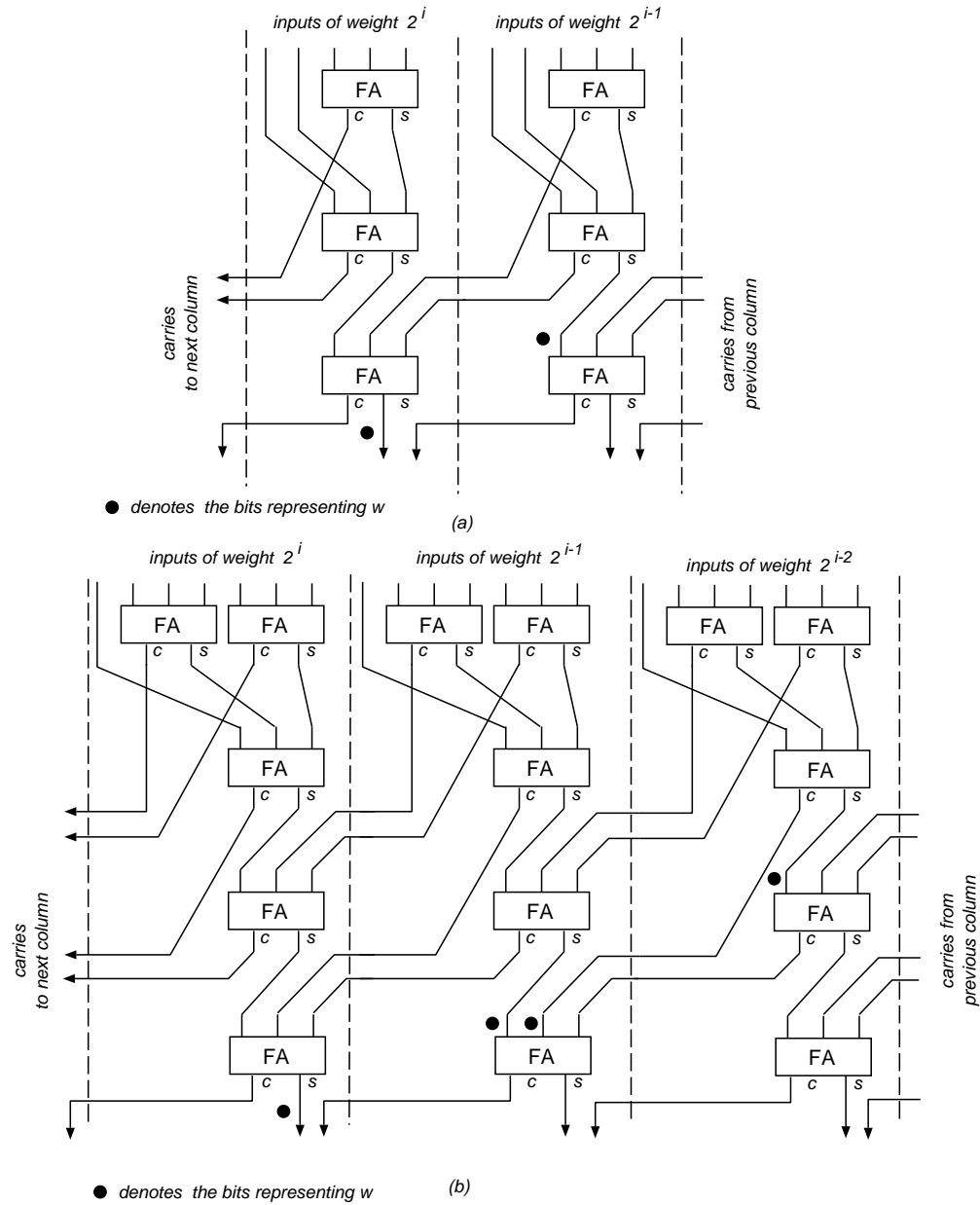


Figure 3.6: (a) [5:2] module. (b) [7:2] module.



# $(p:q]$ COUNTERS FOR REDUCTION BY COLUMNS

---

$$\sum_{i=0}^{p-1} x_i = \sum_{j=0}^{q-1} y_j 2^j$$

$$2^q - 1 \geq p, \text{ i.e., } q = \lceil \log_2(p + 1) \rceil$$

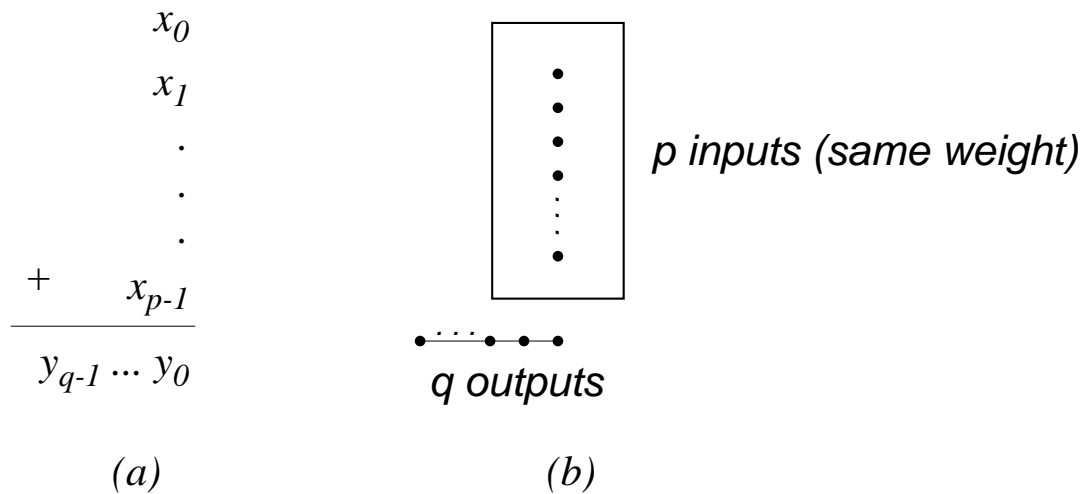


Figure 3.7: (a)  $(p:q]$  reduction. (b) Counter representation.

# IMPLEMENTATION OF $(p:q]$ COUNTERS

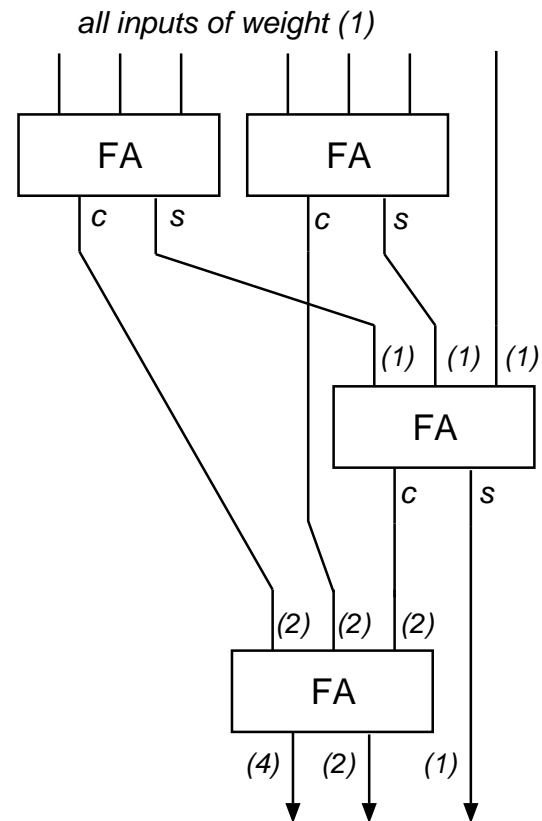


Figure 3.8: Implementation of  $(7:3]$  counter by an array of full adders.

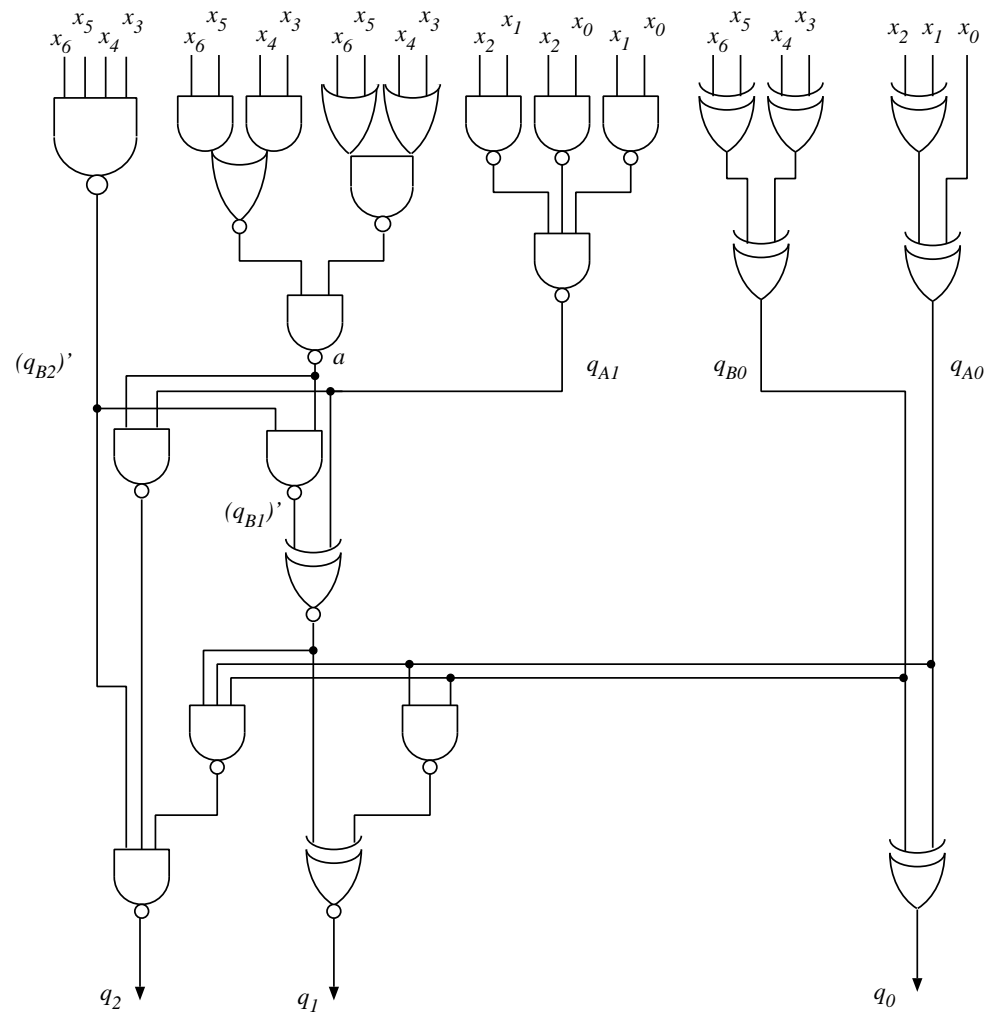


Figure 3.9: Gate network of a (7:3] counter.

# MULTICOLUMN COUNTER

---

$$(p_{k-1}, p_{k-2}, \dots, p_0 : q]$$

$$v = \sum_{i=0}^{k-1} \sum_{j=1}^{p_i} a_{ij} 2^i \leq 2^q - 1$$

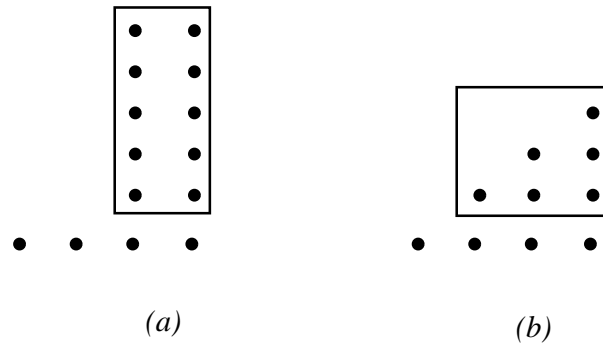


Figure 3.10: (a) (5,5:4] counter. (b) (1,2,3:4] counter.

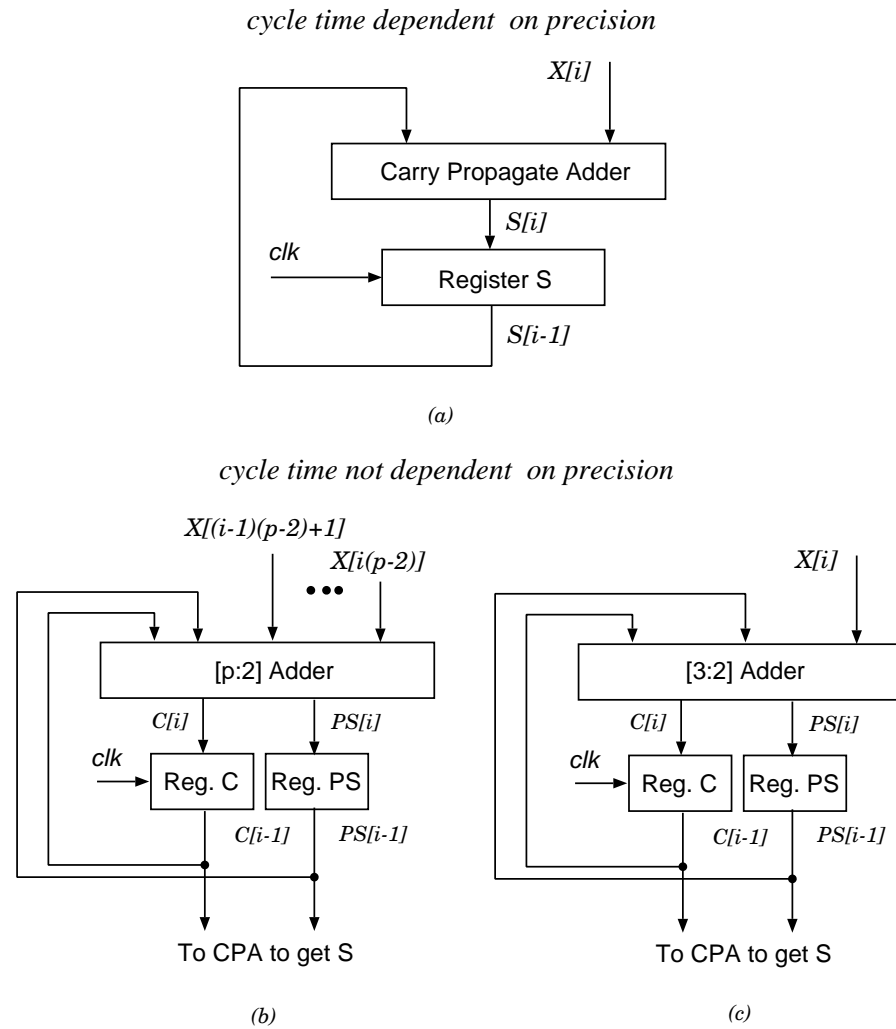


Figure 3.11: SEQUENTIAL MULTIOPERAND ADDITION: a) WITH CONVENTIONAL ADDER. b) WITH  $[p:2]$  ADDER. c) WITH  $[3:2]$  ADDER.

- Reduction by rows: array of adders
  - Linear array
  - Adder tree
- Reduction by columns with  $(p:q]$  counters

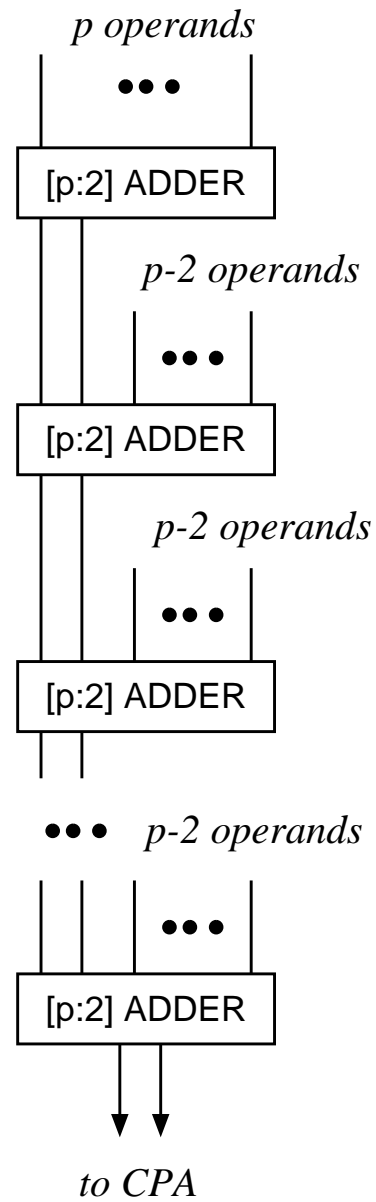


Figure 3.12: LINEAR ARRAY OF  $[p:2]$  ADDERS FOR MULTIOPERAND ADDITION.

# ADDER TREE

- $k$  - the number of  $[p:2]$  CS adders for  $m$  operands:

$$pk = m + 2(k - 1)$$

$$k = \left\lceil \frac{m - 2}{p - 2} \right\rceil \quad [p:2] \text{ carry-save adders}$$

- The number of adder levels

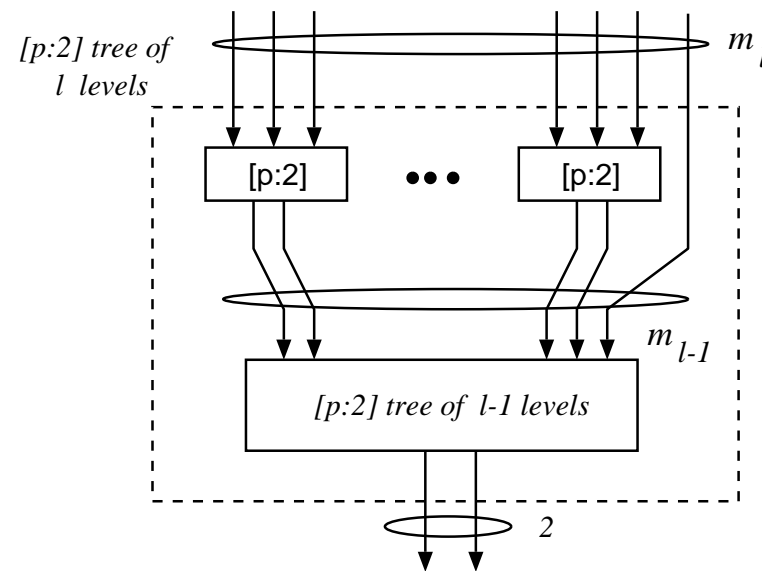


Figure 3.13: Construction of a  $[p:2]$  carry-save adder tree.

$$m_l = p \left\lfloor \frac{m_{l-1}}{2} \right\rfloor + m_{l-1} \bmod 2$$



## NUMBER OF LEVELS (cont.)

---

Table 3.1: [3:2] Reduction sequence.

$l$	1	2	3	4	5	6	7	8	9
$m_l$	3	4	6	9	13	19	28	42	63

$$m_l \approx \frac{p^l}{2^{l-1}}$$

$$l \approx \log_{p/2}(m_l/2)$$

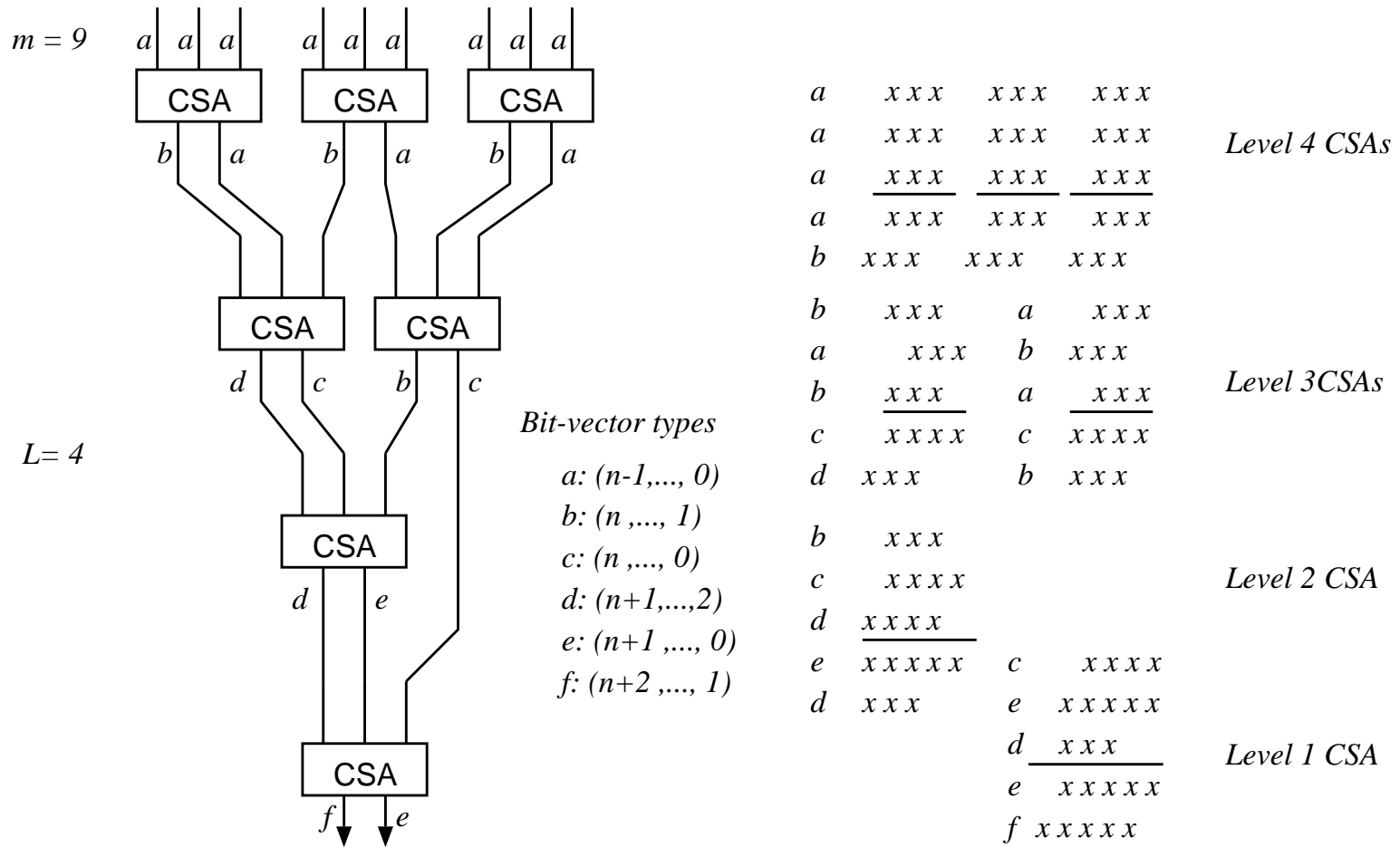


Figure 3.14: [3:2] adder tree for 9 operands (magnitudes with  $n = 3$ ).

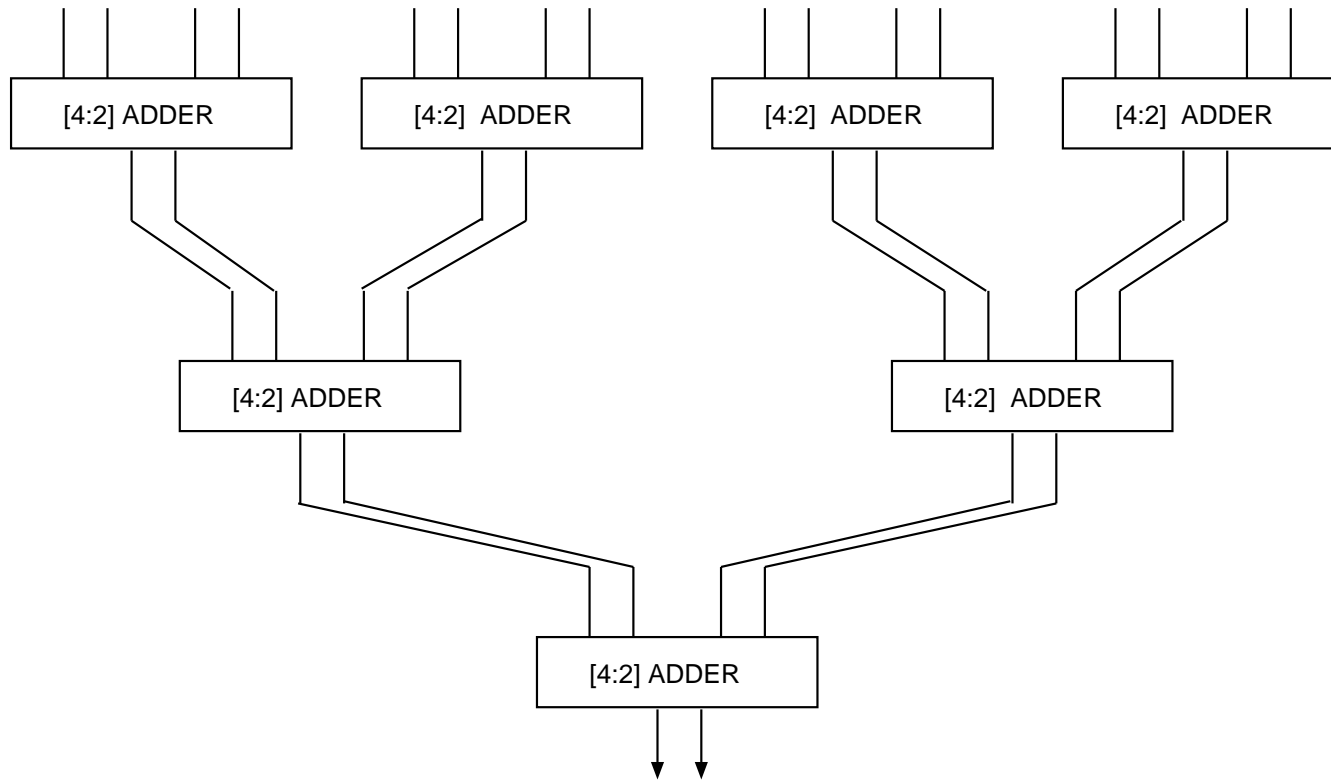


Figure 3.15: Tree of [4:2] adders for  $m = 16$ .

# REDUCTION BY COLUMNS WITH (p:q] COUNTERS

---

$$\begin{array}{rcccc}
 & 1 & 0 & 1 & 1 \\
 & 0 & 0 & 1 & 0 \\
 & 1 & 0 & 0 & 1 \\
 & 0 & 1 & 1 & 0 \\
 & 1 & 0 & 1 & 0 \\
 & 1 & 1 & 1 & 1 \\
 & 0 & 1 & 1 & 0 \\
 \hline
 & 0 & 1 & 0 & 1 \\
 & 0 & 1 & 1 & 1 \\
 1 & 0 & 1 & 0 & 
 \end{array}$$

Figure 3.16: Example of reduction using (7:3] counters.

# NUMBER OF COUNTER LEVELS

$$m_1 = p$$

$$m_l = p \left\lfloor \frac{m_{l-1}}{q} \right\rfloor + m_{l-1} \bmod q$$

$$l \approx \log_{p/q}(m_l/q)$$

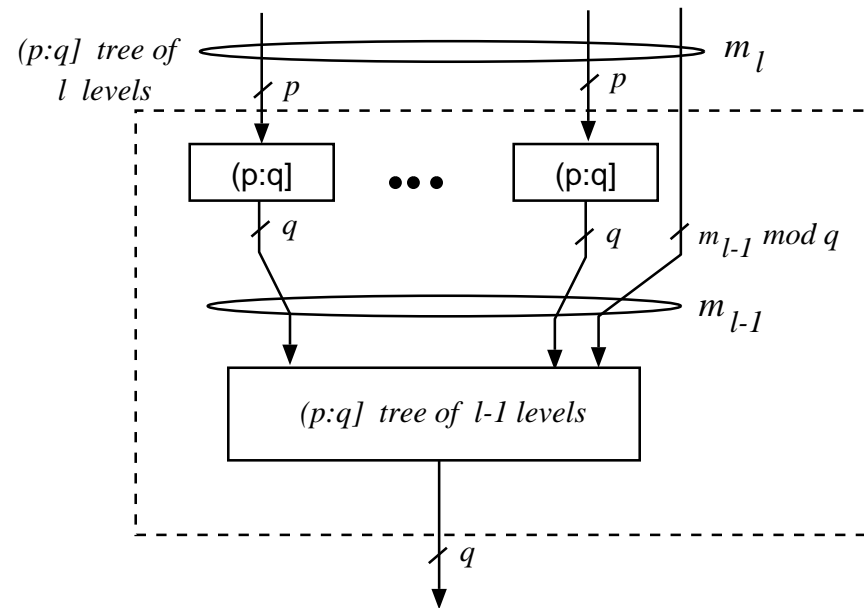


Figure 3.17: Construction of  $(p:q)$  reduction tree.

Table 3.2: Sequence for (7:3] counters

Number of levels	1	2	3	4	...
Max. number of rows	7	15	35	79	...

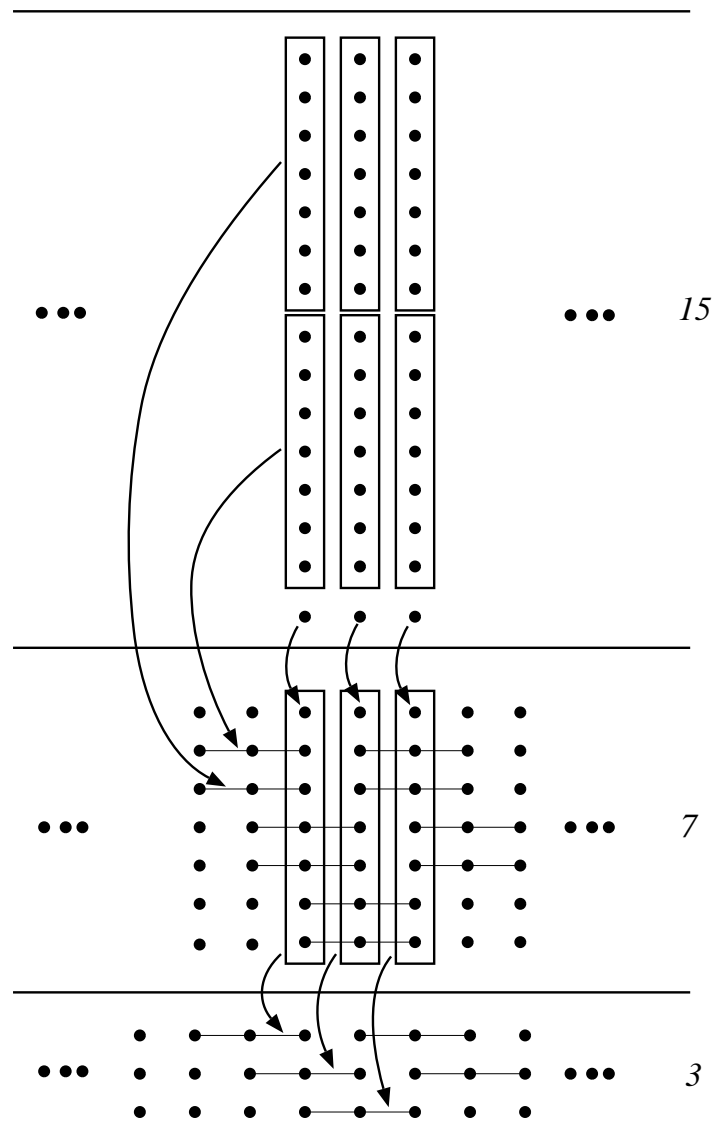


Figure 3.18: Multilevel reduction with  $(7:3]$  counters

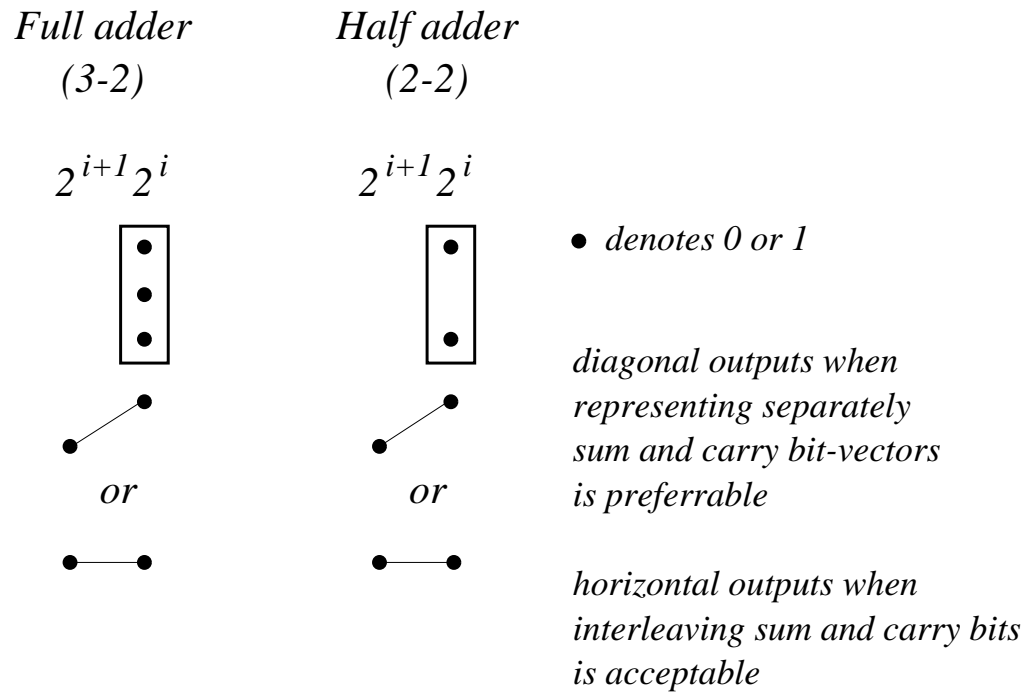


Figure 3.19: Full adder and half adder as (3:2] and (2:2] counters.



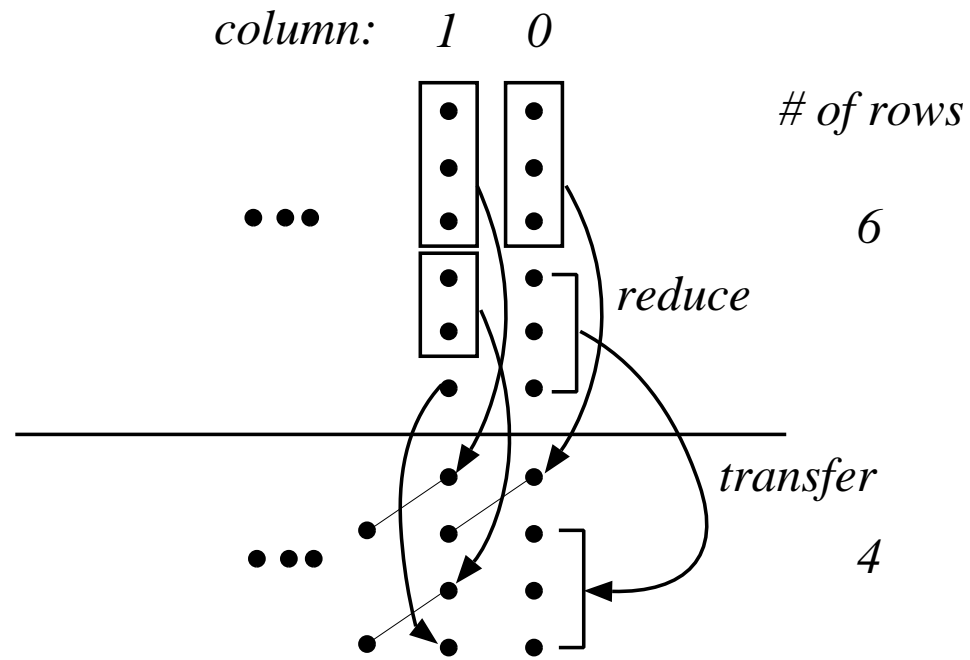


Figure 3.20: Reduction process.

## RELATION AT LEVEL $l$

---

$e_i$  – number of bits in column  $i$

$f_i$  – number of full adders in column  $i$

$h_i$  – number of half adders in column  $i$

$$e_i - 2f_i - h_i + f_{i-1} + h_{i-1} = m_{l-1}$$

resulting in

$$2f_i + h_i = e_i - m_{l-1} + f_{i-1} + h_{i-1} = p_i$$

Solution producing min number of carries:

$$f_i = \lfloor p_i/2 \rfloor \quad h_i = p_i \bmod 2$$

	$i$						
	6	5	4	3	2	1	0
$l = 4$							
$e_i$			8	8	8	8	8
$m_3$			6	6	6	6	6
$h_i$			0	0	0	1	0
$f_i$			2	2	2	1	1
$l = 3$							
$e_i$		2	6	6	6	6	6
$m_2$		4	4	4	4	4	4
$h_i$		0	0	0	0	1	0
$f_i$		0	2	2	2	1	1
$l = 2$							
$e_i$		4	4	4	4	4	4
$m_1$		3	3	3	3	3	3
$h_i$		0	0	0	0	0	1
$f_i$		1	1	1	1	1	0
$l = 1$							
$e_i$	1	3	3	3	3	3	3
$m_0$	2	2	2	2	2	2	2
$h_i$	0	0	0	0	0	0	1
$f_i$	0	1	1	1	1	1	0

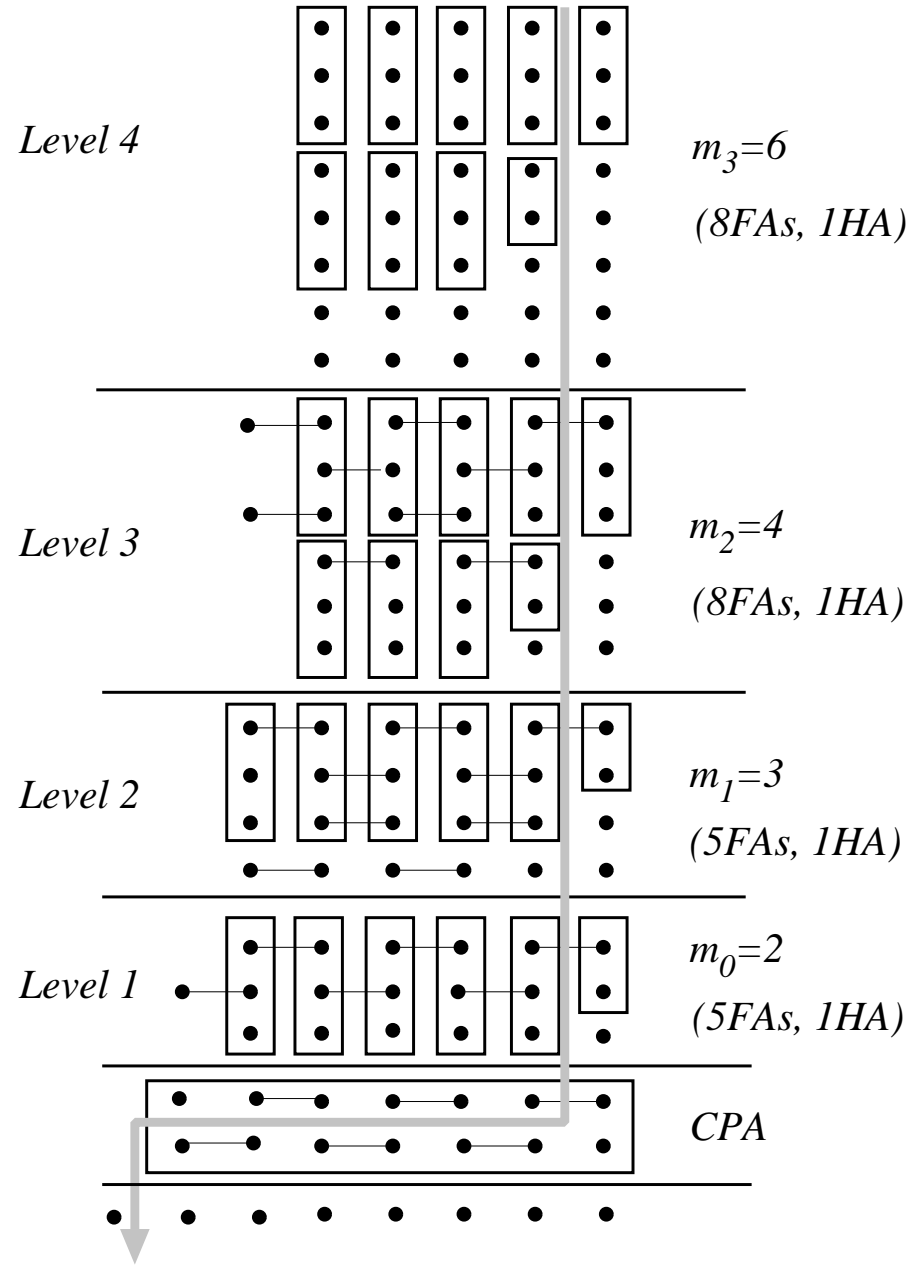


Figure 3.21: Reduction by columns of 8 5-bit magnitudes. Cost of reduction: 26 FAs and 4 HAs.

## EXAMPLE: ARRAY FOR $f = a + 3b + 3c + d$

---

Operands in  $[-4,3)$ . Result range:

$$-4 + (-12) + (-12) - 4 = -32 \leq f \leq 3 + 9 + 9 + 3 = 24$$

$$\begin{array}{r|rrrrrr}
 a & a_2 & a_2 & a_2 & a_2 & a_1 & a_0 \\
 b & b_2 & b_2 & b_2 & b_2 & b_1 & b_0 \\
 2b & b_2 & b_2 & b_2 & b_1 & b_0 & 0 \\
 c & c_2 & c_2 & c_2 & c_2 & c_1 & c_0 \\
 2c & c_2 & c_2 & c_2 & c_1 & c_0 & 0 \\
 d & d_2 & d_2 & d_2 & d_2 & d_1 & d_0
 \end{array}$$

transformed into

$$\begin{array}{r|rrrr}
 a & & a'_2 & a_1 & a_0 \\
 & & -1 & & \\
 b & & b'_2 & b_1 & b_0 \\
 & & -1 & & \\
 2b & b'_2 & b_1 & b_0 & \\
 & -1 & & & \\
 c & & c'_2 & c_1 & c_0 \\
 & & -1 & & \\
 2c & c'_2 & c_1 & c_0 & \\
 & -1 & & & \\
 d & & d'_2 & d_1 & d_0 \\
 & & -1 & &
 \end{array}$$


FINAL BIT MATRIX

---

$$\begin{array}{cccccc} 1 & 0 & b'_2 & a'_2 & a_1 & a_0 \\ & & c'_2 & b'_2 & b_1 & b_0 \\ & & & b_1 & b_0 & \\ & & & c'_2 & c_1 & c_0 \\ & & & c_1 & c_0 & \\ & & & d'_2 & d_1 & d_0 \end{array}$$

	$i$					
	5	4	3	2	1	0
$l = 3$						
$e_i$	1	0	2	6	6	4
$m_2$	4	4	4	4	4	4
$h_i$	0	0	0	1	0	0
$f_i$	0	0	0	1	1	0
$l = 2$						
$e_i$	1	0	4	4	4	4
$m_1$	3	3	3	3	3	3
$h_i$	0	0	0	0	0	1
$f_i$	0	0	1	1	1	0
$l = 1$						
$e_i$	1	1	3	3	3	3
$m_0$	2	2	2	2	2	1*
$h_i$	0	0	0	0	0	0
$f_i$	0	0	1	1	1	1



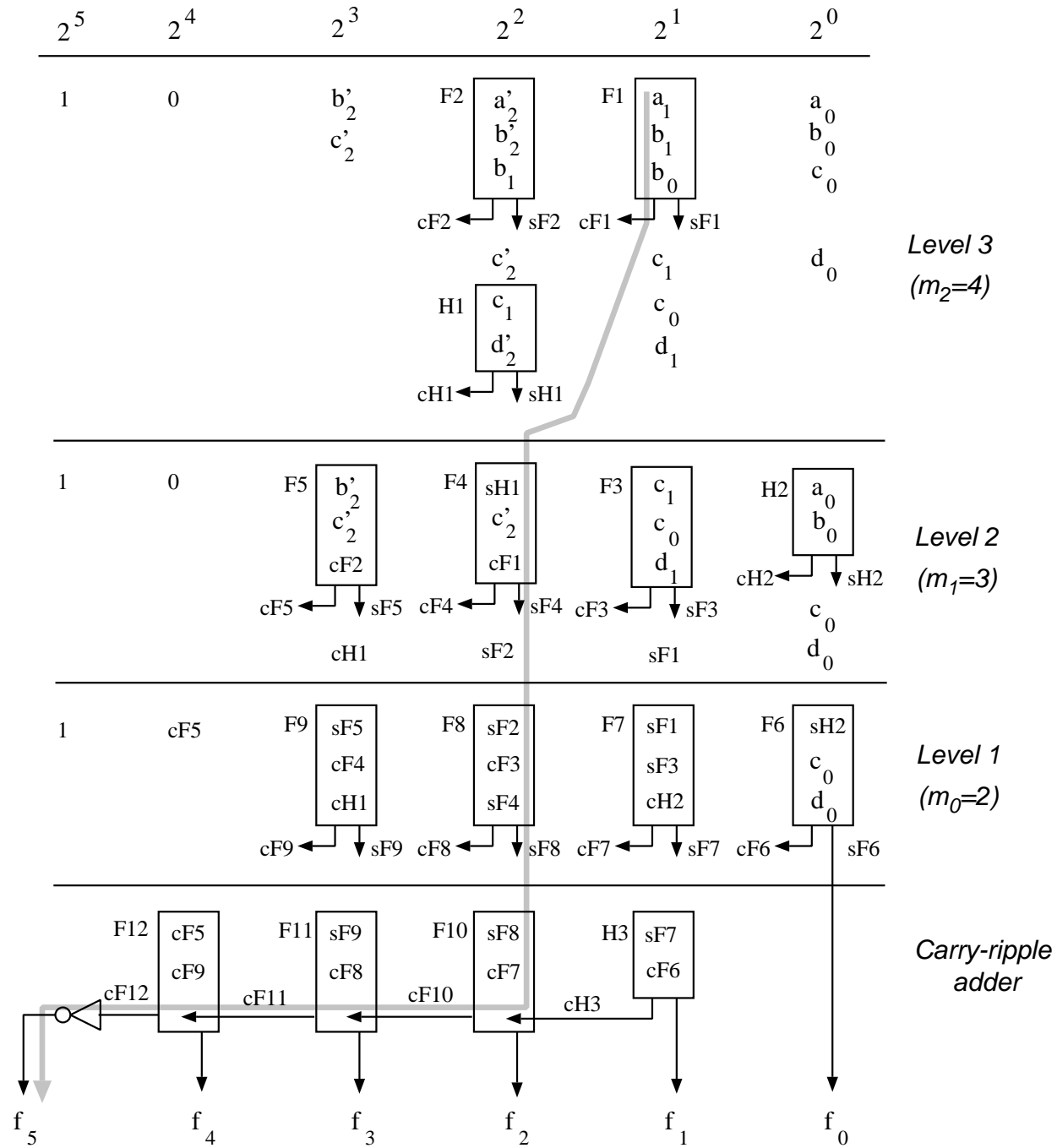

Digital Arithmetic - Ercegovac/Lang 2003 Figure 3.22: Reduction array  $f = a + 3b + 3c + d$ .

# PIPELINED LINEAR ARRAY

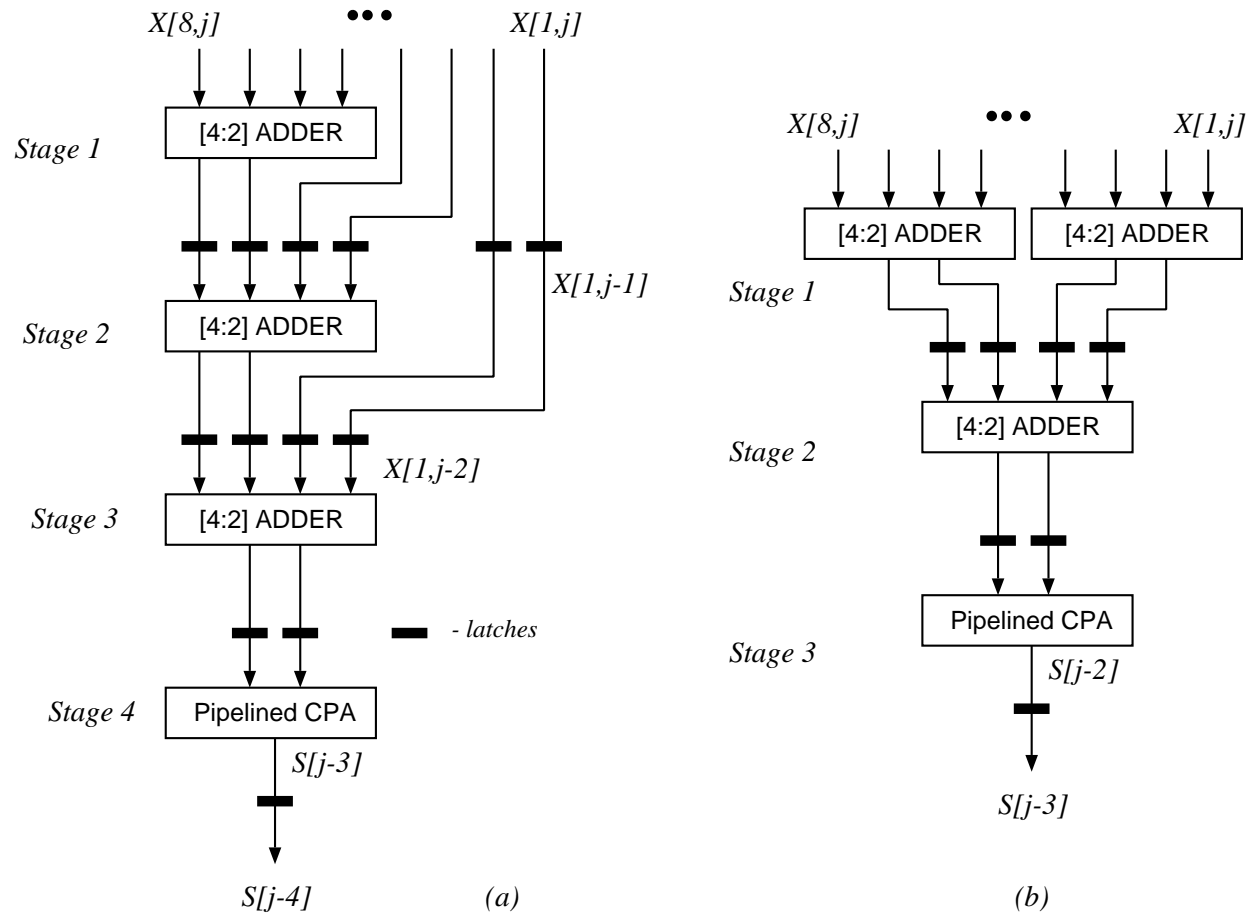


Figure 3.23: Pipelined arrays with [4:2] adders for computing  $S[j] = \sum_{i=1}^8 X[i, j]$ ,  $j = 1, \dots, N$ : (a) Linear array. (b) Tree array.

# PARTIALLY COMBINATIONAL IMPLEMENTATION

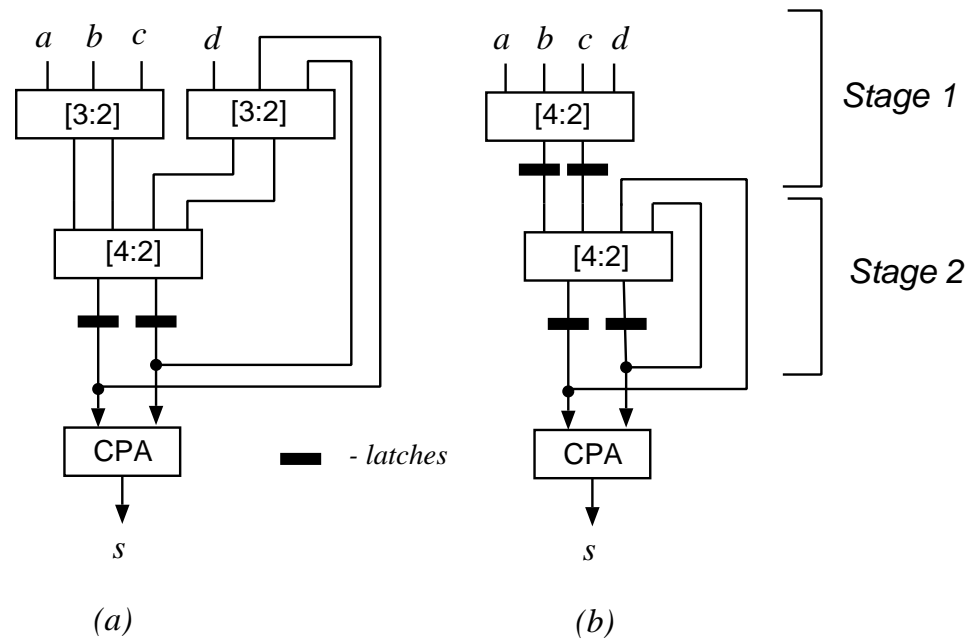


Figure 3.24: Partially combinational scheme for summation of 4 operands per iteration: (a) Nonpipelined. (b) Pipelined.

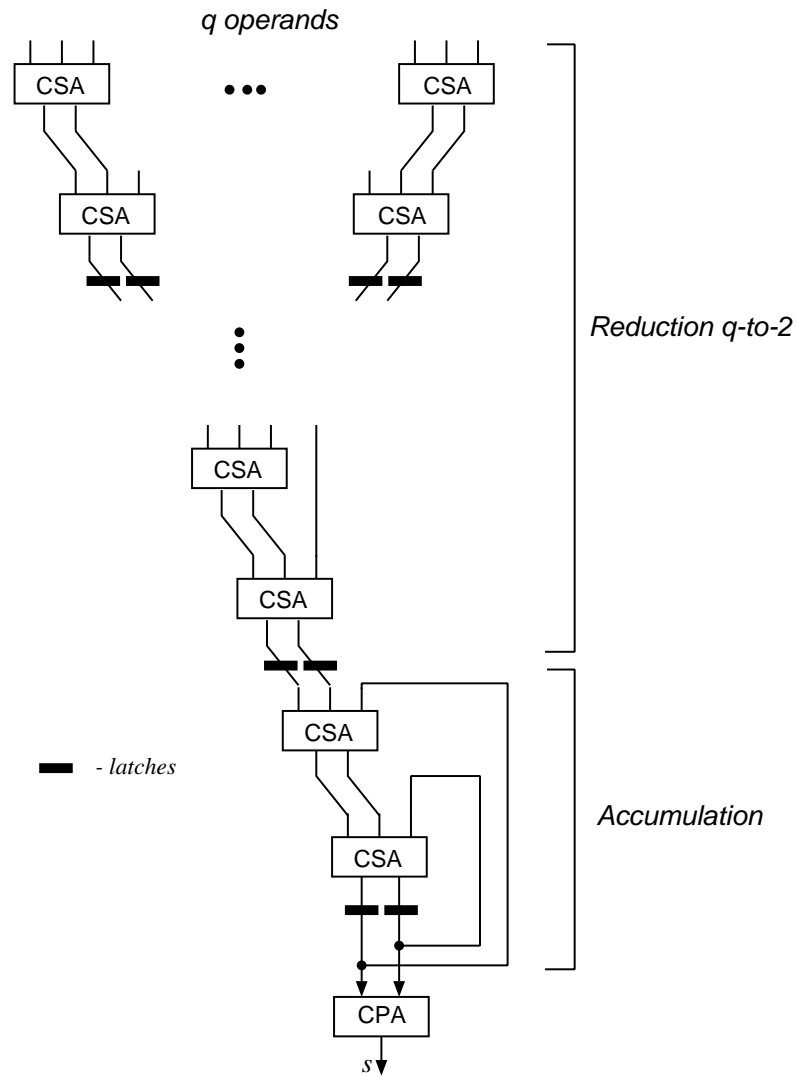


Figure 3.25: Scheme for summation of  $q$  operands per iteration.