DATA AND CONTROL SUBSYSTEMS

- COMPONENTS AND ORGANIZATION OF DATA SUBSYSTEM
- DESIGN OF DATA SUBSYSTEM
- IMPLEMENTATION OF CONTROL SUBSYSTEM AS A SEQUENTIAL MACHINE
- SPECIFICATION AND IMPLEMENTATION OF A MICROPROGRAMMED CONTROLLER

DATA SUBSYSTEM

i) STORAGE MODULES

ii) FUNCTIONAL MODULES (operators)

iii) DATAPATHS (switches and wires)

iv) CONTROL POINTS

v) CONDITION POINTS

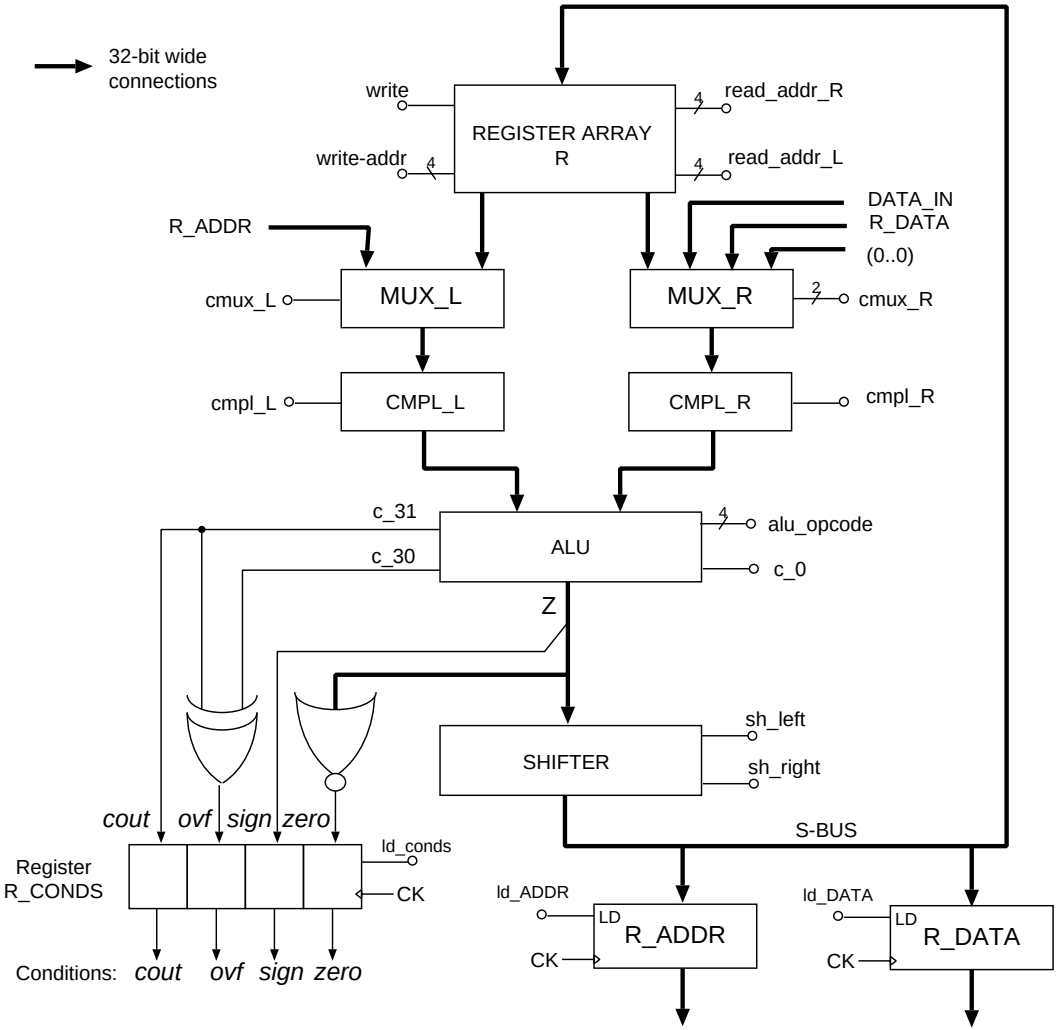

Figure 14.1: EXAMPLE OF A DATA SUBSYSTEM.

STORAGE MODULES

- INDIVIDUAL REGISTERS, with separate connections and controls;
- ARRAYS OF REGISTERS, sharing connections and controls;
  - REGISTER FILE
  - RANDOM-ACCESS MEMORY (RAM)
- COMBINATION OF INDIVIDUAL REGISTERS AND ARRAYS OF REGISTERS.

REGISTER FILE

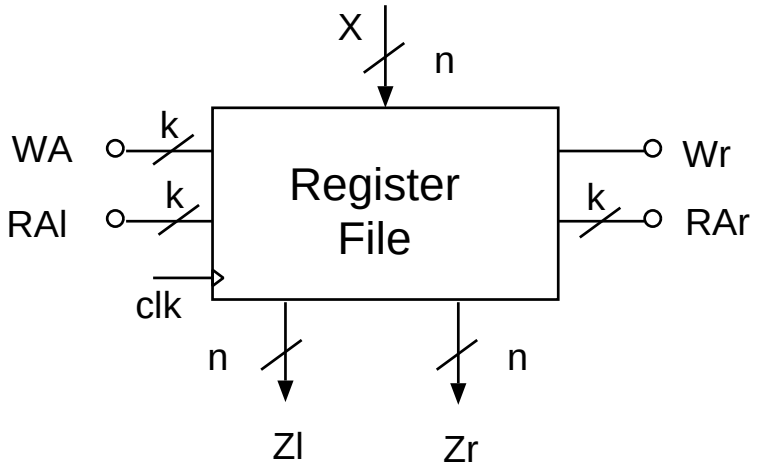

Figure 14.2: REGISTER FILE

```
USE WORK.BitDefs_pkg.ALL;
ENTITY reg_file IS
  GENERIC(n: NATURAL:=16;        -- word width
          p: NATURAL:= 8;        -- register file size
          k: NATURAL:= 3;        -- bits in address vector
         Td: TIME:=  5 ns);  -- read address to output
  PORT(X    : IN  UNSIGNED(n-1 DOWNTO 0);    -- input
       WA   : IN  UNSIGNED(k-1 DOWNTO 0);    -- write address
       RAl  : IN  UNSIGNED(k-1 DOWNTO 0);    -- read address (left)
       RAr  : IN  UNSIGNED(k-1 DOWNTO 0);    -- read address (right)
       Zl,Zr: OUT UNSIGNED(n-1 DOWNTO 0);    -- output (left,right)
       Wr   : IN  BIT;           -- write control signal
       clk  : IN  BIT);          -- clock
END reg_file;
```

REGISTER FILE DESCRIPTION

```
ARCHITECTURE behavioral OF reg_file IS
  SUBTYPE  WordT    IS UNSIGNED(n-1 DOWNTO 0);
  TYPE     StorageT IS ARRAY(0 TO p-1) OF WordT;
  SIGNAL   RF: StorageT;          -- reg. file contents
BEGIN
  PROCESS (clk)                   -- state transition
  BEGIN
    IF (clk'EVENT AND clk = '1') AND (Wr = '1') THEN
      RF(CONV_INTEGER(WA)) <= X;   -- write operation
    END IF;
  END PROCESS;

  PROCESS (RAl,RAr,RF)
  BEGIN                           -- output function
    Zl <= RF(CONV_INTEGER(RAl)) AFTER Td;
    Zr <= RF(CONV_INTEGER(RAr)) AFTER Td;
  END PROCESS; END behavioral;
```

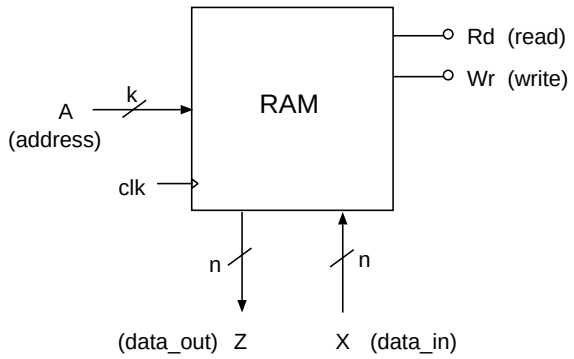


```
ENTITY ram IS
  GENERIC(n: NATURAL:= 16;     -- RAM word width
          p: NATURAL:=256;     -- RAM size
          k: NATURAL:=  8;     -- bits in address vector
         Td: TIME:= 40 ns);    -- RAM read delay
  PORT(X    : IN  UNSIGNED(n-1 DOWNTO 0);   -- input bit-vector
       A    : IN  UNSIGNED(k-1 DOWNTO 0);   -- address bit-vector
       Z    : OUT UNSIGNED(n-1 DOWNTO 0);   -- output bit-vector
       Rd,Wr: IN  BIT;          -- control signals
       Clk  : IN  BIT);         -- clock signal
END ram;
```

Figure 14.3: DESCRIPTION OF A RAM MODULE.

RAM DESCRIPTION

```
ARCHITECTURE behavioral OF ram IS
  SUBTYPE  WordT    IS UNSIGNED(n-1 DOWNTO 0);
  TYPE     StorageT IS ARRAY(0 TO p-1) OF WordT;
  SIGNAL   Memory: StorageT;            -- RAM state
BEGIN
  PROCESS (Clk)                         -- state transition
  BEGIN
    IF (Clk'EVENT AND Clk = '1') AND (Wr = '1') THEN
      Memory(CONV_INTEGER(A)) <= X;  -- write operation
    END IF;
  END PROCESS;

  PROCESS (Rd,Memory)                   -- output function
  BEGIN
    IF (Rd = '1') THEN                  -- read operation
        Z <= Memory(CONV_INTEGER(A)) AFTER Td;
    END IF;
  END PROCESS; END behavioral;
```

FUNCTIONAL MODULES

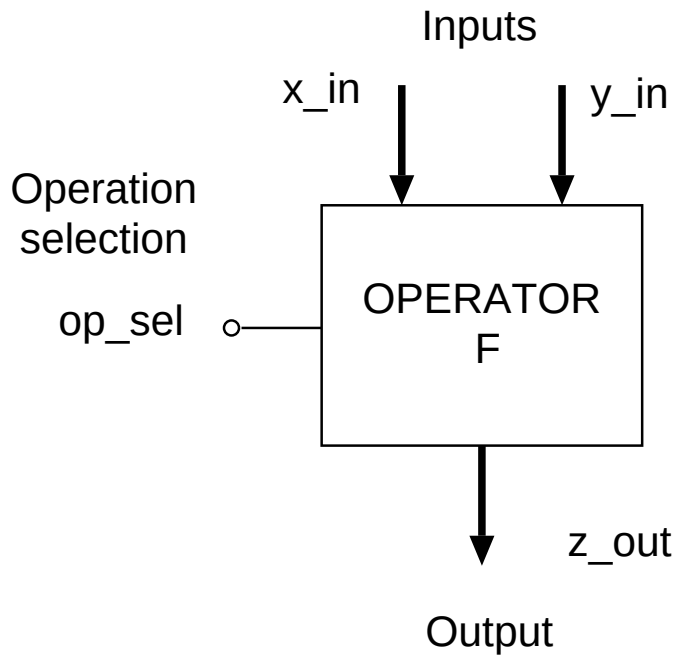

Figure 14.4: OPERATOR

```
CASE op_sel IS
  WHEN F1 => z_out <= x_in op1 y_in AFTER delay;
  WHEN F2 => z_out <= x_in op2 y_in AFTER delay;
  ....
END CASE;
```

DATAPATHS

- WIDTH OF DATAPATH
  PARALLEL OR SERIAL

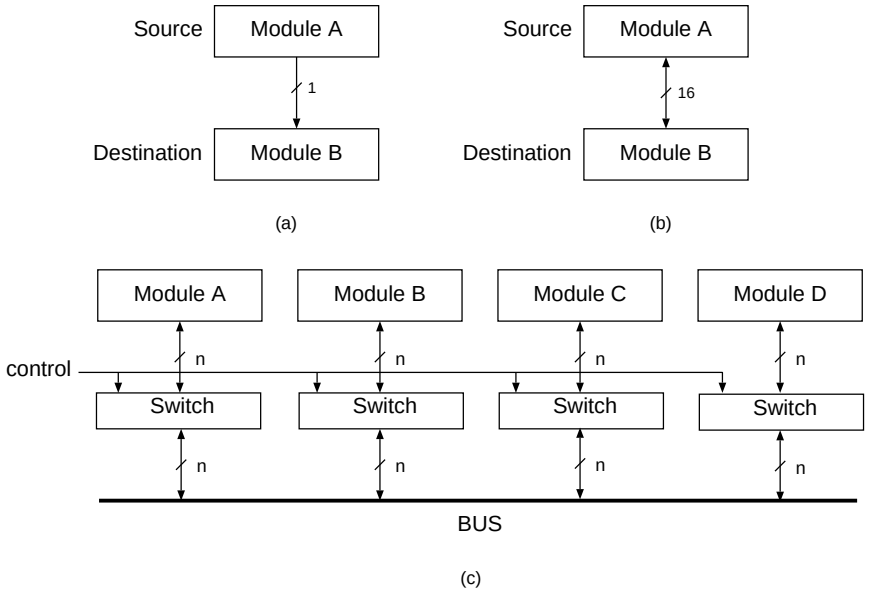

Figure 14.5: EXAMPLES OF DATAPATHS: a) unidirectional dedicated datapath (serial); b) bidirectional dedicated datapath (parallel); c) shared datapath (bus).

- UNIDIRECTIONAL OR BIDIRECTIONAL
- DEDICATED OR SHARED (bus)
- DIRECT OR INDIRECT

SWITCHES: VECTOR GATES AND SELECTORS

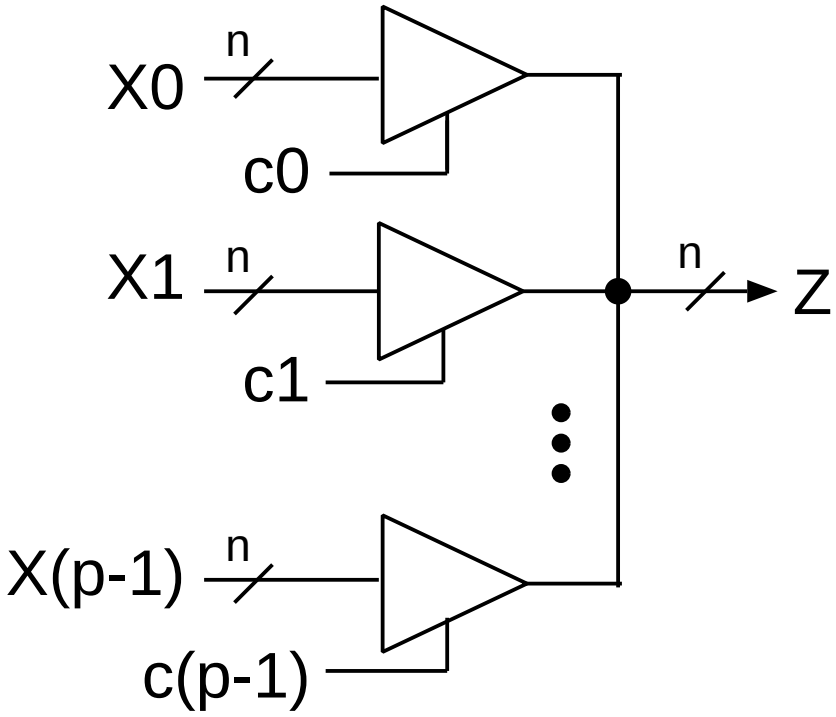

Figure 14.6: VECTOR GATE SWITCHES.

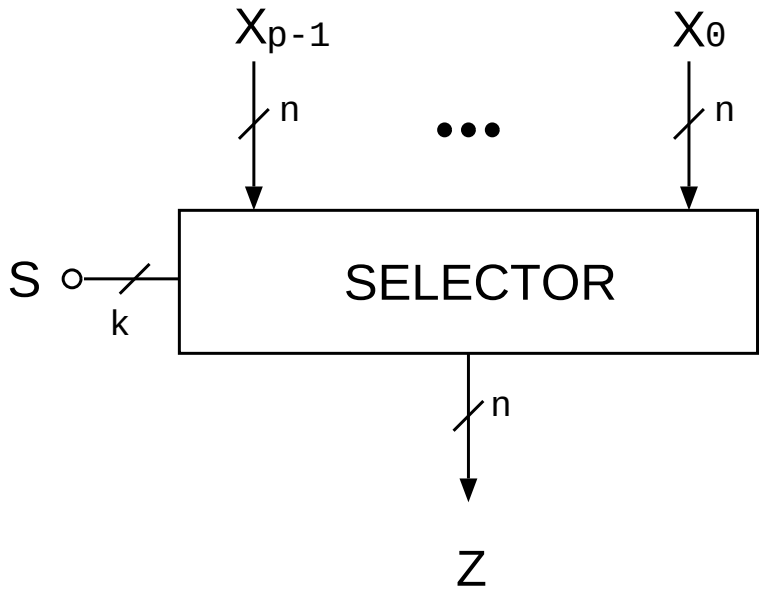

Figure 14.7: SELECTOR

```
PROCESS (Xp1,...,X0,S)
BEGIN
  CASE S IS
    WHEN "0..0" => Z <= X0;
    WHEN "0..1" => Z <= X1;
    ....
    WHEN "1..1" => Z <= Xp;
  END CASE; END PROCESS;
```

TYPES OF DATAPATHS

- COMPLETE INTERCONNECTION: CROSSBAR
- SINGLE BUS INTERCONNECTION

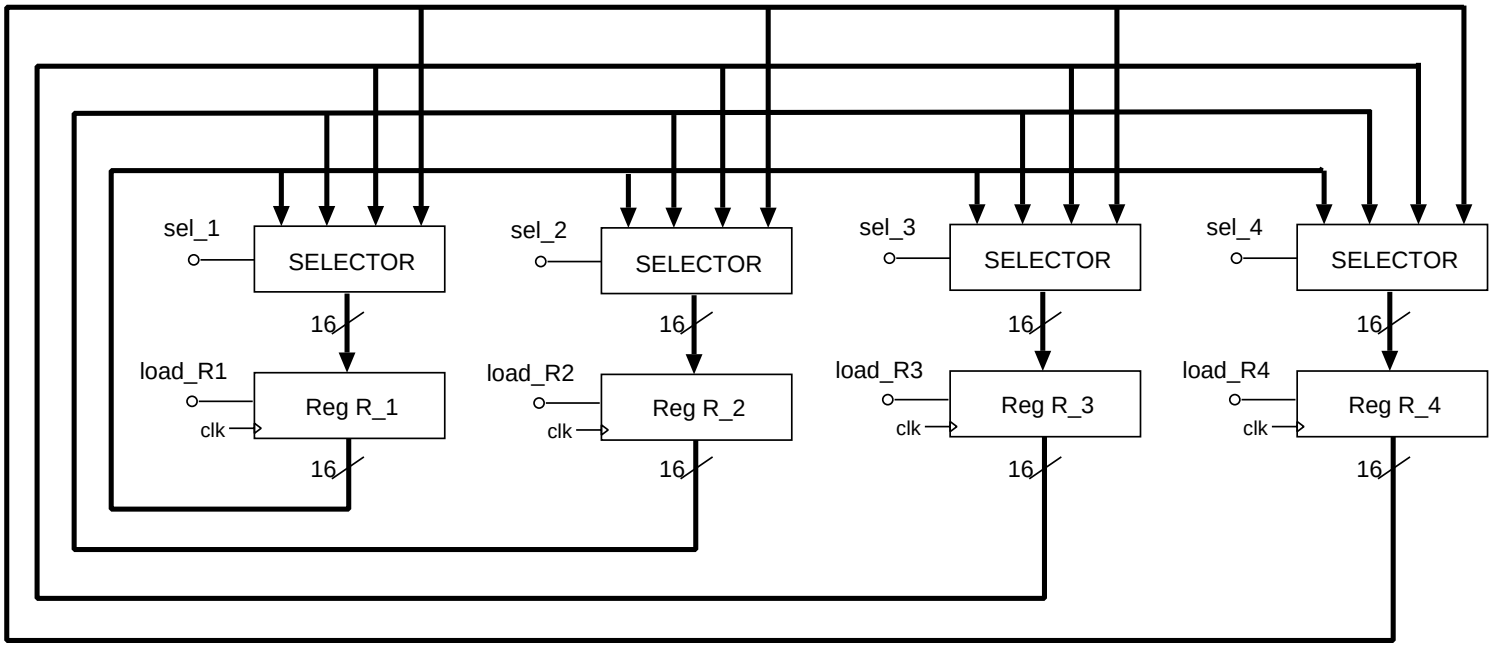

Figure 14.8: CROSSBAR INTERCONNECTION

CROSSBAR DESCRIPTION

```
  SIGNAL R_1,R_2,R_3,R_4: BIT_VECTOR(15 DOWNTO 0);
PROCESS (clk)
  VARIABLE Sel1,Sel2,Sel3,Sel4: BIT_VECTOR(15 DOWNTO 0);
BEGIN
  CASE sel_1 IS
    WHEN "00" => Sel1:= R1;
    WHEN "01" => Sel1:= R2;
    WHEN "10" => Sel1:= R3;
    WHEN "11" => Sel1:= R4;
  END CASE;
  ....
  CASE sel_4 IS
    WHEN "00" => Sel4:= R1;
    WHEN "01" => Sel4:= R2;
    WHEN "10" => Sel4:= R3;
    WHEN "11" => Sel4:= R4;
  END CASE;

  IF (clk='1') THEN
    IF (load_R1 = '1') THEN R_1 <= Sel1; ENDIF;
    IF (load_R2 = '1') THEN R_2 <= Sel1; ENDIF;
    IF (load_R3 = '1') THEN R_3 <= Sel1; ENDIF;
    IF (load_R4 = '1') THEN R_4 <= Sel4; ENDIF;
  END IF;
END PROCESS;
```

SINGLE BUS

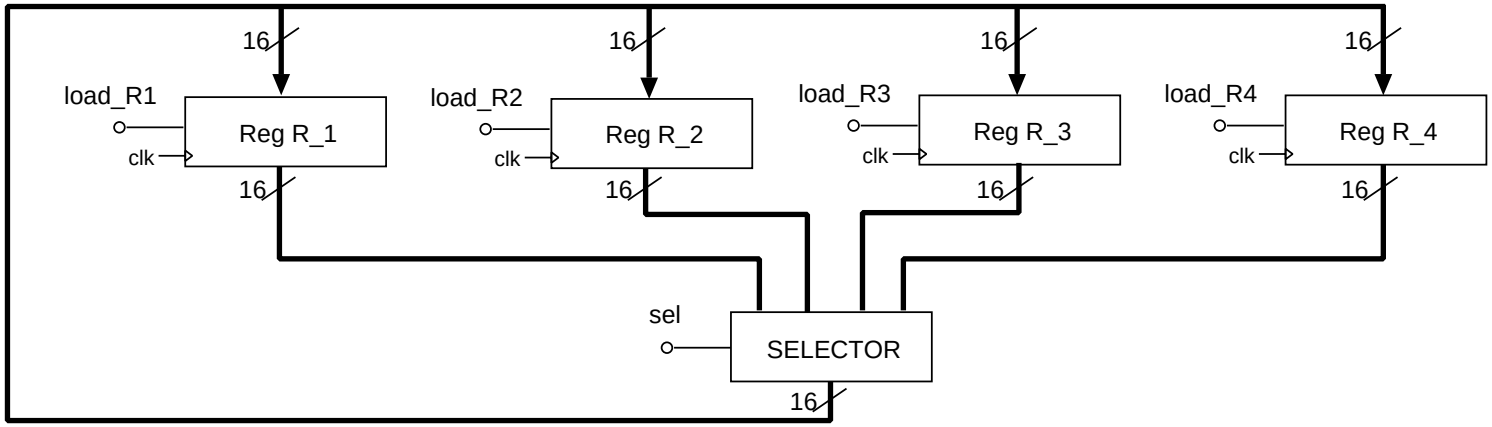

Figure 14.9: SINGLE BUS INTERCONNECTION NETWORK

SINGLE BUS DESCRIPTION

```
  SIGNAL R_1,R_2,R_3,R_4: BIT_VECTOR(15 DOWNTO 0);
PROCESS (clk)
  VARIABLE Sel_out: BIT_VECTOR(15 DOWNTO 0);
BEGIN
  CASE sel IS
    WHEN "00" => Sel_out:= R_1;
    WHEN "01" => Sel_out:= R_2;
    WHEN "10" => Sel_out:= R_3;
    WHEN "11" => Sel_out:= R_4;
  END CASE;

  IF (clk='1') THEN
    IF (load_R1 = '1') THEN R_1 <= Sel_out; ENDIF;
    IF (load_R2 = '1') THEN R_2 <= Sel_out; ENDIF;
    IF (load_R3 = '1') THEN R_3 <= Sel_out; ENDIF;
    IF (load_R4 = '1') THEN R_4 <= Sel_out; ENDIF;
  END IF; END PROCESS;
```

CONTROL SUBSYSTEM

- INPUTS: *control inputs* to the system and *conditions* from the data subsystem
- OUTPUTS: *control signals*
- ONE STATE PER STATEMENT IN REGISTER-TRANSFER SEQUENCE
- TRANSITION FUNCTION CORRESPONDS TO SEQUENCING
- OUTPUT FOR EACH STATE CORRESPONDS TO CONTROL SIGNALS

STATE ASSIGNMENT

- UNCONDITIONAL: only one successor to a state

- CONDITIONAL: several possible successors depending on the value of a condition

COUNTER-BASED CONTROL SUBSYSTEM

PS	Condition	NS	Count Enable	Parallel Load	Parallel Inputs	Active Control Signals
S0	`start = 0`	S0	0	1	000	`set_done`
S0	`start = 1`	S1	1	0	–	`set_done`
S1	–	S2	1	0	–	`reset_done, ld_arg, ld_rec, ld_eps`
S2	–	S3	1	0	–	`ld_w, selM`
S3	–	S4	1	0	–	`ld_y`
S4	`k = 1`	S2	0	1	010	`ld_rec, selR`
S4	`k = 0`	S0	0	1	000	`ld_rec, selR`

(a)

COUNTER-BASED CONTROL SUBSYSTEM

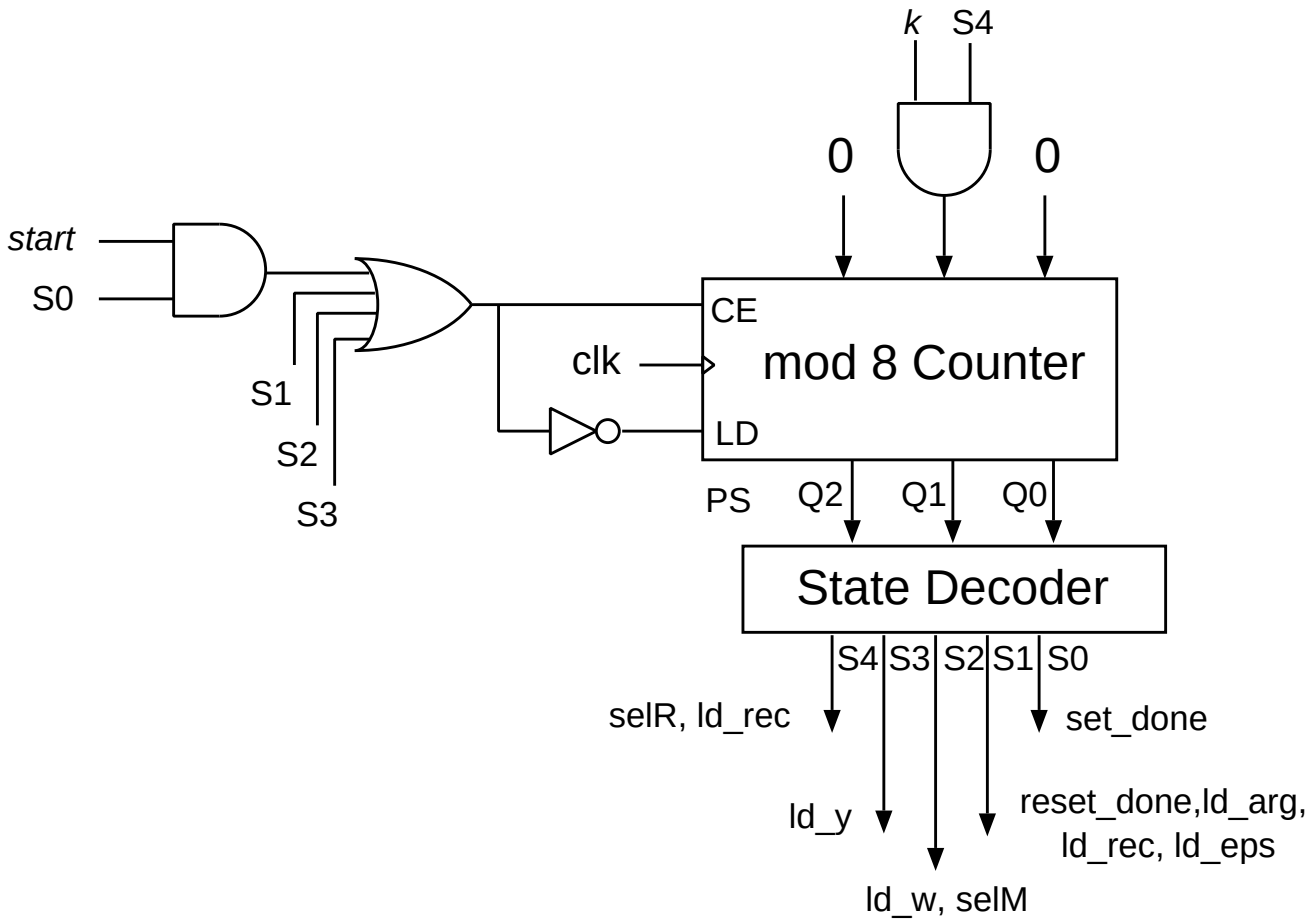

Figure 14.10: CONTROLLER NETWORK

ONE FF PER STATE APPROACH

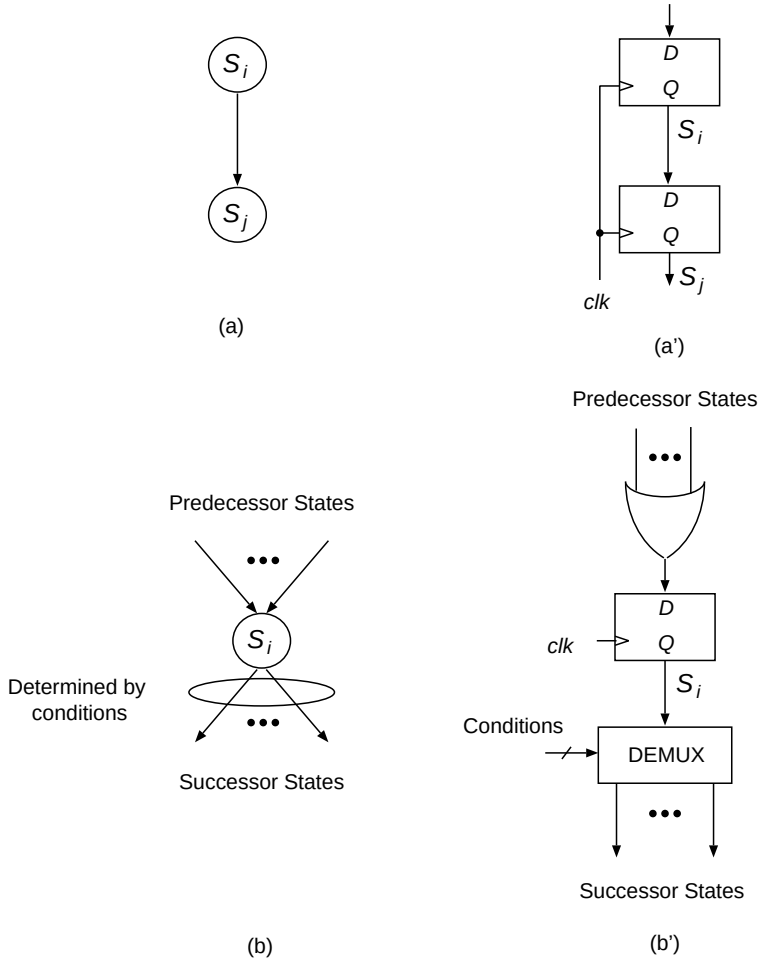

Figure 14.11: PRIMITIVES FOR THE "one flip-flop per state" APPROACH.

CONTROL SIGNALS

```
IF (sign = '0') THEN A <= B;
ELSE                 C <= D;
END IF;
```

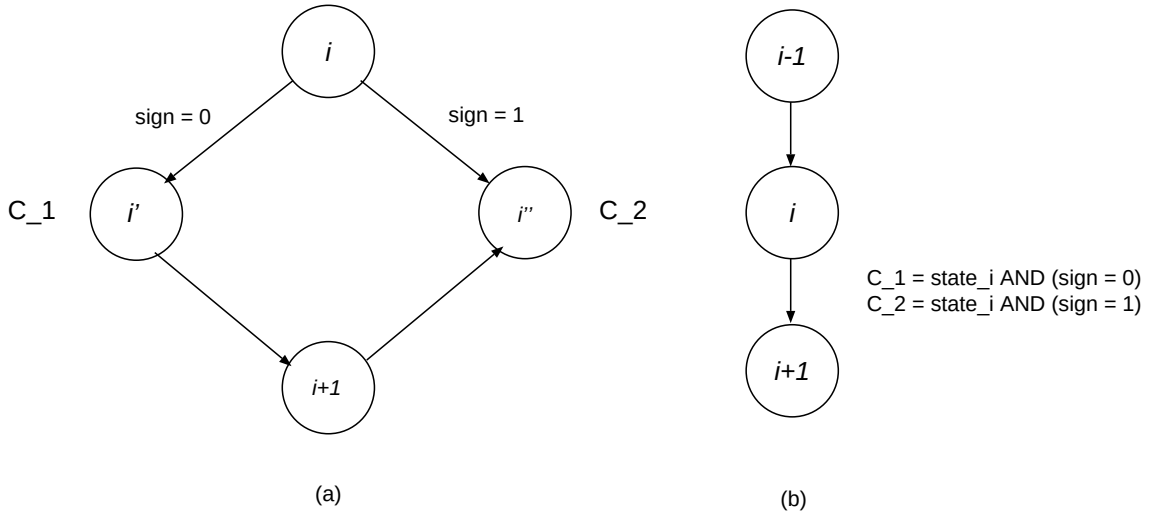

Figure 14.12: IMPLEMENTATION ALTERNATIVES FOR CONTROL SIGNALS: a) Moore-type implementation; b) Mealy-type implementation.

CLOCKED CELL FOR GENERATING CONTROL SIGNALS

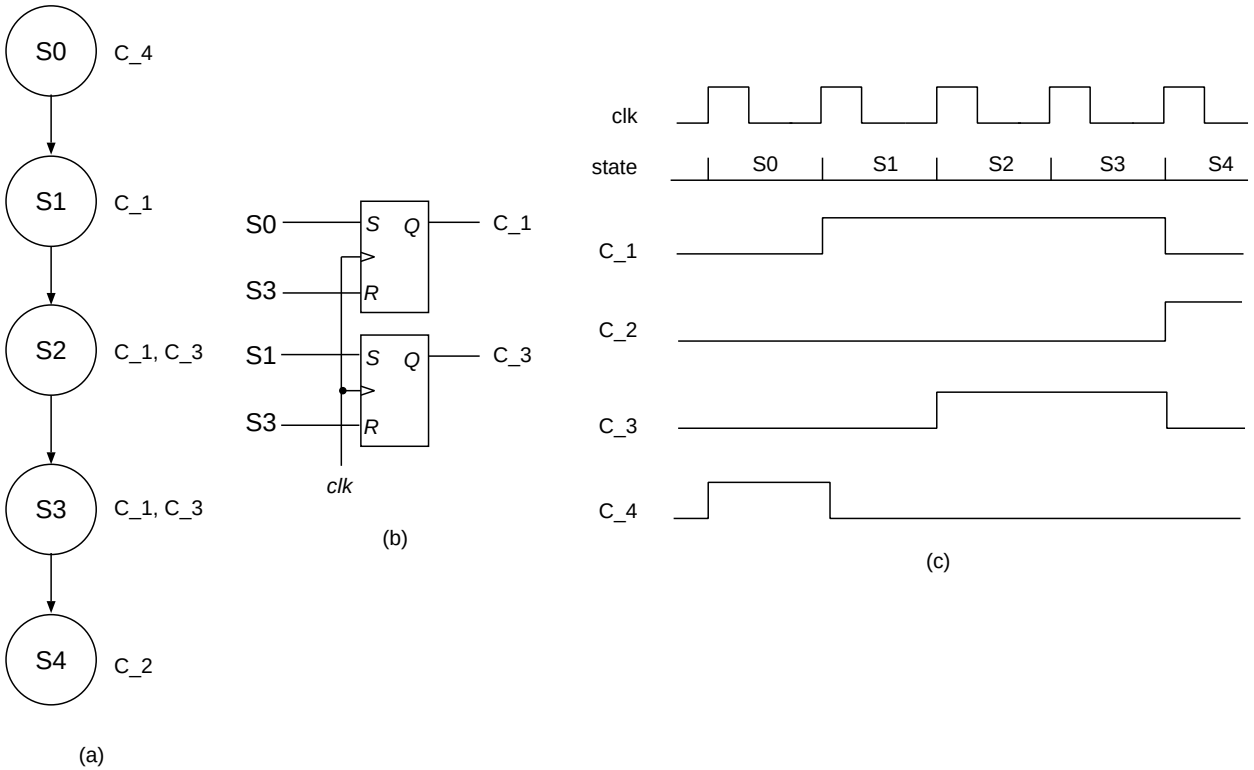

Figure 14.13: CLOCKED CELL: a) STATE DIAGRAM; b) IMPLEMENTATION OF SIGNALS c_1 and c_3; c) TIMING DIAGRAM.

DESIGN EXAMPLE: IncDec SYSTEM

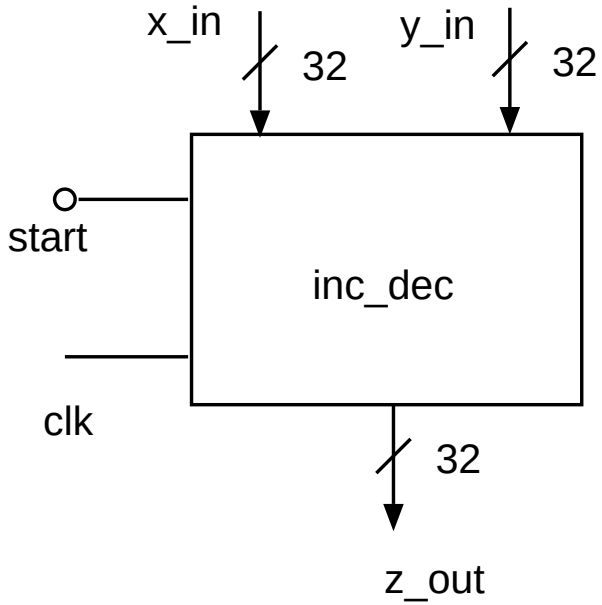


```
ENTITY incdec IS
  GENERIC (n: NATURAL := 16);
  PORT(strt     : IN  BIT;
       x_in,y_in: IN  SIGNED(n-1 DOWNTO 0);
       z_out    : OUT SIGNED(n-1 DOWNTO 0);
       clk      : IN  BIT);
END incdec;
```

```
ARCHITECTURE behavioral OF incdec IS
  TYPE    stateT IS (waiting, setup, abs_val, chk_iter,
                     iterate, multiply);
  SIGNAL state : stateT:= waiting;
  SIGNAL x,y   : SIGNED(n-1 DOWNTO 0);
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk'EVENT AND clk = '1') THEN
      CASE state IS
        WHEN waiting  => IF (strt='1') THEN state <= setup;
                         ELSE              state <= waiting;
                         END IF;
        WHEN setup    => x     <= x_in;
                         y     <= y_in;
                         state <= abs_val;
        WHEN abs_val  => IF (y(n-1) = '1') THEN y <= -y;
                         END IF;
                         state <= chk_iter;
        WHEN chk_iter => IF (x < y) THEN state <= iterate;
                         ELSE            state <= multiply;
                         END IF;
        WHEN iterate  => x     <= x+1;
                         y     <= y-1;
                         state <= chk_iter;
        WHEN multiply => z_out <= x(n-3 DOWNTO 0) & "00";
                         state <= waiting;
      END CASE;
    END IF; END PROCESS; END behavioral;
```

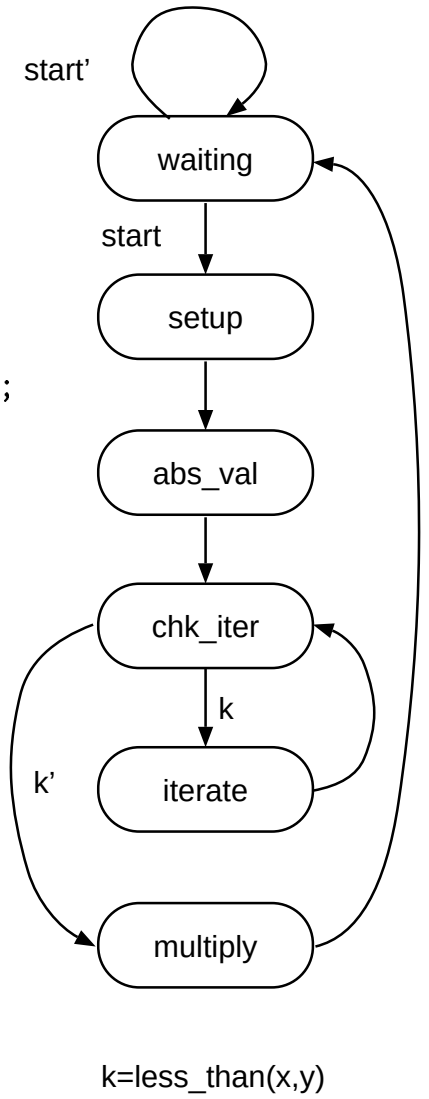

DATA SUBSYSTEM

- REGISTERS `x` and `y` to store x and y, respectively.
- OPERATORS `abs()`,`inc()`,`dec()`,`left_shift2()`, and < (less_than).
- DATAPATHS to connect the registers and operators.
  - from `x` to operators `left_shift2`, `inc`, and <.
  - from `y` to operators `dec`, `abs`, and <.
  - from `inc` and `x_in` to `x`.
  - from `dec`, `abs`, and `y_in` to `y`.
- CONTROL POINTS:

Operation	Control Points
`load register x`	`ldX`
`load register y`	`ldY`
`select input to x (1 bit)`	`selX`
`select input to y (2 bit)`	`selY`

- CONDITION

$$k = \begin{cases} 1 \ \textbf{if} \ \ x < y \\ 0 \ \textbf{otherwise} \end{cases}$$

DATA SUBSYSTEM BLOCK DIAGRAM

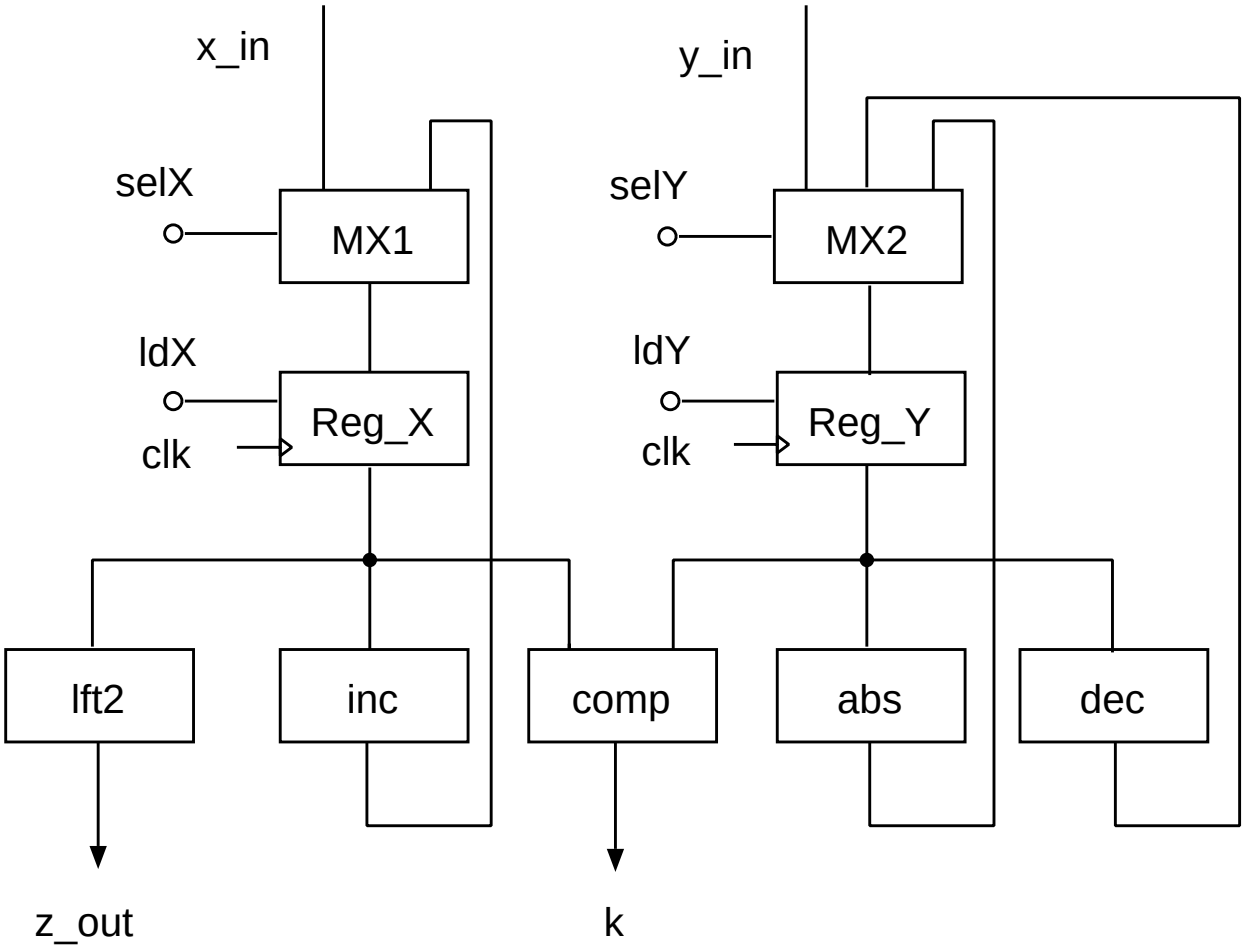

Figure 14.14: DATA SUBSYSTEM FOR DESIGN EXAMPLE

STRUCTURAL DESCRIPTION OF DATA SUBSYSTEM

```
ARCHITECTURE structural OF incdec_data IS
  SIGNAL inc_out,dec_out,abs_out,lft_out,mux1_out: BIT_VECTOR(n-1 DOWNTO 0);
  SIGNAL mux2_out,xreg_out,yreg_out,zero_32      : BIT_VECTOR(n-1 DOWNTO 0);
BEGIN
  x   : ENTITY reg         PORT MAP (mux1_out, ldX, xreg_out, clk);
  y   : ENTITY reg         PORT MAP (mux2_out, ldY, yreg_out, clk);
  inc : ENTITY incrementer PORT MAP (xreg_out, inc_out);
  dec : ENTITY decrementer PORT MAP (yreg_out, dec_out);
  ab  : ENTITY absolute    PORT MAP (yreg_out, abs_out);
  mx1 : ENTITY mux2        PORT MAP (x_in, inc_out, selX, mux1_out);
  mx2 : ENTITY mux4        PORT MAP (y_in, dec_out, abs_out, zero_32,
                                     selY, mul2_out);
  lft2: ENTITY lft_shift2  PORT MAP (xreg_out, lft_out);
  comp: ENTITY less_than   PORT MAP (xreg_out, yreg_out, k);
END structural;
```

BEHAVIORAL DESCRIPTION OF DATA SUBSYSTEM

```
USE WORK.BitDefs_pkg.ALL;
ENTITY data_subsystem IS
  GENERIC(n : NATURAL:= 16);
  PORT(x_in, y_in : IN  BIT_VECTOR(n-1 DOWNTO 0); -- data inputs
       ldX,ldY    : IN  BIT;                      -- control signals
       selX       : IN  BIT;
       selY       : IN  BIT_VECTOR(1 DOWNTO 0);
       k          : OUT BIT;                      -- conditions
       z_out      : OUT BIT_VECTOR(n-1 DOWNTO 0); -- data outputs
       clk        : IN  BIT);
END data_subsystem;
```

```
ARCHITECTURE behavioral OF data_subsystem IS
  SIGNAL x,y,z : BIT_VECTOR(n-1 DOWNTO 0);
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk = '1') THEN
      IF (ldX = '1') AND (selX = '0')  THEN x <= x_in;   END IF;
      IF (ldX = '1') AND (selX = '1')  THEN x <= inc(x); END IF;
      IF (ldY = '1') AND (selY = "00") THEN y <= y_in;   END IF;
      IF (ldY = '1') AND (selY = "01") THEN y <= dec(y); END IF;
      IF (ldY = '1') AND (selY = "10") THEN y <= ABS(y); END IF;
      IF (x < y) THEN k <= '1';
      ELSE            k <= '0';
      END IF;
      z_out <= shift_left(x,2);
    END IF;
  END PROCESS;
END behavioral;
```

STRUCTURAL DESCRIPTION OF IncDec SYSTEM

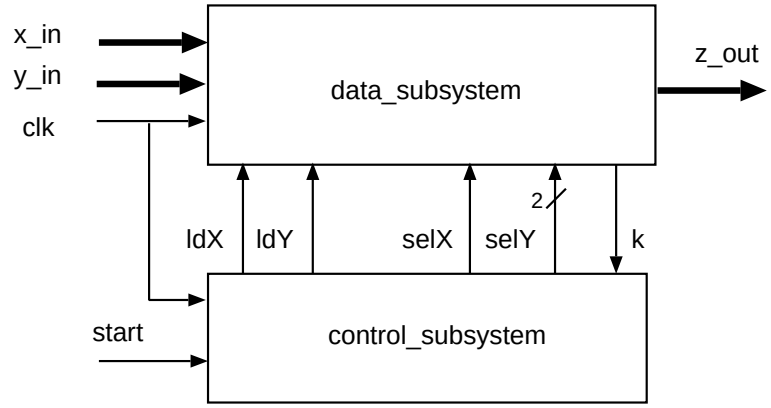

Figure 14.17: THE SYSTEM

```
ARCHITECTURE structural OF incdec IS
  SIGNAL selY          : BITV_VECTOR(1 DOWNTO 0);
  SIGNAL ldX,ldY,selX  : BIT;
  SIGNAL k             : BIT;
BEGIN
  datasub: ENTITY incdec_data
           PORT MAP (x_in,y_in,ldX,ldY,selX,selY,k,z_out,clk);
  ctrlsub: ENTITY incdec_ctrl
           PORT MAP (start,k,ldX,ldY,selX,selY,clk);
END structural;
```

ABSOLUTE VALUE MODULE

```
ENTITY absolute IS
  PORT (x_in : IN  SIGNED;
        z_out: OUT SIGNED);
END absolute;

ARCHITECTURE behavioral OF absolute IS
BEGIN
  PROCESS (x_in)
  BEGIN
    IF x_in(x_in'LEFT) = '1' THEN z_out <= -x_in;
    ELSE z_out <= x_in;
    END IF;
  END PROCESS;
END behavioral;
```

CONTROL SUBSYSTEM

State	ldX	ldY	selX	selY	Next state
waiting	0	0	-	–	setup, waiting
setup	1	1	0	00	abs_val
abs_val	0	1	-	01	chk_iter
chk_iter	0	0	-	–	iterate, multiply
iterate	1	1	1	10	chk_iter
multiply	0	0	-	–	waiting

BEHAVIORAL DESCRIPTION OF IncDec CONTROL SUBSYSTEM

```
ENTITY incdec_ctrl IS
  PORT(strt,k, clk  : IN  BIT;     -- control input, condition, clock
       ldX, ldY: OUT BIT;     -- control signals
       selX    : OUT BIT;
       selY    : OUT BIT_VECTOR(1 DOWNTO 0));
END incdec_ctrl ;

ARCHITECTURE behavioral OF incdec_ctrl IS
  TYPE stateT IS (waiting,setup,abs_val,chk_iter,iterate,multiply);
  SIGNAL state : stateT:= waiting;
BEGIN
  PROCESS (clk)                      -- transition function
  BEGIN
    IF (clk'EVENT AND clk = '1') THEN
      CASE state IS
        WHEN waiting  => IF (strt = '1') THEN state <= setup; END IF;
        WHEN setup    => state <= abs_val ;
        WHEN abs_val  => state <= chk_iter;
        WHEN chk_iter => IF (k = '1') THEN state <= iterate ;
                         ELSE              state <= multiply;
                         END IF;
        WHEN iterate  => state <= chk_iter;
        WHEN multiply => state <= waiting ;
      END CASE;
    END IF; END PROCESS;
```

IncDec CONTROL SUBSYSTEM (cont.)

```
  PROCESS (state)                          -- output function
    VARIABLE ctrls : BIT_VECTOR(4 DOWNTO 0);
  BEGIN
    CASE state IS
      WHEN waiting  => ctrls(4 downto 3):= "00"   ;
      WHEN setup    => ctrls             := "11000";
      WHEN abs_val  => ctrls(4 downto 3):= "01"   ;
                       ctrls(1 downto 0):= "01"   ;
      WHEN chk_iter => ctrls(4 downto 3):= "00"   ;
      WHEN iterate  => ctrls             := "11110";
      WHEN multiply => ctrls(4 downto 3):= "00"   ;
    END CASE;
    ldX  <= ctrls(4); ldY  <= ctrls(3);
    selX <= ctrls(2); selY <= ctrls(1 DOWNTO 0);
  END PROCESS;
END behavioral;
```

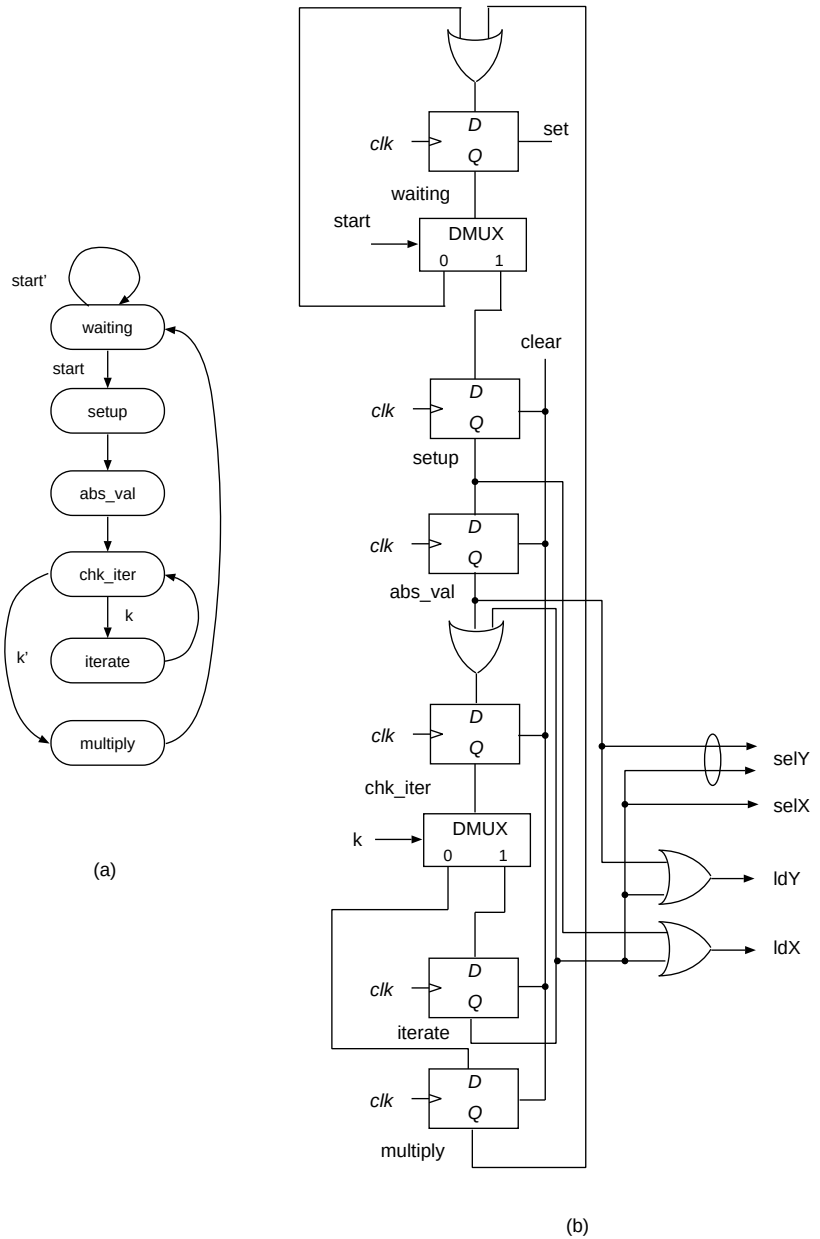

Figure 14.20: IMPLEMENTATION OF CONTROL SUBSYSTEM.

MICROPROGRAMMED CONTROLLER

- GENERALIZATION OF ROM-BASED CONTROLLER
- STATE-TRANSITION AND OUTPUT FUNCTIONS IMPLEMENTED USING TABLE LOOK-UP
- **microinstruction** – A WORD IN MEMORY SPECIFYING

  1. THE VALUES OF THE CONTROL SIGNALS;
  2. THE SEQUENCING INFORMATION THAT DETERMINES WHICH MICROINSTRUCTION IS EXECUTED NEXT

- **microprogram** - A SEQUENCE OF MICROINSTRUCTIONS

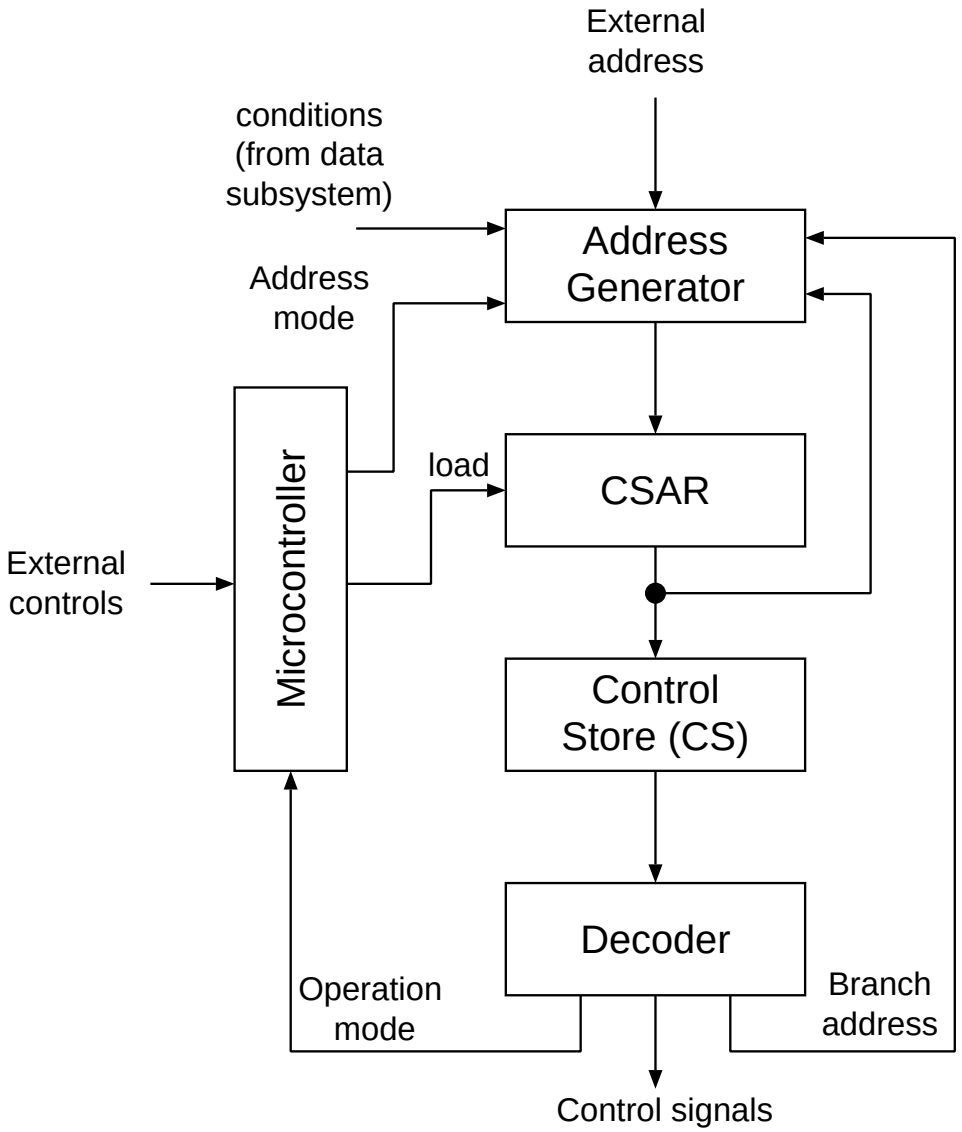

Figure 14.21: A MICROPROGRAMMED CONTROLLER.

STRUCTURE (cont.)

- CONTROL STORE CS - CONTAINS THE MICROPROGRAM
  - Uses ROM, PROM, or RAM
  - ROM-based implementation is permanent; PROM or RAM-based implementations allow modifying the microprogram
  - A RAM-based implementation: *writable control store*
  - Systems with writable control store called *microprogrammable*

- CONTROL-STORE ADDRESS REGISTER (CSAR)

- CS ADDRESS GENERATOR (CSAGEN)

- DECODER - GENERATES CONTROL SIGNALS

- MICROCONTROLLER The "control unit" of the microprogrammed controller

ADVANTAGES AND DISADVANTAGES

+ The structure of the controller is modular, regular and independent of the particular computation implemented by the system
+ The implementation of the controller for a complex computation consists of writing the corresponding microprogram
+ Simpler to write a microprogram than implement a fixed controller
+ Easily modified
- Might be slower

MICROINSTRUCTION FORMAT

- DIVIDED INTO FIELDS
  - A CONTROL FIELD:
    contains the values of control signals
  - A SEQUENCING FIELD:
    specifies the address of the next microinstruction

CONTROL FIELD

- HORIZONTAL (unpacked, decoded)
- VERTICAL (packed, encoded)

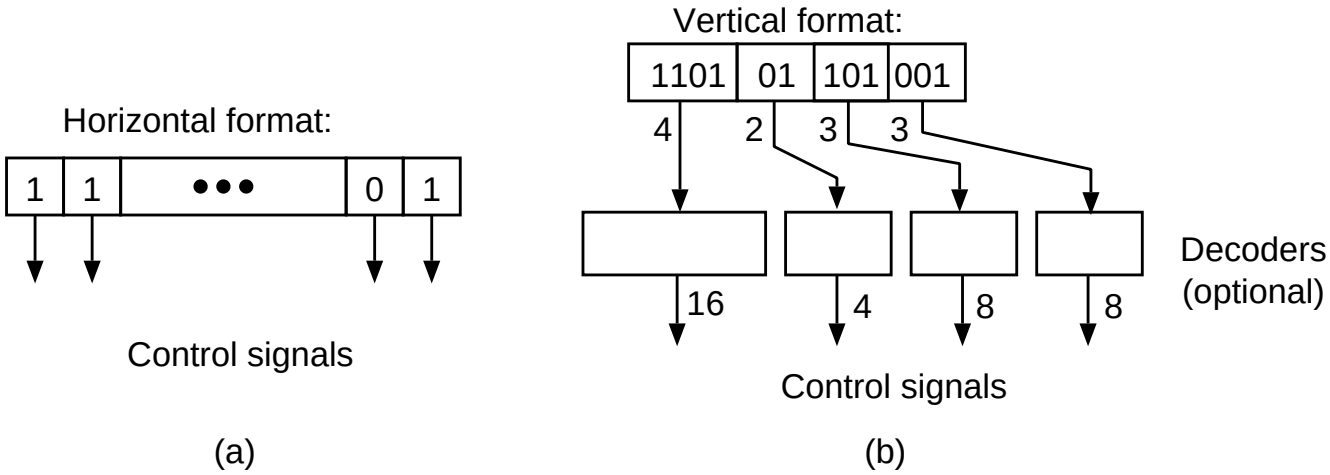

Figure 14.22: FORMATS OF THE CONTROL FIELD.

VERTICAL FORMAT (cont.)

- A DECODER PER SUBFIELD
- ALLOCATION TO SUBFIELDS
- ASSIGNED TO THE SAME SUBFIELD ONLY IF
  - the operations they control are not required at the same time in the microprogram; or
  - the data subsystem does not allow the simultaneous use of such control signals.

EXAMPLE OF CONTROL FIELDS

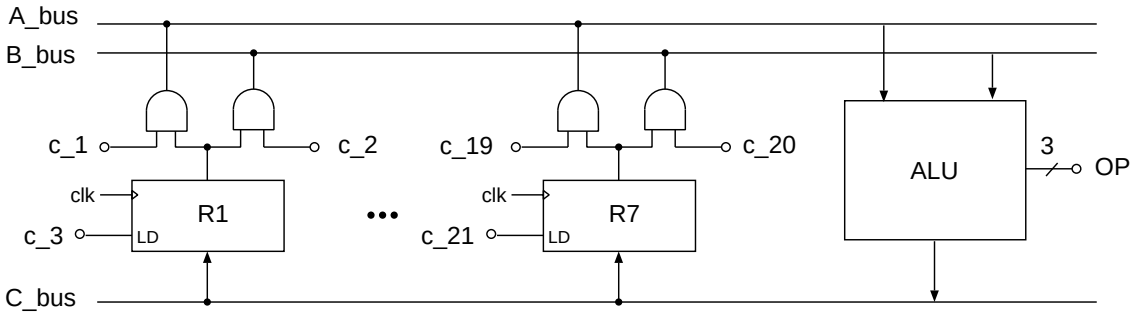

(a)

Horizontal format (24 bits):

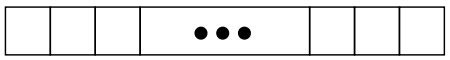

Vertical format (12 bits):

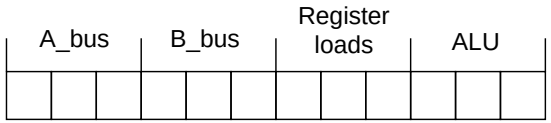

(b)

Register transfer R_1 <= R_2 XOR R_6

(XOR code = 110)

Microinstructions: Horizontal format: c_3, c_4, c_17, c_22, c_23 = 1
other c_i = 0

Vertical format: 010 110 001 110

(c)

Figure 14.23: VERTICAL AND HORIZONTAL ENCODING OF CONTROL FIELD for Example 14.1

MICROINSTRUCTION SEQUENCING

- EXPLICIT SEQUENCING
- IMPLICIT SEQUENCING

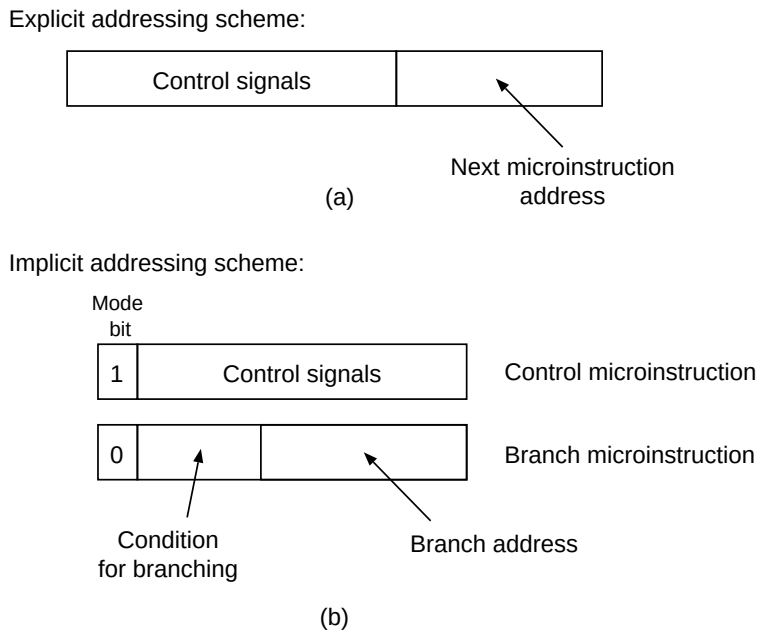

Figure 14.24: MICROINSTRUCTION ADDRESSING SCHEMES: a) explicit sequencing; b) implicit sequencing.

IMPLICIT SEQUENCING

TWO TYPES OF CONTROL STORE ADDRESS CALCULATIONS REQUIRED:

- INCREMENT CSAR if not a branch, or if the condition not satisfied
- LOAD CSAR with the branch address if the current microinstruction is a branch and the condition satisfied.

MICROINSTRUCTION TIMING

1. LOADING THE ADDRESS of the next microinstruction into CSAR.
2. FETCHING (reading) the corresponding microinstruction
3. DECODING the fields.
4. EXECUTING the microoperations.
5. CALCULATING THE ADDRESS of the next microinstruction; this calculation can be overlapped with the execution part of the cycle.

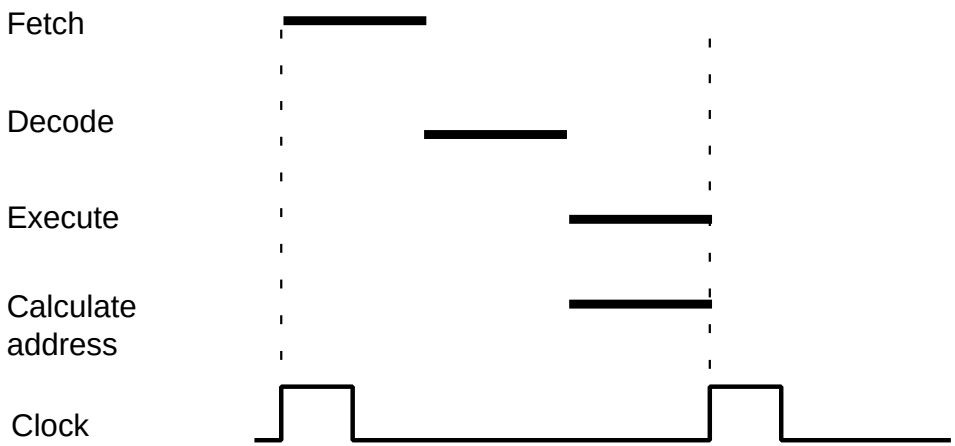

Figure 14.25: MICROINSTRUCTION CYCLE.

EXAMPLE OF MICROPROGRAMMABLE SYSTEM

DATA SUBSYSTEM

- REGISTER FILE with 8 registers of 8 bits each. Two read and one write operations can be performed simultaneously.
- ALU: ADD, SUB, XOR and INC; conditions ZERO, NEG and CY.
- 8-bit INPUT REGISTER.
- 8-bit OUTPUT REGISTER.

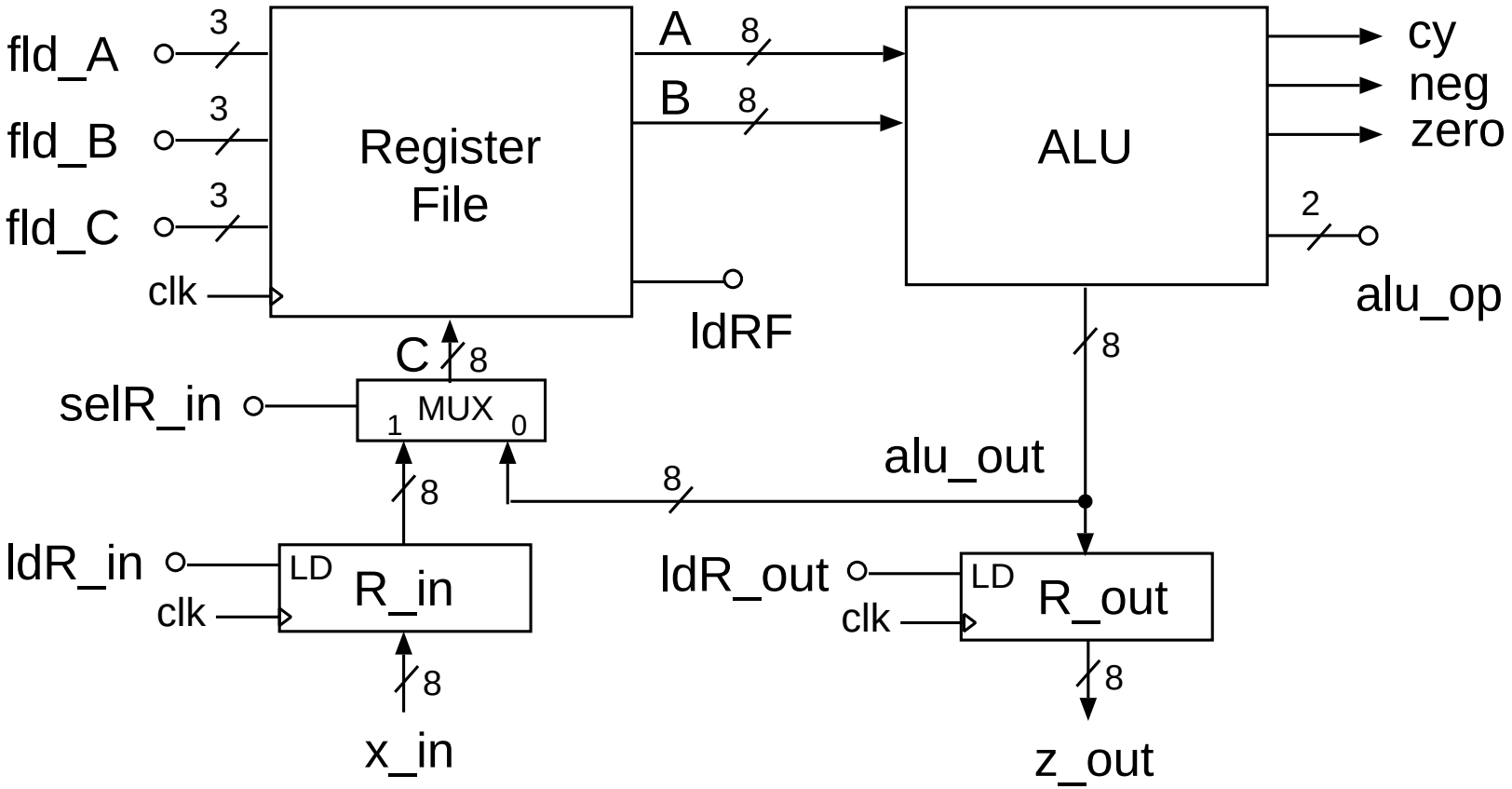

Figure 14.26: DATA SUBSYSTEM.

EXAMPLE: CONTROL INPUTS TO DATA SUBSYSTEM

Control signal	Description
`fld_A`	address for read port A
`fld_B`	address for read port B
`fld_C`	address for write
`ldRF`	load register file (write)
`alu_op`	operation performed in ALU
	00 - ADD
	01 - SUB
	10 - XOR
	11 - INC
`ldR_in`	load R_in
`ldR_out`	load R_out
`selR_in`	select R_in
	0 - select ALU output
	1 - select R_in

EXAMPLE: CONDITIONS

Condition	Signal	Description
`alu_out = 0`	`zero`	result is zero
`alu_out < 0`	`neg`	result is negative
`carry`	`cy`	result generated carry

BEHAVIORAL SPECIFICATION OF DATA SUBSYSTEM

```
ENTITY microdata IS
  PORT(x_in                       : IN  SIGNED(7 DOWNTO 0);
       fld_A, fld_B, fld_C        : IN  UNSIGNED(2 DOWNTO 0);
       alu_op                     : IN  UNSIGNED(1 DOWNTO 0);
       ldR_in, ldR_out, selR_in   : IN  STD_LOGIC ;
       ldRF                       : IN  STD_LOGIC ;
       zero, neg, cy              : OUT STD_LOGIC ;
       z_out                      : OUT SIGNED(7 DOWNTO 0);
       clk                        : IN  STD_LOGIC);
END microdata;

ARCHITECTURE behavioral OF microdata IS
  TYPE   reg_fileT IS ARRAY(0 TO 7) OF SIGNED(7 DOWNTO 0);
  SIGNAL RF: reg_fileT ;
  SIGNAL R_in: SIGNED(7 DOWNTO 0);
BEGIN
  PROCESS(clk)
    VARIABLE A,B,C  : SIGNED(7 DOWNTO 0);
    VARIABLE alu_out: SIGNED(7 DOWNTO 0);
    VARIABLE zzero,nneg,ccy: STD_LOGIC;
```

EXAMPLE: BEHAVIORAL DESCRIPTION (cont.)

```
  BEGIN                                  -- combinational modules
    A:= RF(CONV_INTEGER(fld_A));                -- ALU
    B:= RF(CONV_INTEGER(fld_B));
    CASE alu_op IS
      WHEN "00" => alu(zzero,nneg,ccy,alu_out,A,B,op_add);
      WHEN "01" => alu(zzero,nneg,ccy,alu_out,A,B,op_sub);
      WHEN "10" => alu(zzero,nneg,ccy,alu_out,A,B,op_xor);
      WHEN "11" => alu(zzero,nneg,ccy,alu_out,A,B,op_inc);
      WHEN OTHERS => NULL;
    END CASE;
    zero <= zzero;  neg <= nneg;  cy <= ccy;
    IF (selR_in = '0') THEN C:= alu_out;    -- multiplexer
    ELSE                    C:= R_in ;
    END IF;
    IF (clk'EVENT AND clk = '1') THEN
      IF (ldR_in  = '1') THEN R_in <= x_in   ; END IF;
      IF (ldR_out = '1') THEN z_out<= alu_out; END IF;
      IF (ldRF    = '1') THEN RF(CONV_INTEGER(fld_C))<= C; END IF;
    END IF;
  END PROCESS;
END behavioral;
```

CONTROL SUBSYSTEM - MICROPROGRAMMED

```
Inputs:   start
          zero, neg, cy
Outputs:  fld_A, fld_B, fld_C
          alu_op
          ldR_in, ldR_out
          selR_in, ldRF, done
```

- IMPLICIT SEQUENCING

- TWO MICROINSTRUCTION FORMATS: operations and branch

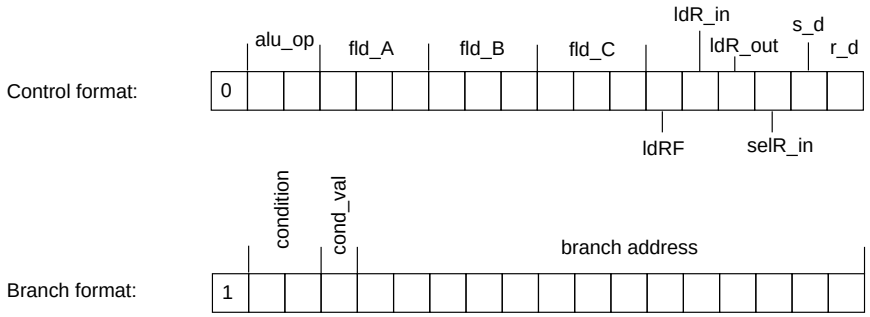

Figure 14.28: MICROINSTRUCTION FORMATS.

ENCODING OF FIELDS

- Field `cond` encoding

Condition	Code
start	00
zero	01
neg	10
cy	11

- Field `cond_val` specifies the value of the condition for the branch to execute

BEHAVIORAL DESCRIPTION OF CONTROL SUBSYSTEM

```
  ENTITY microctrl IS
  GENERIC(cssize: NATURAL:=16);
  PORT(start,zero,neg,cy: IN  STD_LOGIC       ;
       fld_A,fld_B,fld_C: OUT UNSIGNED(2 DOWNTO 0);
       alu_op           : OUT UNSIGNED(1 DOWNTO 0);
       ldR_in,ldR_out   : OUT STD_LOGIC       ;
       selR_in,ldRF,done: OUT STD_LOGIC       ;
       clk              : IN  STD_LOGIC      );
END microctrl;

ARCHITECTURE behav_microprogr OF microctrl IS
  SIGNAL csar     : NATURAL    ;              -- state
  SIGNAL uinstr   : UNSIGNED(17 DOWNTO 0); -- microinstruction
  ALIAS  mode     : STD_LOGIC IS uinstr(17);       -- branch mode
  ALIAS  condition: UNSIGNED(1 DOWNTO 0) IS uinstr(16 DOWNTO 15);
  ALIAS  cond_val : STD_LOGIC IS uinstr(14);       -- condition value
  PROCESS(clk)
    VARIABLE index: UNSIGNED(13 DOWNTO 0);
```

BEHAVIORAL DESCRIPTION OF CONTROL SUBSYSTEM: Transition Function

```
BEGIN
  IF (clk'EVENT AND clk = '1') THEN
    IF (mode = '0') THEN csar <= csar + 1;
    ELSE
      CASE condition IS
        WHEN "00" => IF (start = cond_val) THEN
                          index:= uinstr(13 DOWNTO 0);
                          csar <= CONV_INTEGER(index);
                     ELSE csar <= csar + 1;
                     END IF;
        WHEN "01" => IF (zero = cond_val)  THEN
                          index:= uinstr(13 DOWNTO 0);
                          csar <= CONV_INTEGER(index);
                     ELSE csar <= csar + 1;
                     END IF;
```

TRANSITION FUNCTION (cont.)

```
        WHEN "10" => IF (neg = cond_val)   THEN
                             index:= uinstr(13 DOWNTO 0);
                             csar <= CONV_INTEGER(index);
                           ELSE csar <= csar + 1;
                           END IF;
        WHEN "11" => IF (cy = cond_val)    THEN
                             index:= uinstr(13 DOWNTO 0);
                             csar <= CONV_INTEGER(index);
                           ELSE csar <= csar + 1;
                           END IF;
        WHEN OTHERS => NULL;
      END CASE;
    END IF;
  END IF;
END PROCESS;
```

BEHAVIORAL DESCRIPTION: OUTPUT FUNCTION

```
PROCESS (csar)                          -- output function
  TYPE     csarray IS ARRAY(0 to cssize-1)
                                          OF UNSIGNED(17 DOWNTO 0);
  VARIABLE cs: csarray
  -- here the microprogram as initial contents of ARRAY cs
                        := (0 => "0010000000000100010",
                            1 => "1000000000000000001",
                            2 => "0110000000111100001",
                            3 => "0000000000101001000",
                            4 => "0000000001111000000",
                            5 => "0000100100101000000",
                            6 => "1110000000000001000",
                            7 => "0111110001111000000",
                            8 => "0000110110111000000",
                            9 => "1110000000000000101",
                           10 => "0001110001111010000",
                           11 => "1110000000000000000");
-- Continuation --
```

BEHAVIORAL DESCRIPTION: Check Mode

```
BEGIN
    uinstr <= cs(csar);
    CASE uinstr(17) IS              -- check mode
      WHEN '0' => alu_op <= uinstr(16 DOWNTO 15);
                  fld_A  <= uinstr(14 DOWNTO 12);
                  fld_B  <= uinstr(11 DOWNTO  9);
                  fld_C  <= uinstr( 8 DOWNTO  6);
                  ldRF   <= uinstr(5);
                  ldR_in <= uinstr(4);
                  ldR_out<= uinstr(3);
                  selR_in<= uinstr(2);
                  IF (uinstr(1) = '1') THEN done <= '1'; END IF;
                  IF (uinstr(0) = '1') THEN done <= '0'; END IF;
      WHEN '1' => ldRF    <= '0'; ldR_out <= '0'; ldR_in <= '0';
      WHEN OTHERS => NULL;
    END CASE; END PROCESS; END behav_microprogr;
```

STRUCTURAL DESCRIPTION

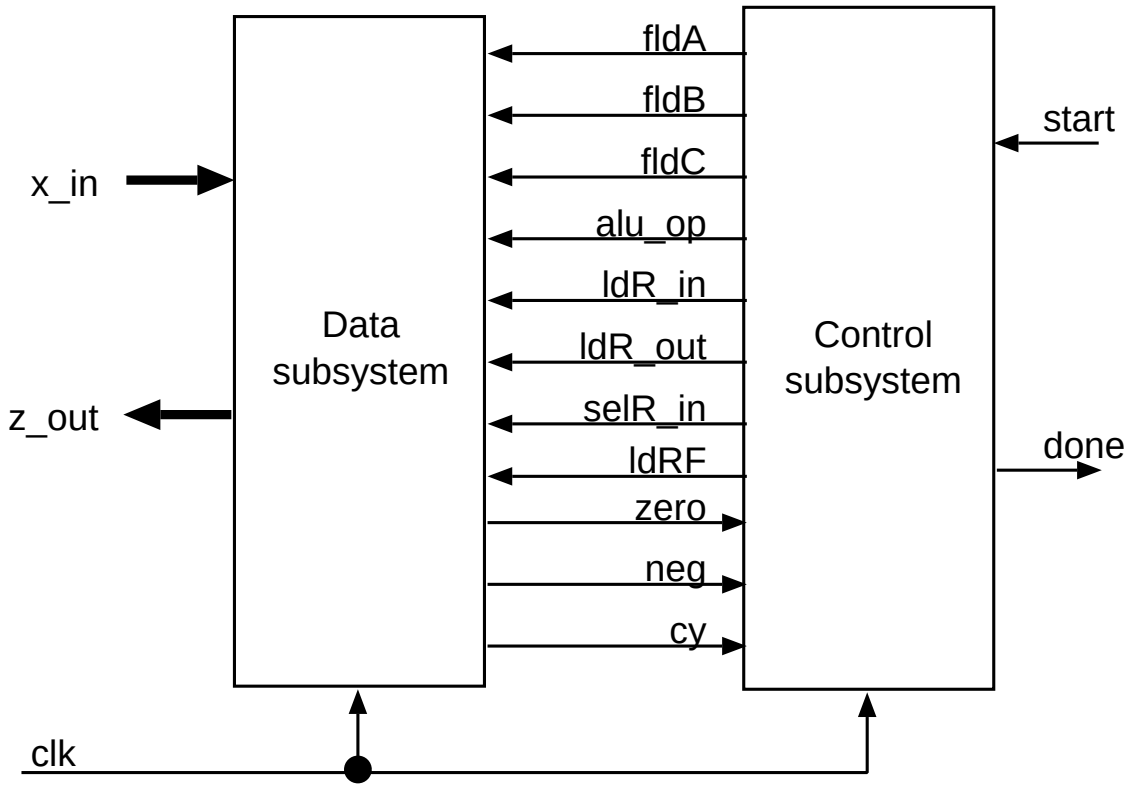

Figure 14.31: BLOCK DIAGRAM

STRUCTURAL DESCRIPTION (cont.)

```
 ARCHITECTURE structural OF micro IS
  SIGNAL fld_A,fld_B,fld_C: UNSIGNED(2 DOWNTO 0);
  SIGNAL alu_op           : UNSIGNED(1 DOWNTO 0);
  SIGNAL zero, neg, cy    : STD_LOGIC ;
  SIGNAL ldR_in,ldR_out   : STD_LOGIC ;
  SIGNAL selR_in,ldRF     : STD_LOGIC ;
BEGIN
  U1: ENTITY microdata
      PORT MAP(x_in,fld_A,fld_B,fld_C,alu_op,
               ldR_in,ldR_out,selR_in,ldRF,zero,neg,cy,z_out,clk)
  U2: ENTITY microctrl
      PORT MAP(start,zero,neg,cy,fld_A,fld_B,fld_C,alu_op,
               ldR_in,ldR_out,selR_in,ldRF,done,clk);
END structural;
```

Example 14.3: COUNTING THE NUMBER OF ONES

- Count the number of 1's in an 8-bit input vector
- Use the system of Fig. 14.26

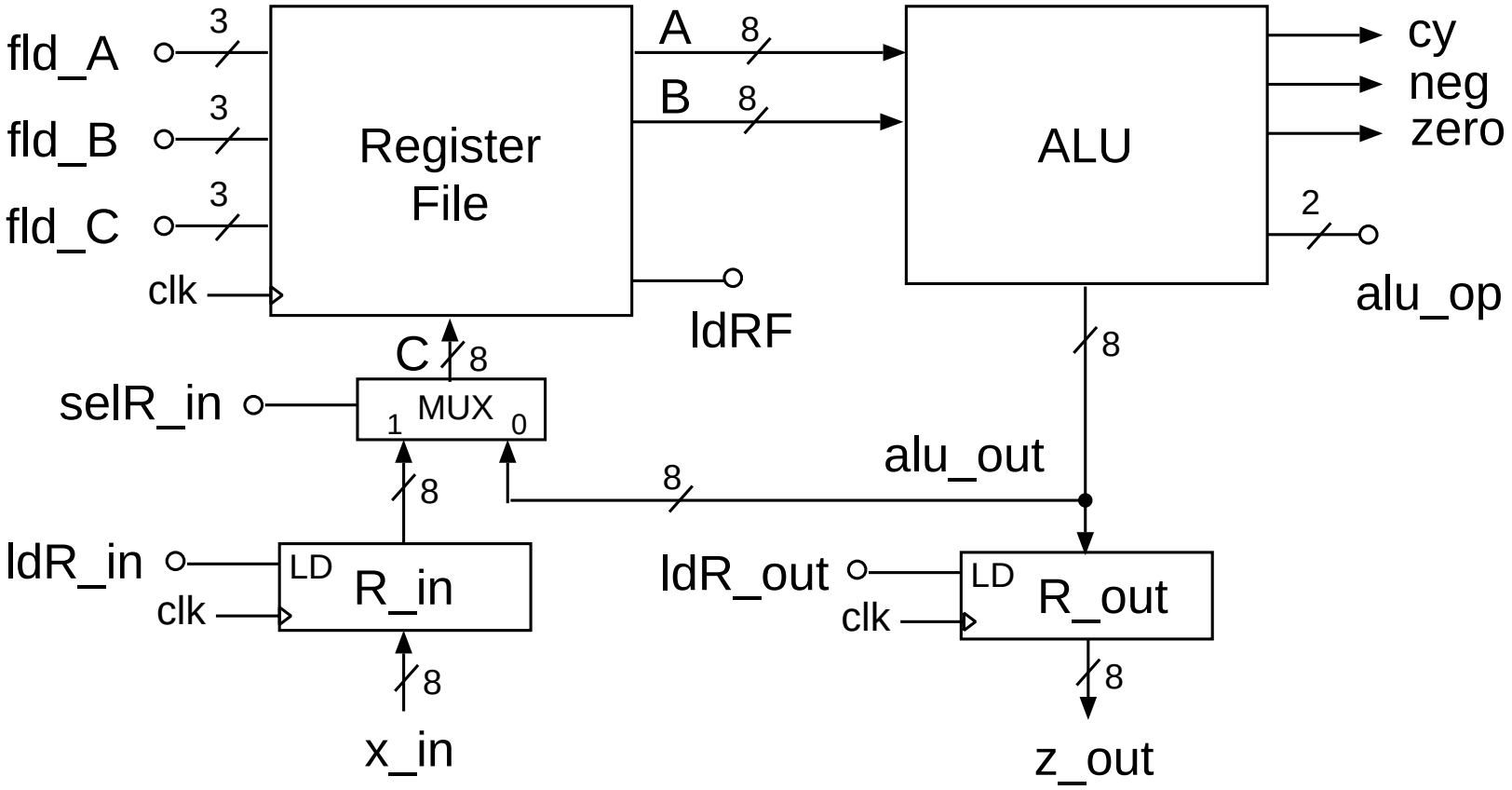

Figure 14.26: DATA SUBSYSTEM.

SPECIFICATION OF SYSTEM IN Example 14.3

```
ENTITY micro IS
  PORT(start: IN  STD_LOGIC          ;   -- start signal
       x_in : IN  SIGNED(7 DOWNTO 0);   -- input vector
       z_out: OUT SIGNED(7 DOWNTO 0);   -- result
       done : OUT STD_LOGIC          ;   -- done signal
       clk  : IN  STD_LOGIC)         ;
END micro;

ARCHITECTURE specif OF micro IS
BEGIN
  PROCESS (start)
    VARIABLE x,n: SIGNED(7 DOWNTO 0);
  BEGIN
    IF (start'EVENT AND start = '1') THEN
      done <= '0';
      x:= x_in;  n:= (OTHERS => '0');
      FOR i IN 1 TO 8 LOOP
        IF (x(x'LEFT) = '1') THEN n:= n+1; END IF;
        x:= x(x'LEFT-1 DOWNTO 0) & '0' ;
      END LOOP;
      z_out <= n;
      done  <= '1';
    END IF;
  END PROCESS;
END specif;
```

	mode	alu_op	fld_			ldRF	ldR_		selR_	s_d	r_d	control format
			A	B	C		in	out	in			
	mode	(cond., cond_val)	branch address									branch format
0:	0	sub=01	0	0	0	1	0	0	0	1	0	R0 <- 0; set done
1:	1	(start,0) =000	1									branch if start = 0
2:	0	inc=11	0	0	3	1	1	0	0	0	1	input x_in; R3 <- 1; clear done
3:	0	add=00	0	0	2	1	0	0	1	0	0	R2 <- Rin;
4:	0	add=00	0	0	7	1	0	0	0	0	0	R7 <- 0;
5:	0	add=00	2	2	2	1	0	0	0	0	0	R2 <- R2+R2;
6:	1	(cy,0) =110	8									branch if cy = 0
7:	0	inc=11	7	0	7	1	0	0	0	0	0	R7 <- R7+1;
8:	0	add=00	3	3	3	1	0	0	0	0	0	R3 <- R3+R3
9:	1	(cy,0) =110	5									branch if cy = 0
10:	0	add=00	7	0	7	1	0	1	0	0	0	Rout <- R7;
11:	1	(cy,0) =110	0									done; branch to 0

Figure 14.33: MICROPROGRAM FOR Example 14.3.

```
-- to be included in description of control subsystem
-- (spaces inserted between fields for clarity)
    VARIABLE cs: csarray                -- control store
                       := (0 => "0 01 000 000 000 1 00 0 10",
                           1 => "1 000       000000000000001",
                           2 => "0 11 000 000 011 1 10 0 01",
                           3 => "0 00 000 000 010 1 00 1 00",
                           4 => "0 00 000 000 111 1 00 0 00",
                           5 => "0 00 010 010 010 1 00 0 00",
                           6 => "1 110       000000000001000",
                           7 => "0 11 111 000 111 1 00 0 00",
                           8 => "0 00 011 011 011 1 00 0 00",
                           9 => "1 110       000000000000101",
                          10 => "0 00 111 000 111 1 01 0 00",
                          11 => "1 110       000000000000000");
```

Figure 14.34: CONTROL STORE CONTENTS FOR Example 14.3.