DESIGN OF GATE NETWORKS

- DESIGN OF TWO-LEVEL NETWORKS:
  AND-OR and OR-AND NETWORKS

- MINIMAL TWO-LEVEL NETWORKS
  KARNAUGH MAPS
  MINIMIZATION PROCEDURE AND TOOLS
  LIMITATIONS OF TWO-LEVEL NETWORKS

- DESIGN OF TWO-LEVEL NAND-NAND and NOR-NOR NETWORKS

- PROGRAMMABLE LOGIC: PLAs and PALs.

DESIGN OF TWO-LEVEL NETWORKS

IMPLEMENTATION:

Level 1 (optional) NOT GATES

Level 2 AND GATES

Level 3 OR GATES

LITERALS
(uncomplemented and complemented variables)
NOT GATES (IF NEEDED)

PRODUCTS: AND gates

SUM: OR gate

MULTIOUTPUT NETWORKS: ONE OR GATE USED FOR EACH OUTPUT

PRODUCT OF SUMS NETWORKS - SIMILAR

MODULO-64 INCREMENTER

Input: $0 \leq x \leq 63$

Output: $0 \leq z \leq 63$

Function: $z = (x + 1) \bmod 64$

x	010101
z	010110

x	001111
z	010000

- RADIX-2 REPRESENTATION

$$z_i = \begin{cases} 1 \text{ if } (x_i = 1 \text{ and } \textit{there exists } j < i \textit{ such that } x_j = 0) \\ \quad \text{or } (x_i = 0 \text{ and } x_j = 1 \textit{ for all } j < i) \\ 0 \text{ otherwise} \end{cases}$$

$$\begin{aligned} z_5 &= x_5(x_4' + x_3' + x_2' + x_1' + x_0') + x_5' x_4 x_3 x_2 x_1 x_0 \\ &= x_5 x_4' + x_5 x_3' + x_5 x_2' + x_5 x_1' + x_5 x_0' + x_5' x_4 x_3 x_2 x_1 x_0 \\ z_4 &= x_4 x_3' + x_4 x_2' + x_4 x_1' + x_4 x_0' + x_4' x_3 x_2 x_1 x_0 \\ z_3 &= x_3 x_2' + x_3 x_1' + x_3 x_0' + x_3' x_2 x_1 x_0 \\ z_2 &= x_2 x_1' + x_2 x_0' + x_2' x_1 x_0 \\ z_1 &= x_1 x_0' + x_1' x_0 \\ z_0 &= x_0' \end{aligned}$$

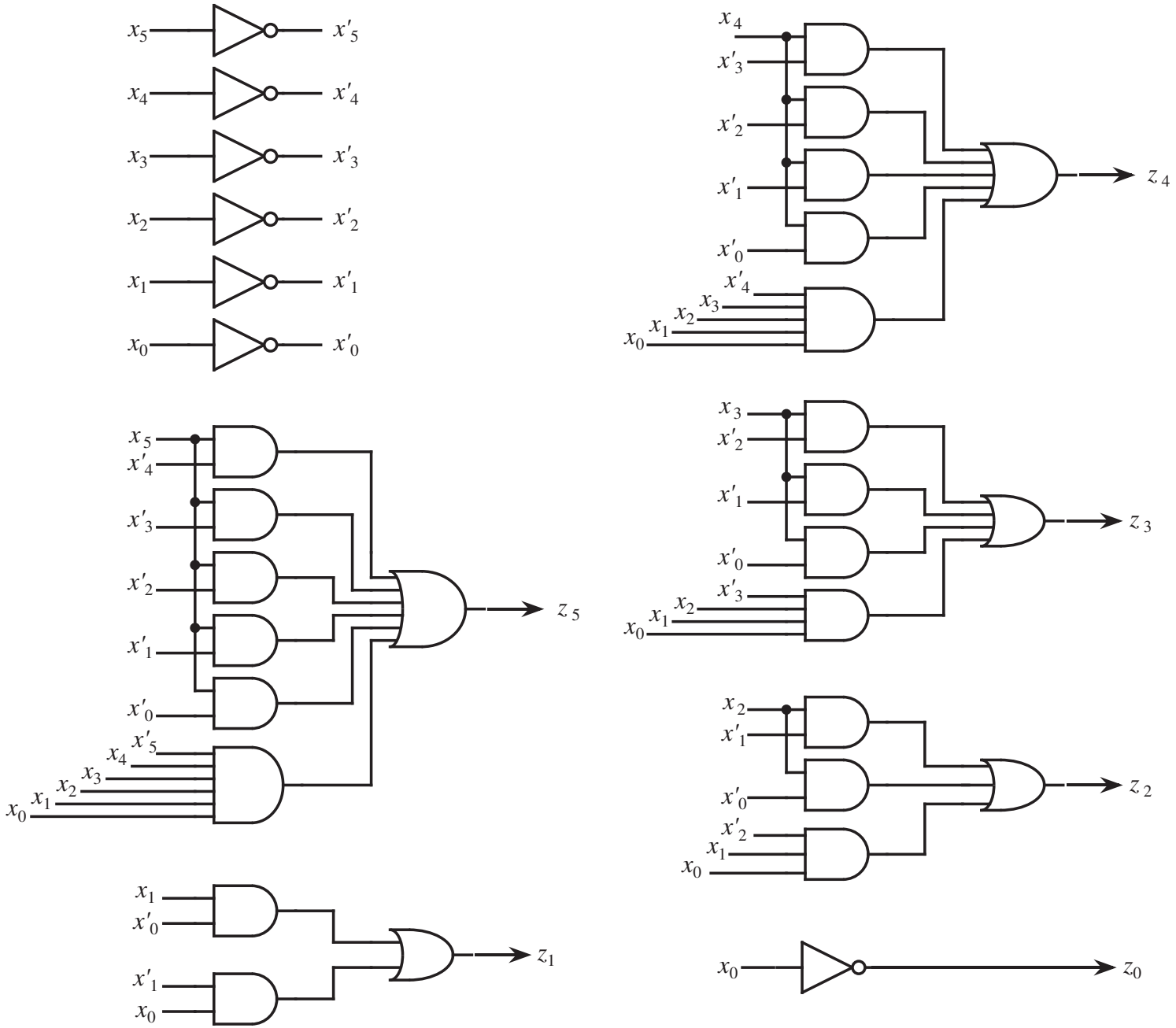

Figure 5.1: NOT-AND-OR MODULO-64 INCREMENTER NETWORK.

UNCOMPLEMENTED AND COMPLEMENTED INPUTS AVAILABLE

- TWO TYPES OF TWO-LEVEL NETWORKS:

AND-OR **NETWORK** $\Leftrightarrow$ SUM OF PRODUCTS (NAND-NAND NETWORK)

OR-AND **NETWORK** $\Leftrightarrow$ PRODUCT OF SUMS (NOR-NOR NETWORK)

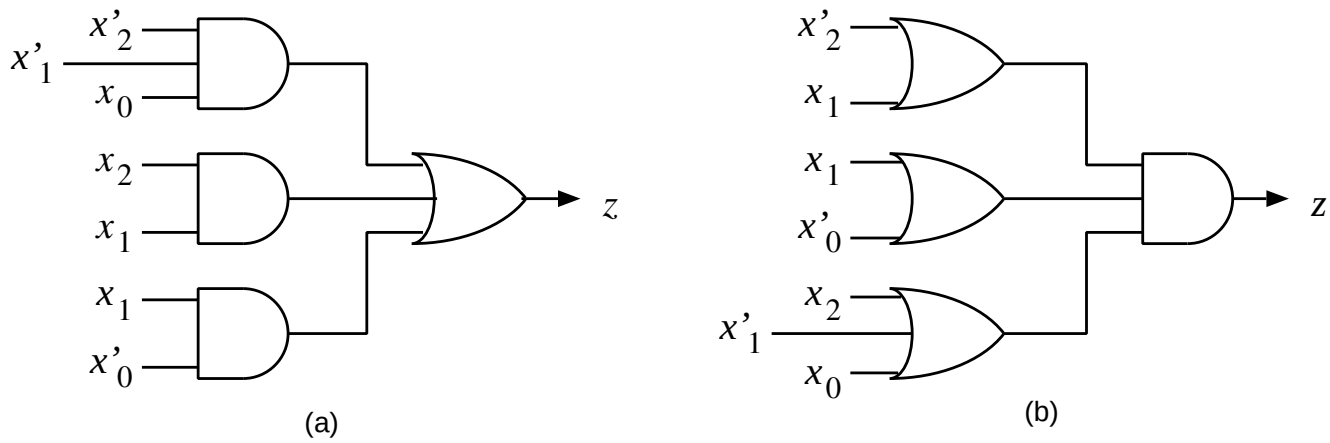

Figure 5.2: AND-OR and OR-AND NETWORKS.

$$E(x_2, x_1, x_0) = x_2' x_1' x_0 + x_2 x_1 + x_1 x_0'$$

$$E(x_2, x_1, x_0) = (x_2' + x_1)(x_1 + x_0')(x_2 + x_1' + x_0)$$

MINIMAL TWO-LEVEL NETWORKS

1. INPUTS: UNCOMPLEMENTED AND COMPLEMENTED

2. FANIN UNLIMITED

3. SINGLE-OUTPUT NETWORKS

4. MINIMAL NETWORK:

   MINIMUM NUMBER OF GATES WITH MINIMUM NUMBER OF INPUTS

   (minimal expression: min. number of terms with min. number of literals)

NETWORKS WITH DIFFERENT COST

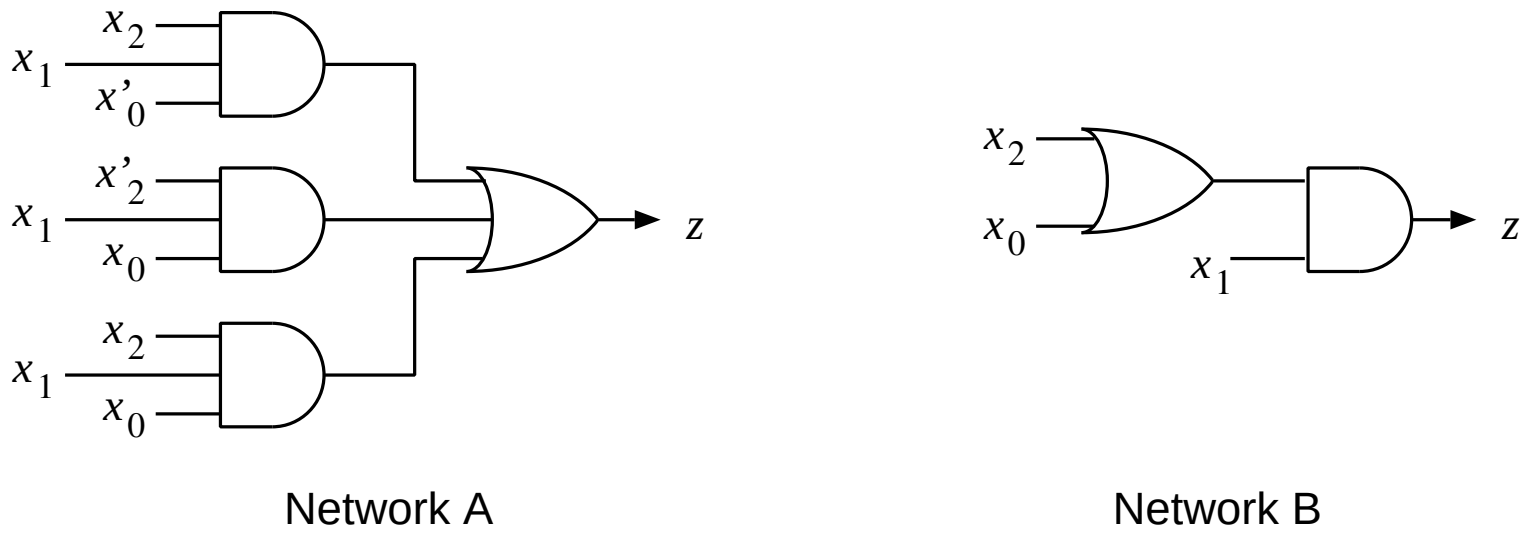

Figure 5.3: NETWORKS WITH DIFFERENT COST TO IMPLEMENT $f(x_2, x_1, x_0) = one\text{-}set(3,6,7)$.

MINIMAL EXPRESSIONS

- EQUIVALENT BUT DIFFERENT COST

$$E_1(x_2, x_1, x_0) = x_2' x_1 x_0' + x_1' x_0 + x_2 x_0$$
$$E_2(x_2, x_1, x_0) = x_2 x_1 x_0 + x_2' x_1 x_0' + x_2' x_1' x_0 + x_2 x_1' x_0$$

- BOTH MINIMAL SP AND PS MUST BE OBTAINED AND COMPARED

- BASIS:

$$ab + ab' = a \quad \text{(for sum of products)}$$
$$(a + b)(a + b') = a \quad \text{(for product of sums)}$$

GRAPHICAL REPRESENTATION OF SWITCHING FUNCTIONS: kARNAUGH MAPS

- 2-DIMENSIONAL ARRAY OF CELLS
- n VARIABLES $\longrightarrow$ 2^n CELLS
- cell i $\longleftrightarrow$ ASSIGNMENT i

  ADJACENCY CONDITION

  ANY SET OF 2^r ADJACENT ROWS (COLUMNS):
  ASSIGNMENTS DIFFER IN r VARIABLES
- REPRESENTING SWITCHING FUNCTIONS
- REPRESENTING SWITCHING EXPRESSIONS
- GRAPHICAL AID IN SIMPLIFYING EXPRESSIONS

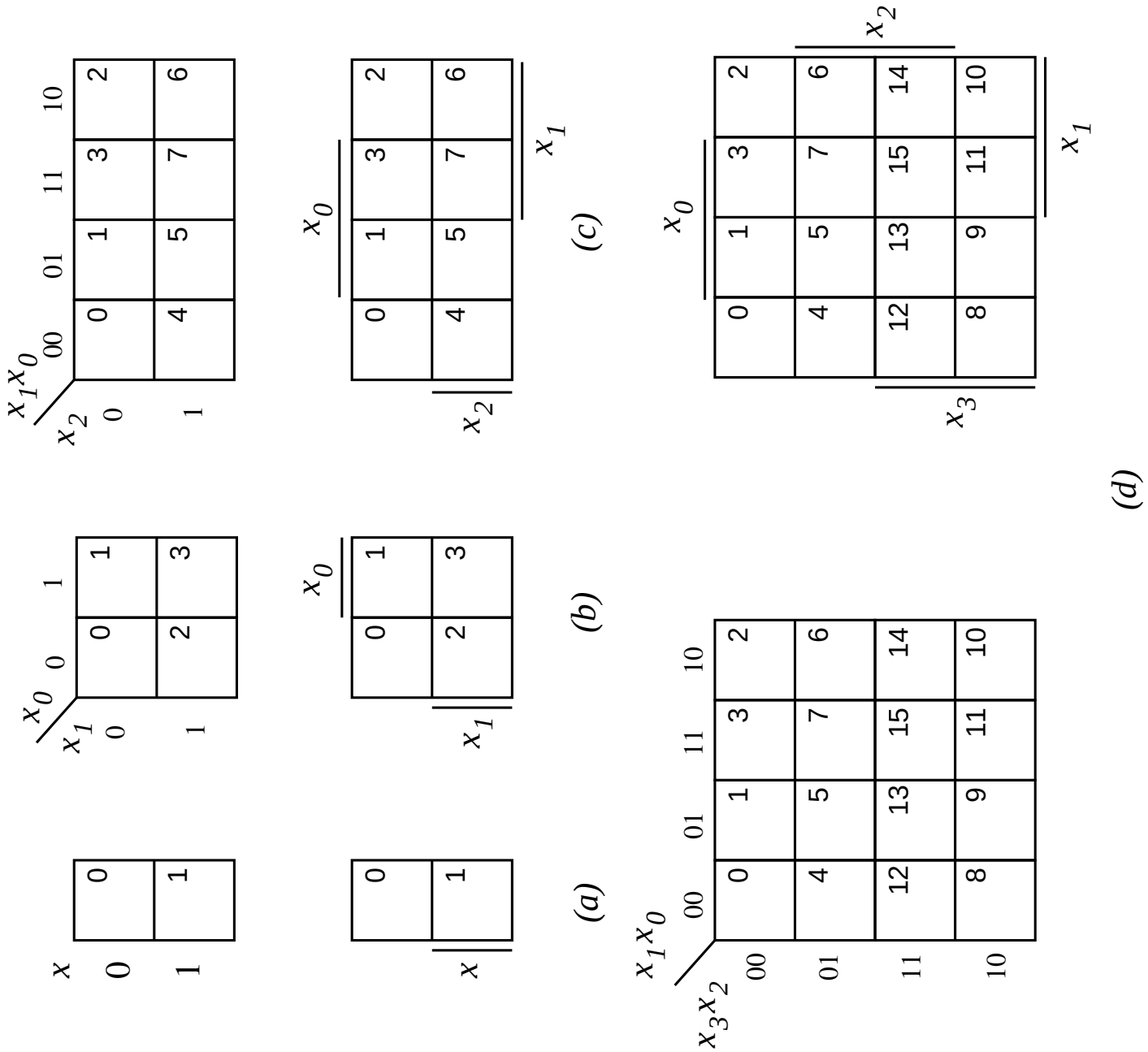

Figure 5.4: K-Maps

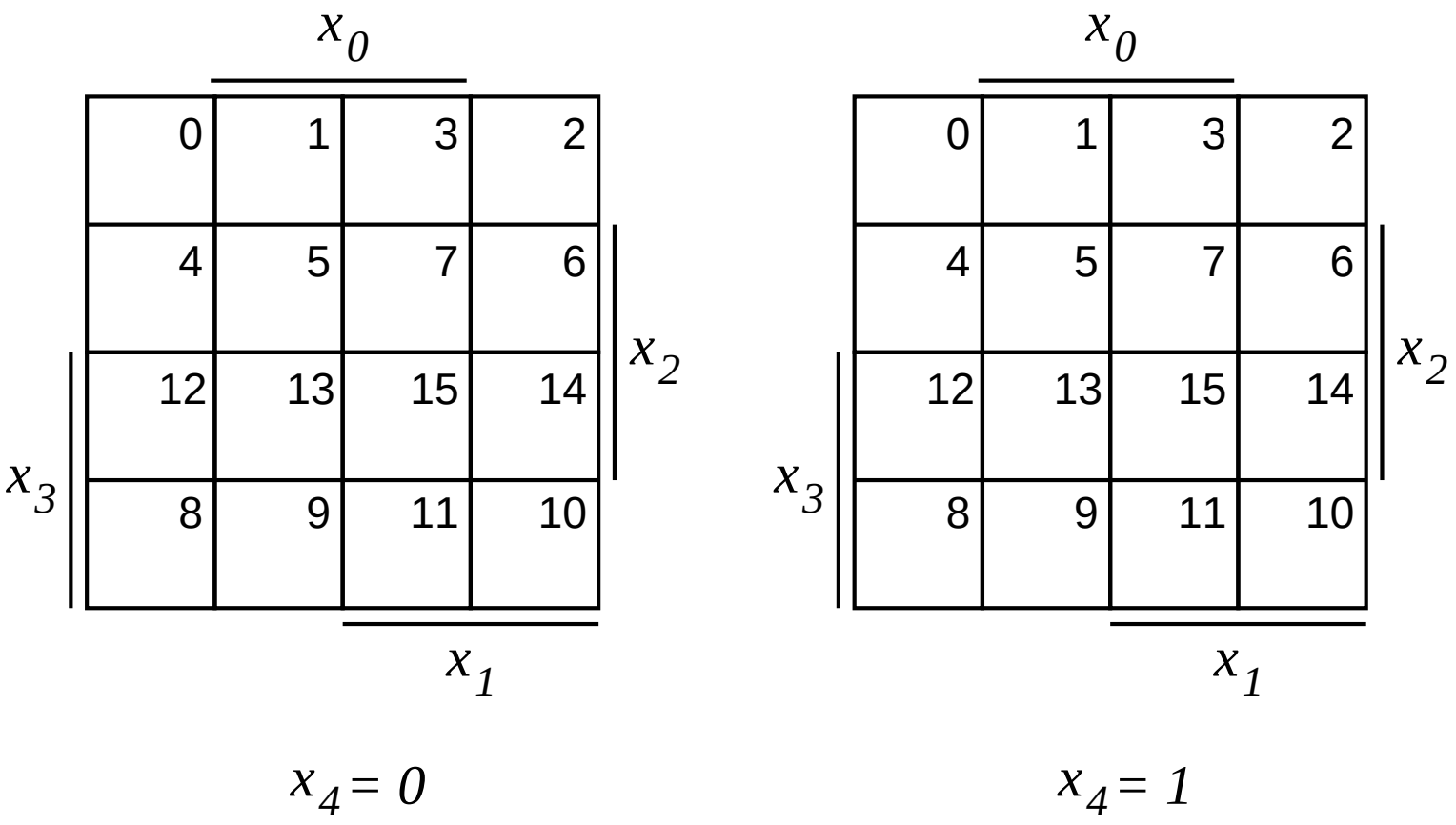

Figure 5.5: K-map FOR FIVE VARIABLES

REPRESENTATION OF SWITCHING FUNCTIONS

$f(x_2, x_1, x_0) = \mathit{one\text{-}set}(0,2,6)$

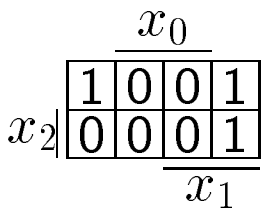

$f(x_3, x_2, x_1, x_0) = \mathit{zero\text{-}set}(1,3,4,6,10,11,13)$

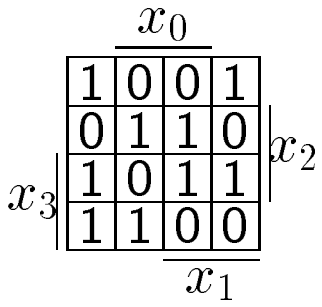

$f(x_2, x_1, x_0) = [\mathit{one\text{-}set}(0,4,5), \quad \mathit{dc\text{-}set}(2,3)]$

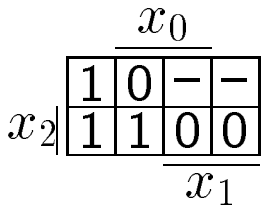

RECTANGLES OF 1-CELLS AND SUM OF PRODUCTS

1. MINTERM m_j CORRESPONDS TO 1-CELL WITH LABEL j.
2. PRODUCT TERM OF $n-1$ LITERALS $\longleftrightarrow$ RECTANGLE OF TWO ADJACENT 1-CELLS

$$\begin{aligned} x_3x_1'x_0 &= x_3x_1'x_0(x_2 + x_2') \\ &= x_3x_2x_1'x_0 + x_3x_2'x_1'x_0 \\ &= m_{13} + m_9 \end{aligned}$$

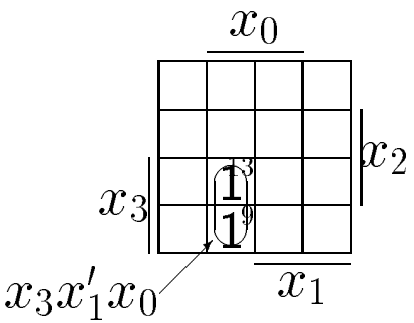

Figure 5.6

RECTANGLES OF 1-CELLS AND SUM OF PRODUCTS (cont.)

3. PRODUCT TERM OF $n-2$ LITERALS $\longleftrightarrow$ RECTANGLE OF FOUR ADJACENT 1-CELLS

$$\begin{aligned} x_3x_0 &= x_3x_0(x_1 + x_1')(x_2 + x_2') \\ &= x_3x_2'x_1'x_0 + x_3x_2'x_1x_0 + x_3x_2x_1'x_0 + x_3x_2x_1x_0 \\ &= m_9 + m_{11} + m_{13} + m_{15} \end{aligned}$$

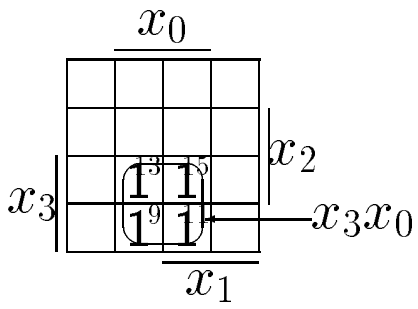

Figure 5.6

4. PRODUCT TERM OF $n-s$ LITERALS $\longleftrightarrow$ RECTANGLE OF 2^s ADJACENT 1-CELLS

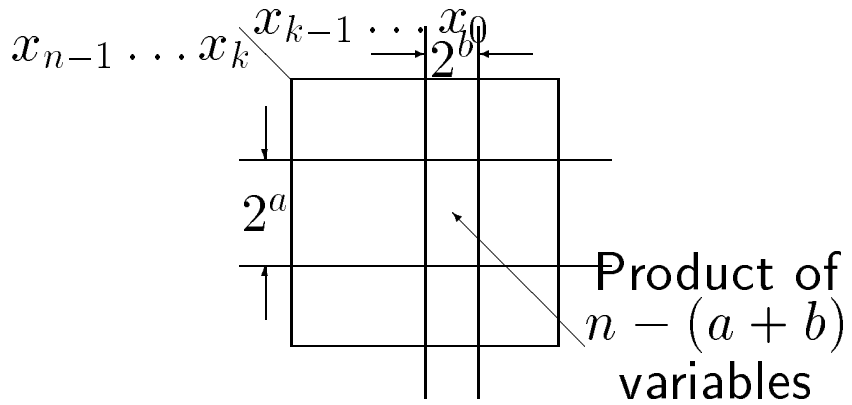

Figure 5.7: Representation of product of $n-(a+b)$ variables.

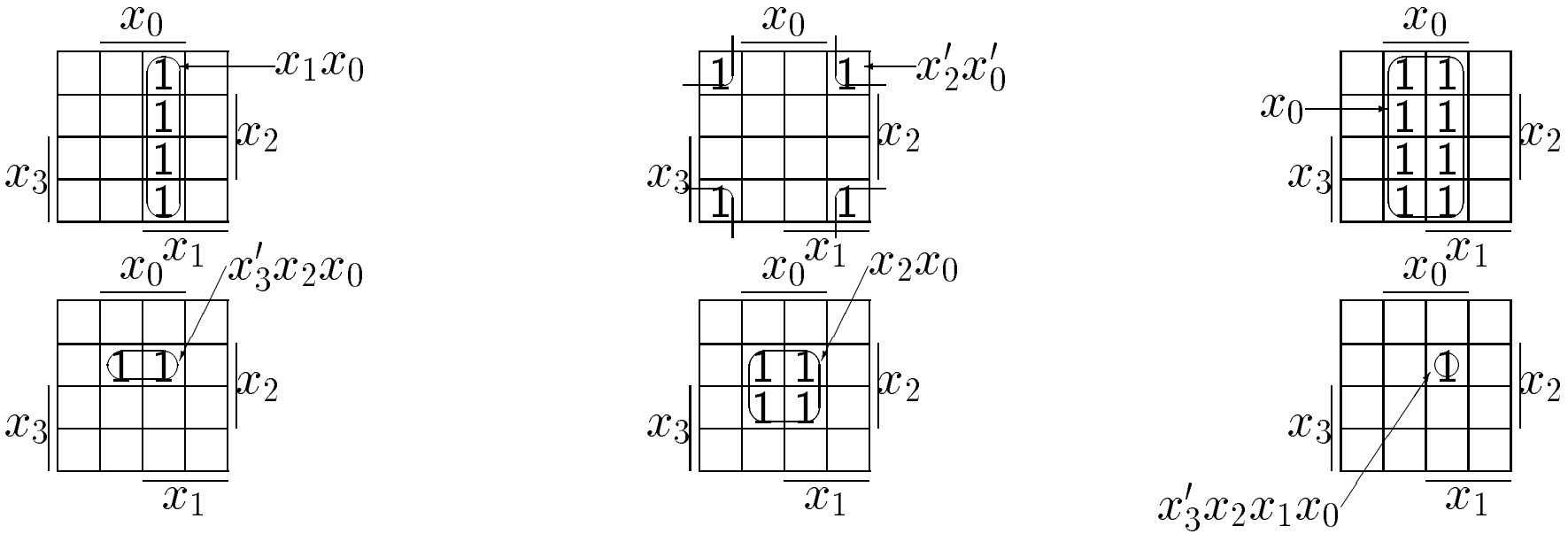

Figure 5.8: Product terms and rectangles of 1-cells.

SUM OF PRODUCTS

represented in a K-map by the union of rectangles

$$E(x_3, x_2, x_1, x_0) = x_3' x_2 x_1 + x_2' x_1 x_0 + x_0'$$

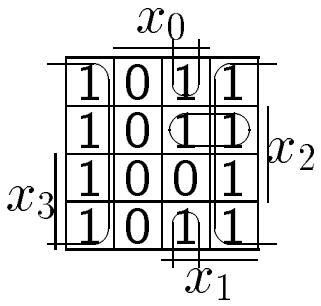

$$E(a, b, c) = ab + ac + b'c'$$

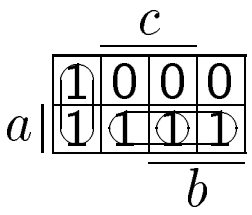

RECTANGLES OF 0-CELLS AND PRODUCT OF SUMS

0-cell 13 CORRESPONDS TO THE MAXTERM

$M_{13} = x_3' + x_2' + x_1 + x_0'$

RECTANGLE OF $2^a \times 2^b$ 0-cells $\longleftrightarrow$ SUM TERM OF $n-(a+b)$ LITERALS

MINIMIZATION OF SUMS OF PRODUCTS

IMPLICANT: PRODUCT TERM FOR WHICH **f=1**

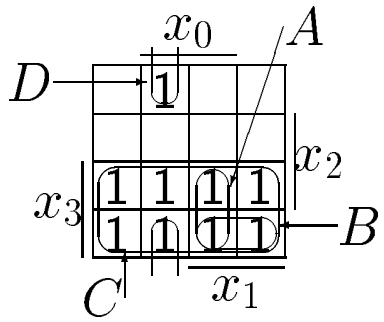

Figure 5.9: Implicant representation.

IMPLICANTS: $x_3'x_2'x_1'x_0$, ALL PRODUCT TERMS WITH x_3

PRIME iMPLICANT: IMPLICANT NOT COVERED BY ANOTHER IMPLICANT

PRIME IMPLICANTS: $x_2'x_1'x_0$, x_3

FIND ALL PIs

a) $f(x_2, x_1, x_0) = \mathit{one\text{-}set}(2,4,6)$

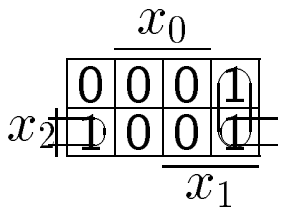

PIs: x_2x_0' and x_1x_0'

b) $f(x_2, x_1, x_0) = \mathit{one\text{-}set}(0,1,5,7)$

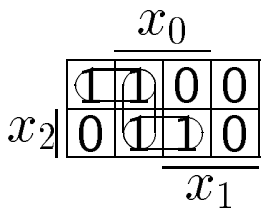

PIs: $x_2'x_1'$, x_2x_0, and $x_1'x_0$

c) $f(x_3, x_2, x_1, x_0) = \mathit{one\text{-}set}(0,3,5,7,11,12,13,15)$

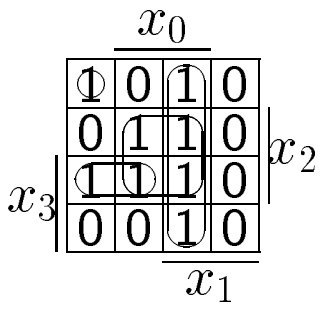

PIs: x_2x_0, x_1x_0, $x_3x_2x_1'$, and $x_3'x_2'x_1'x_0'$

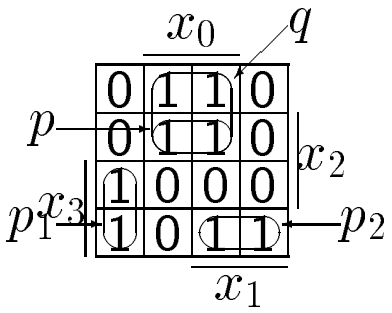

Figure 5.10: MINIMAL SUM OF PRODUCTS AND PRIME IMPLICANTS.

Example 5.9

$$E(x_2, x_1, x_0) = x_2x_1'x_0' + x_2x_1x_0' + x_1x_0'$$

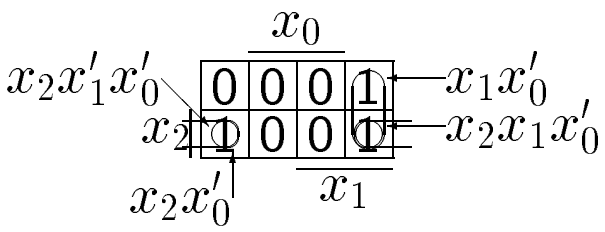

not PIs: $x_2x_1'x_0'$ and $x_2x_1x_0'$

PI: x_2x_0', x_1x_0'

REDUCED SP: $E(x_2, x_1, x_0) = x_2x_0' + x_1x_0'$

ESSENTIAL PRIME IMPLICANTS (EPI)

$p_e(\underline{a}) = 1$ and $p(\underline{a}) = 0$ FOR ANY OTHER PI p

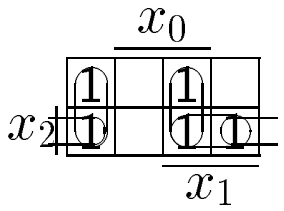

EPIs: $x_1'x_0'$ and x_1x_0

NON-ESSENTIAL: x_2x_1, x_2x_0'.

- ALL EPIs ARE INCLUDED IN A MINIMAL SP

PROCEDURE FOR FINDING MIN SP

1. DETERMINE ALL PIs
2. OBTAIN THE EPIs
3. IF NOT ALL 1-CELLS COVERED, CHOOSE A COVER FROM THE REMAINING PIs

EXAMPLE 5.10

FIND A MINIMAL SP:

a) $E(x_3, x_2, x_1, x_0) = x_3'x_2' + x_3'x_2x_0 + x_1x_0$

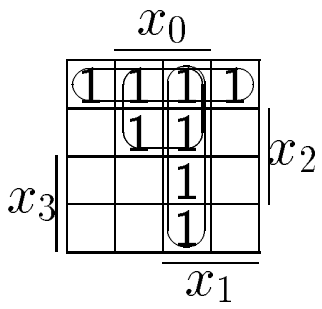

- PIs: $x_3'x_2'$, $x_3'x_0$, and x_1x_0
- ALL EPIs
- UNIQUE MIN SP: $x_3'x_2' + x_3'x_0 + x_1x_0$

b) $E(x_2, x_1, x_0) = \Sigma\, m(0, 3, 4, 6, 7)$

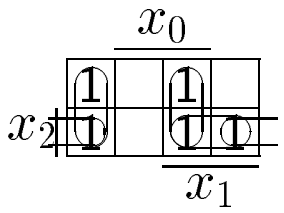

- PIs: $x_1'x_0'$, x_1x_0, x_2x_0', and x_2x_1
- EPIs: $x_1'x_0'$ and x_1x_0
- EXTRA COVER: x_2x_0' or x_2x_1
- TWO MIN SPs:

$$x_1'x_0' + x_1x_0 + x_2x_0' \quad \text{and} \quad x_1'x_0' + x_1x_0 + x_2x_1$$

c) $E(x_2, x_1, x_0) = \Sigma\, m(0, 1, 2, 5, 6, 7)$

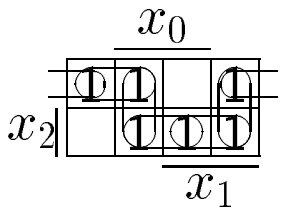

- PIs: $x_2'x_1'$, $x_2'x_0'$, x_2x_0, x_2x_1, $x_1'x_0$, and x_1x_0'
- No EPIs
- TWO MIN SPs

$$x_2'x_1' + x_2x_0 + x_1x_0' \quad \text{and} \quad x_2'x_0' + x_1'x_0 + x_2x_1$$

MINIMAL SPs FOR INCOMPLETELY SPECIFIED FUNCTIONS

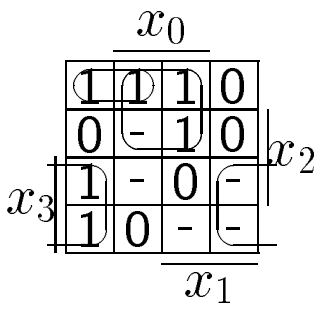

A minimal SP

$$E(x_3, x_2, x_1, x_0) = x_3 x_0' + x_3' x_0 + x_3' x_2' x_1'$$

MINIMIZATION OF PRODUCTS OF SUMS

IMPLICATE: SUM TERM FOR WHICH $f = 0$.

PRIME IMPLICATE: IMPLICATE NOT COVERED BY ANOTHER IMPLICATE

ESSENTIAL PRIME IMPLICATE: AT LEAST ONE "CELL" NOT INCLUDED IN OTHER IMPLICATE

$f(x_3, x_2, x_1, x_0) = \textit{zero-set}(7,13,15)$

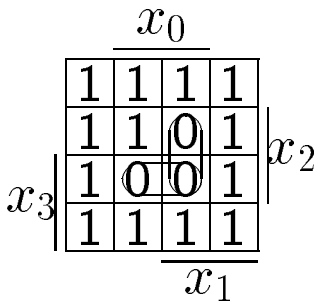

THE PRIME IMPLICATES: $(x_3' + x_2' + x_0')$ and $(x_2' + x_1' + x_0')$

BOTH ESSENTIAL

PROCEDURE FOR FINDING MIN PS

1. DETERMINE ALL PRIME IMPLICATES
2. DETERMINE THE ESSENTIAL PRIME IMPLICATES
3. FROM SET OF NONESSENTIAL PRIME IMPLICATES, SELECT COVER OF REMAINING 0-CELLS

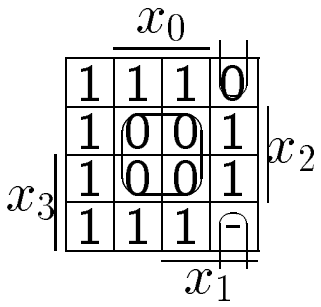

- THE PRIME IMPLICATES: $(x_0' + x_2')$ and $(x_0 + x_2 + x_1')$
- BOTH ESSENTIAL, THE MINIMAL PS IS $(x_0' + x_2')(x_0 + x_2 + x_1')$

MINIMAL TWO-LEVEL GATE NETWORK DESIGN: EXAMPLE 5.14

Input: $x \in \{0, 1, 2, ..., 9\}$, coded in BCD as
$\underline{x} = (x_3, x_2, x_1, x_0),\ x_i \in \{0, 1\}$

Output: $z \in \{0, 1\}$

Function: $z = \begin{cases} 1 \ \textbf{if} \ \ x \in \{0, 2, 3, 5, 8\} \\ 0 \ \textbf{otherwise} \end{cases}$

THE VALUES {10,11,12,13,14,15} ARE "DON'T CARES"

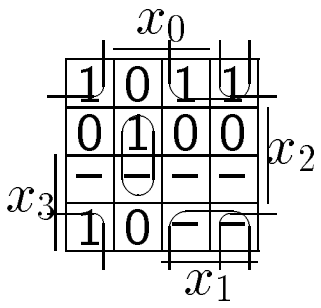

MIN SP: $z = x_2' x_1 + x_2' x_0' + x_2 x_1' x_0$

MIN PS: $z = (x_2' + x_1')(x_2' + x_0)(x_2 + x_1 + x_0')$

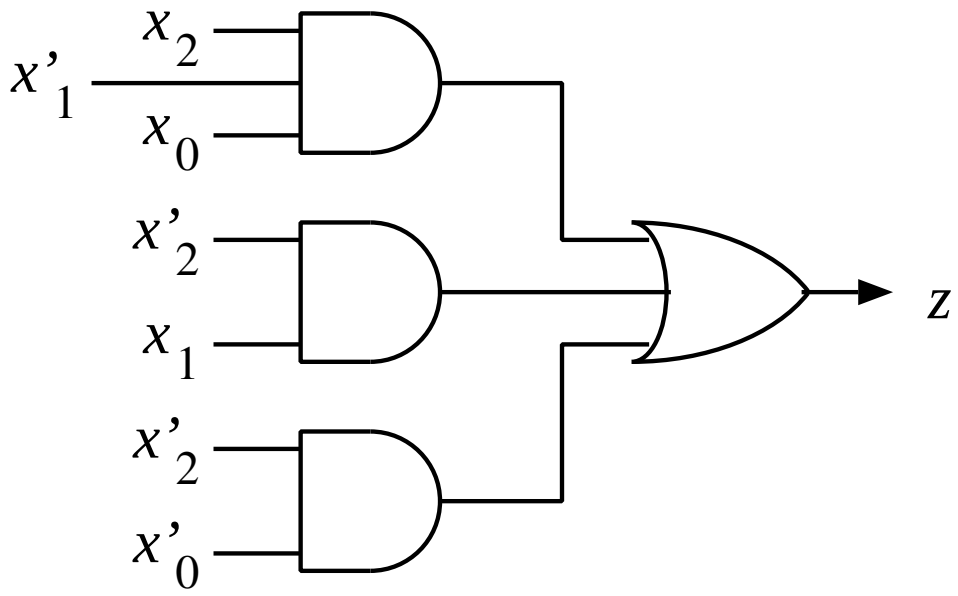

Figure 5.11: MINIMAL AND-OR NETWORK

EXAMPLE 5.15

Input: $x \in \{0, 1, 2, ..., 15\}$
represented in binary code by $\underline{x} = (x_3, x_2, x_1, x_0)$

Output: $z \in \{0, 1\}$

Function: $z = \begin{cases} 1 \ \textbf{if} \ \ x \in \{0, 1, 3, 5, 7, 11, 12, 13, 14\} \\ 0 \ \textbf{otherwise} \end{cases}$

THE K-MAP:

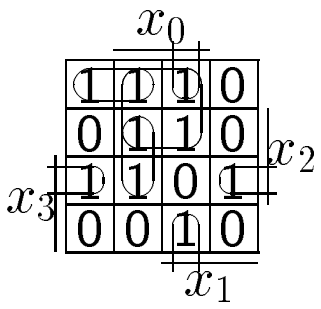

min SP: $z = x_3'x_0 + x_3'x_2'x_1' + x_2x_1'x_0 + x_3x_2x_0' + x_2'x_1x_0$

min PS: $z = (x_3' + x_2 + x_1)(x_3 + x_2' + x_0)(x_2 + x_1' + x_0)(x_3' + x_2' + x_1' + x_0')$

COST(PS) < COST(SP)

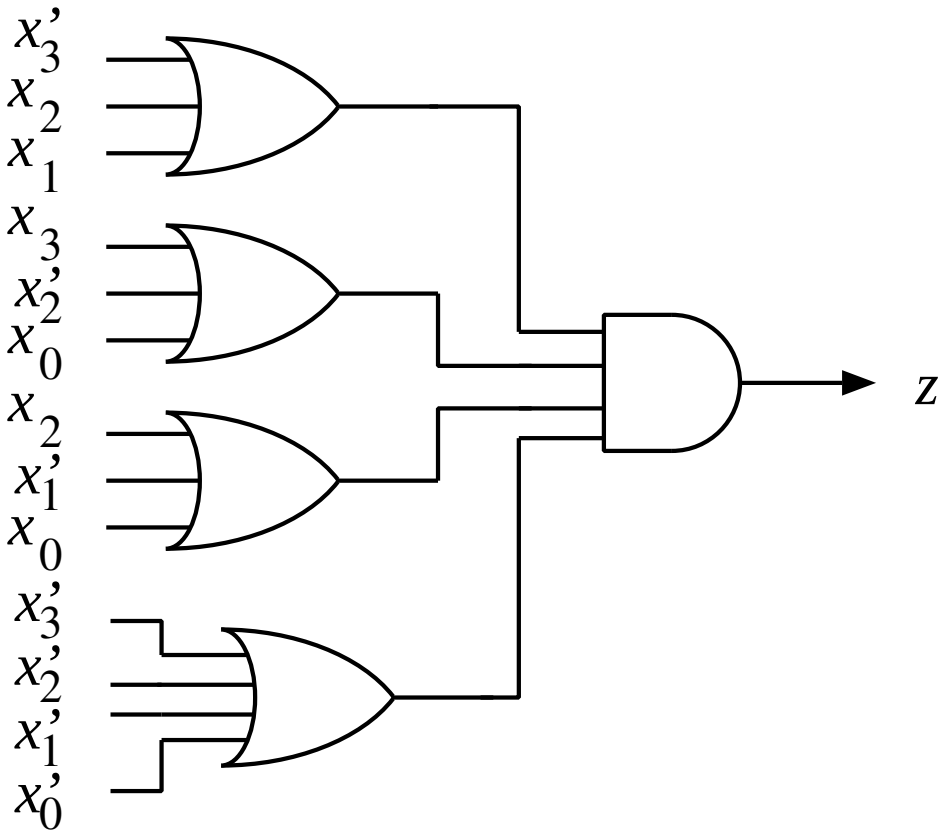

Figure 5.12: MINIMAL OR-AND NETWORK

DESIGN OF MULTIPLE-OUTPUT TWO-LEVEL GATE NETWORKS

- SEPARATE NETWORK FOR EACH OUTPUT: NO SHARING

EXAMPLE 5.16

Inputs: $(x_2, x_1, x_0), \quad x_i \in \{0, 1\}$
Output: $z \in \{0, 1, 2, 3\}$
Function: $z = \Sigma_{i=0}^{2} x_i$

1. THE SWITCHING FUNCTIONS IN TABULAR FORM ARE

x_2	x_1	x_0	z_1	z_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

EXAMPLE 5.16 (cont.)

2. THE CORRESPONDING K-MAPS ARE

z_1

x_2 \ x_0	0	1
0	0	1
1	0	1

z_0

x_2 \ x_0	0	1
0	0	1
1	1	0

3. MINIMAL SPs:

$$z_1 = x_2x_1 + x_2x_0 + x_1x_0$$
$$z_0 = x_2'x_1'x_0 + x_2'x_1x_0' + x_2x_1'x_0' + x_2x_1x_0$$

4. MINIMAL PSs:

$$z_1 = (x_2 + x_0)(x_2 + x_1)(x_1 + x_0)$$
$$z_0 = (x_2 + x_1 + x_0)(x_2 + x_1' + x_0')$$
$$(x_2' + x_1 + x_0')(x_2' + x_1' + x_0)$$

5. SP AND PS EXPRESSIONS HAVE THE SAME COST

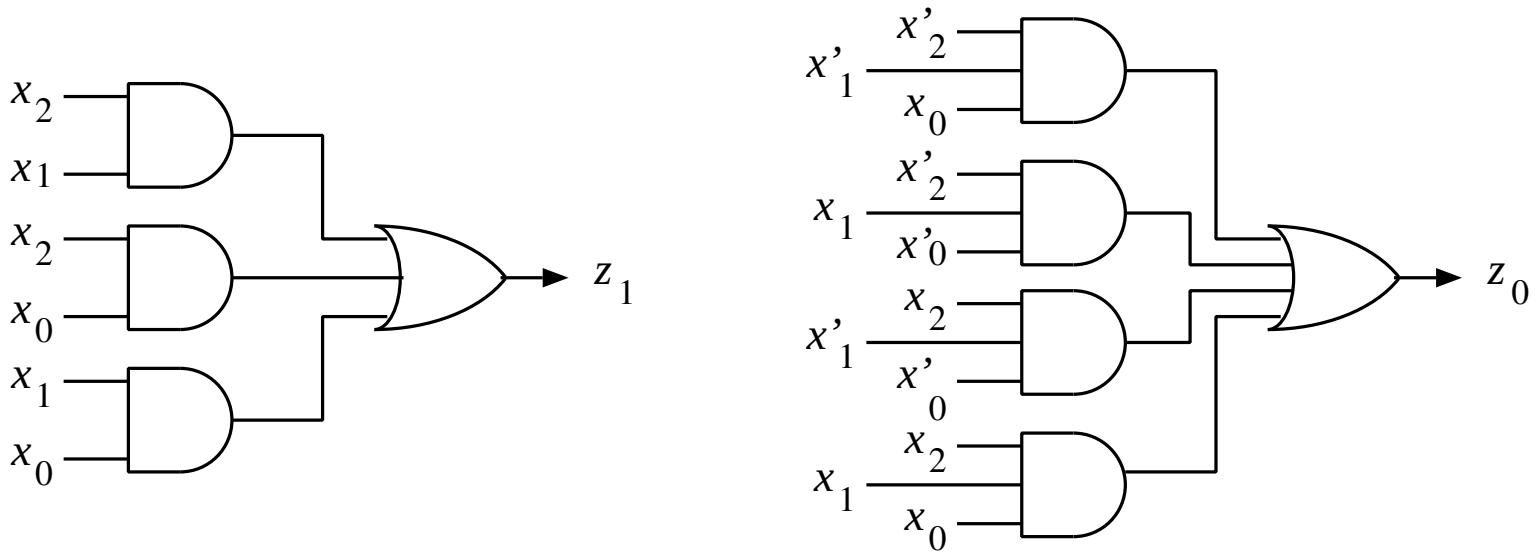

Figure 5.13: MINIMAL TWO-OUTPUT AND-OR NETWORK

TWO-LEVEL NAND-NAND AND NOR-NOR NETWORKS

$$E = p_1 + p_2 + p_3 + \ldots + p_n$$

$p_1, p_2, \ldots$ ARE PRODUCT TERMS

$$E = (p_1' \cdot p_2' \cdot p_3' \ldots p_n')'$$

or

$$E = NAND(NAND_1, NAND_2, NAND_3, \ldots, NAND_n)$$

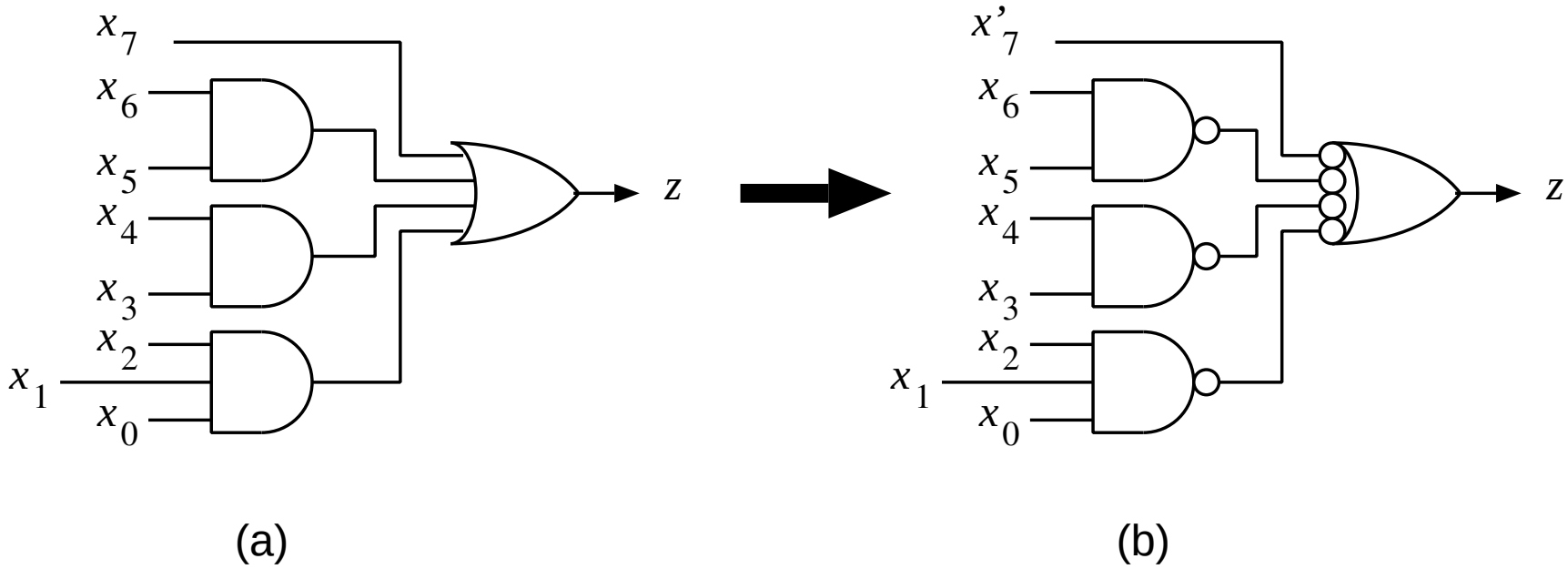

Figure 5.15: TRANSFORMATION OF AND-OR NETWORK INTO NAND NETWORK

EXAMPLE: NOR NETWORK

$$z = x_5'(x_4 + x_3')(x_2 + x_1 + x_0)$$

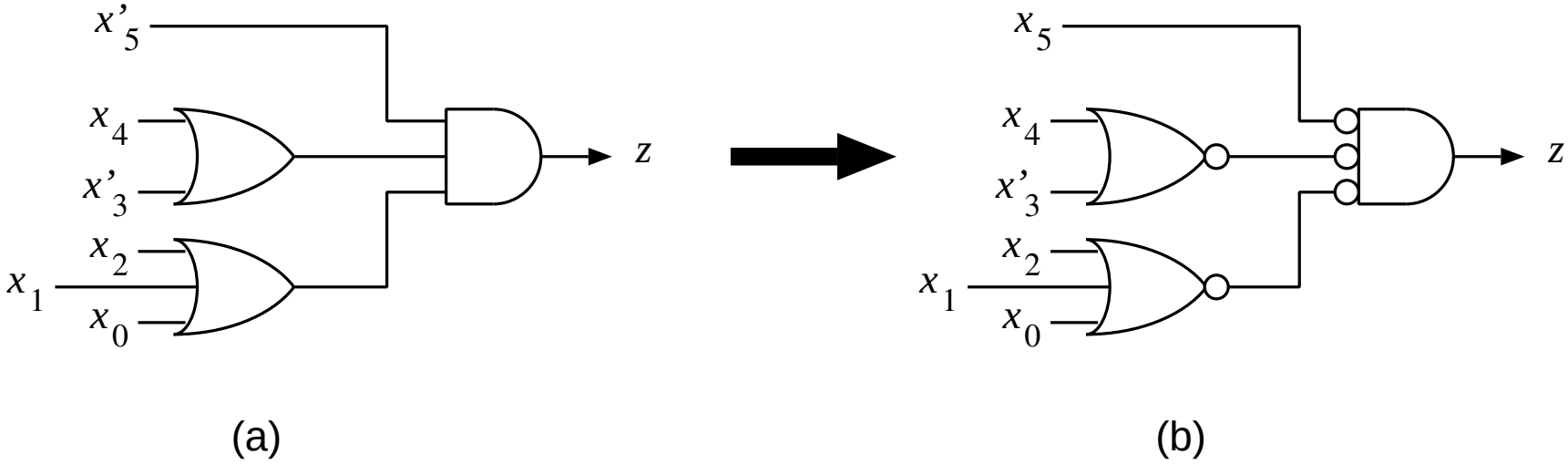

Figure 5.16: EQUIVALENT OR-AND AND NOR NETWORKS

LIMITATIONS OF TWO-LEVEL NETWORKS

1. THE REQUIREMENT OF UNCOMPLEMENTED AND COMPLEMENTED INPUTS

   IF NOT SATISFIED, AN ADDITIONAL LEVEL OF NOT GATES NEEDED

2. A TWO-LEVEL IMPLEMENTATION OF A FUNCTION MIGHT REQUIRE A LARGE NUMBER OF GATES AND IRREGULAR CONNECTIONS

3. EXISTING TECHNOLOGIES HAVE LIMITATIONS IN THE FAN-IN OF THE GATES

4. THE PROCEDURE ESSENTIALLY LIMITED TO THE SINGLE-OUTPUT CASE

5. THE COST CRITERION OF MINIMIZING THE NUMBER OF GATES IS NOT ADEQUATE FOR MANY MSI/LSI/VLSI DESIGNS

PROGRAMMABLE mODULES: PLAs and PALs

- STANDARD (FIXED) STRUCTURE
- CUSTOMIZED (PROGRAMMED) FOR A PARTICULAR FUNCTION
  - DURING THE LAST STAGE OF FABRICATION
  - WHEN INCORPORATED INTO A SYSTEM
- FLEXIBLE USE
- MORE EXPENSIVE AND SLOWER THAN FIXED-FUNCTION MODULES
- OTHER TYPES DISCUSSED IN Chapter 12

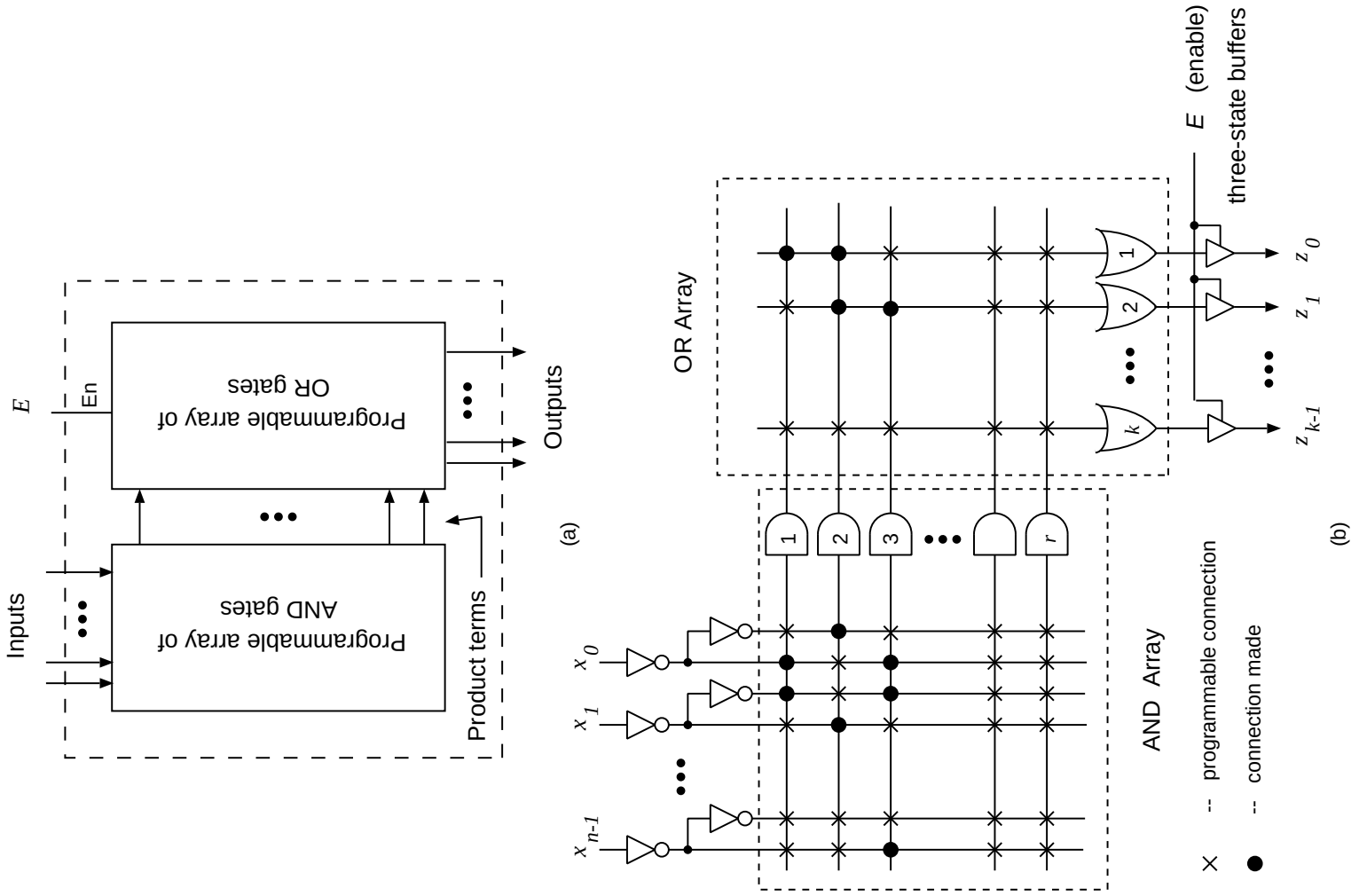

Figure 5.17: PROGRAMMABLE LOGIC ARRAY (PLA): a) BLOCK DIAGRAM; b) LOGIC DIAGRAM.

MOS PLA (OR-AND VERSION)

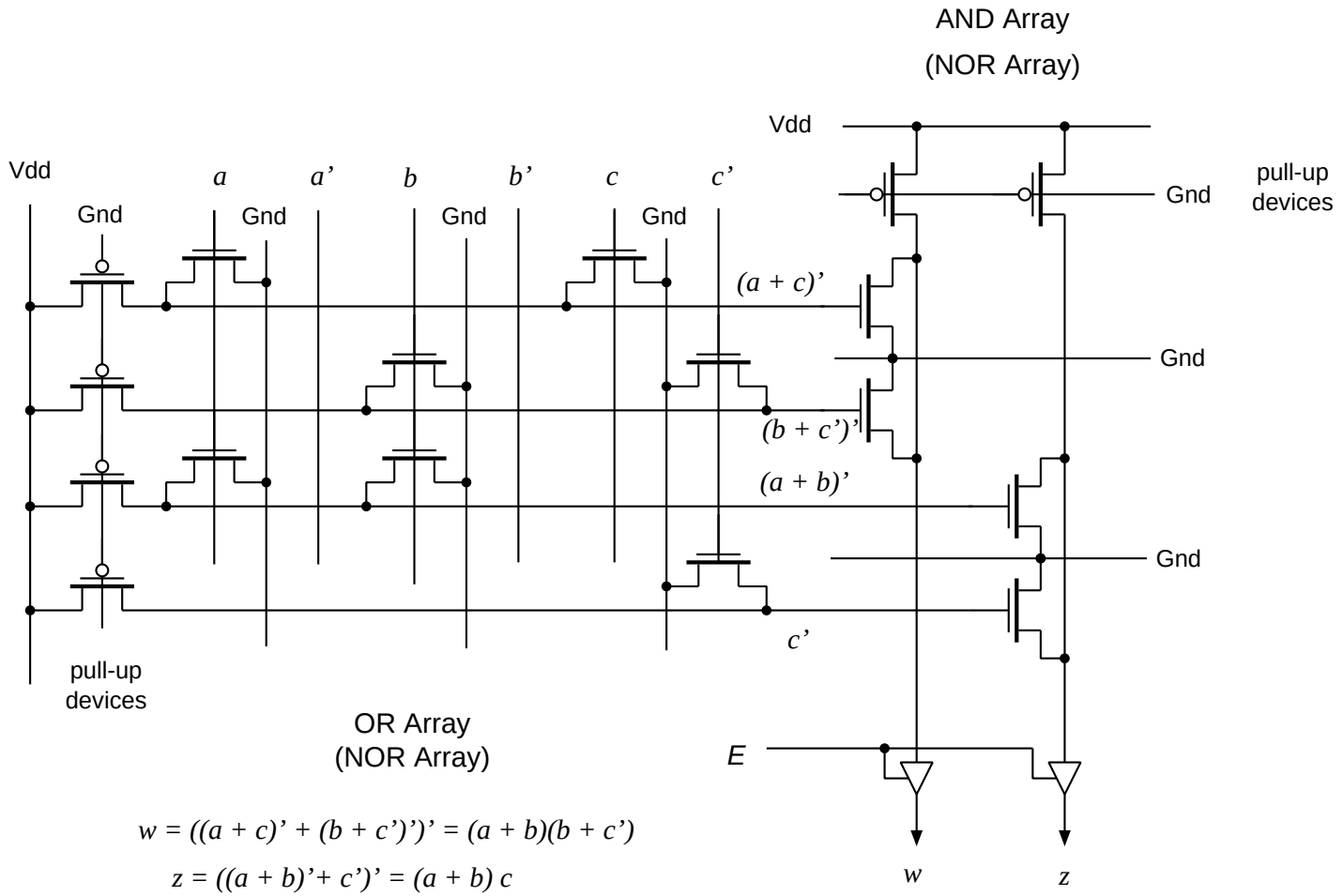

Figure 5.18: EXAMPLE OF PLA IMPLEMENTATION AT THE CIRCUIT LEVEL: FRAGMENT OF A MOS PLA.

IMPLEMENTATION OF SWITCHING FUNCTIONS USING PLAs

A BCD-to-Gray CONVERTER

Inputs: $\underline{d} = (d_3, d_2, d_1, d_0), \quad d_j \in \{0, 1\}$

Outputs: $\underline{g} = (g_3, g_2, g_1, g_0), \quad g_j \in \{0, 1\}$

Function:

i	$d_3d_2d_1d_0$	$g_3g_2g_1g_0$
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101

EXPRESSIONS:

$$g_3 = d_3$$
$$g_2 = d_3 + d_2$$
$$g_1 = d_2'd_1 + d_2d_1'$$
$$g_0 = d_1d_0' + d_1'd_0$$

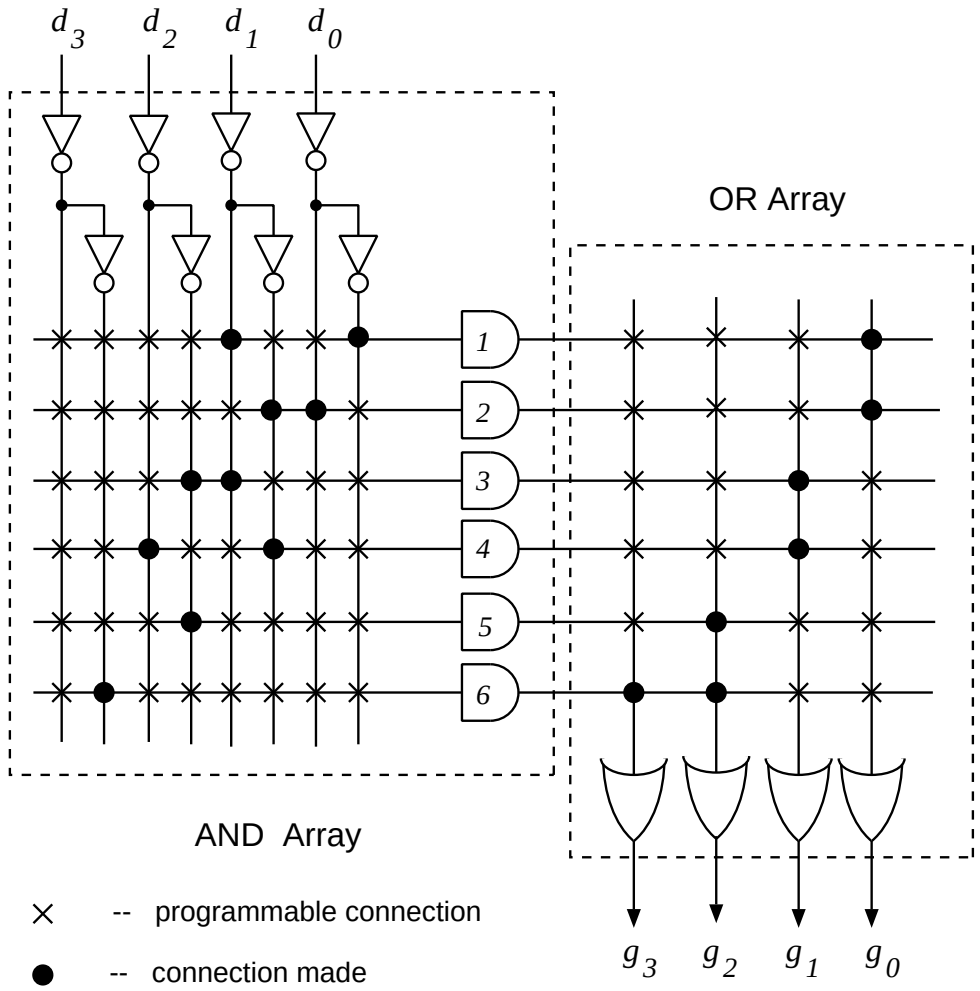

Figure 5.19: PLA IMPLEMENTATION OF BCD-Gray CODE CONVERTER.

PAL : A PROGRAMMABLE MODULE WITH FIXED OR ARRAY

- FASTER, MORE INPUTS AND PRODUCT TERMS COMPARED TO PLAs

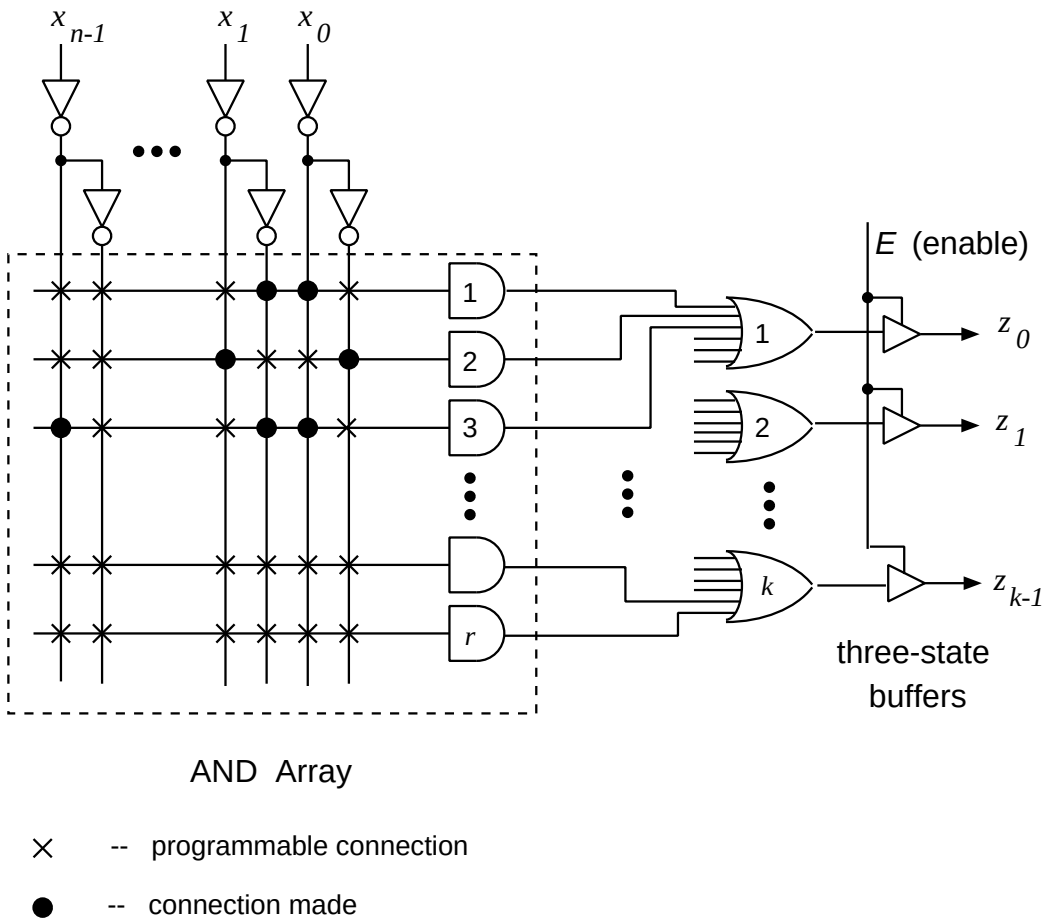

Figure 5.20: LOGIC DIAGRAM OF A PAL

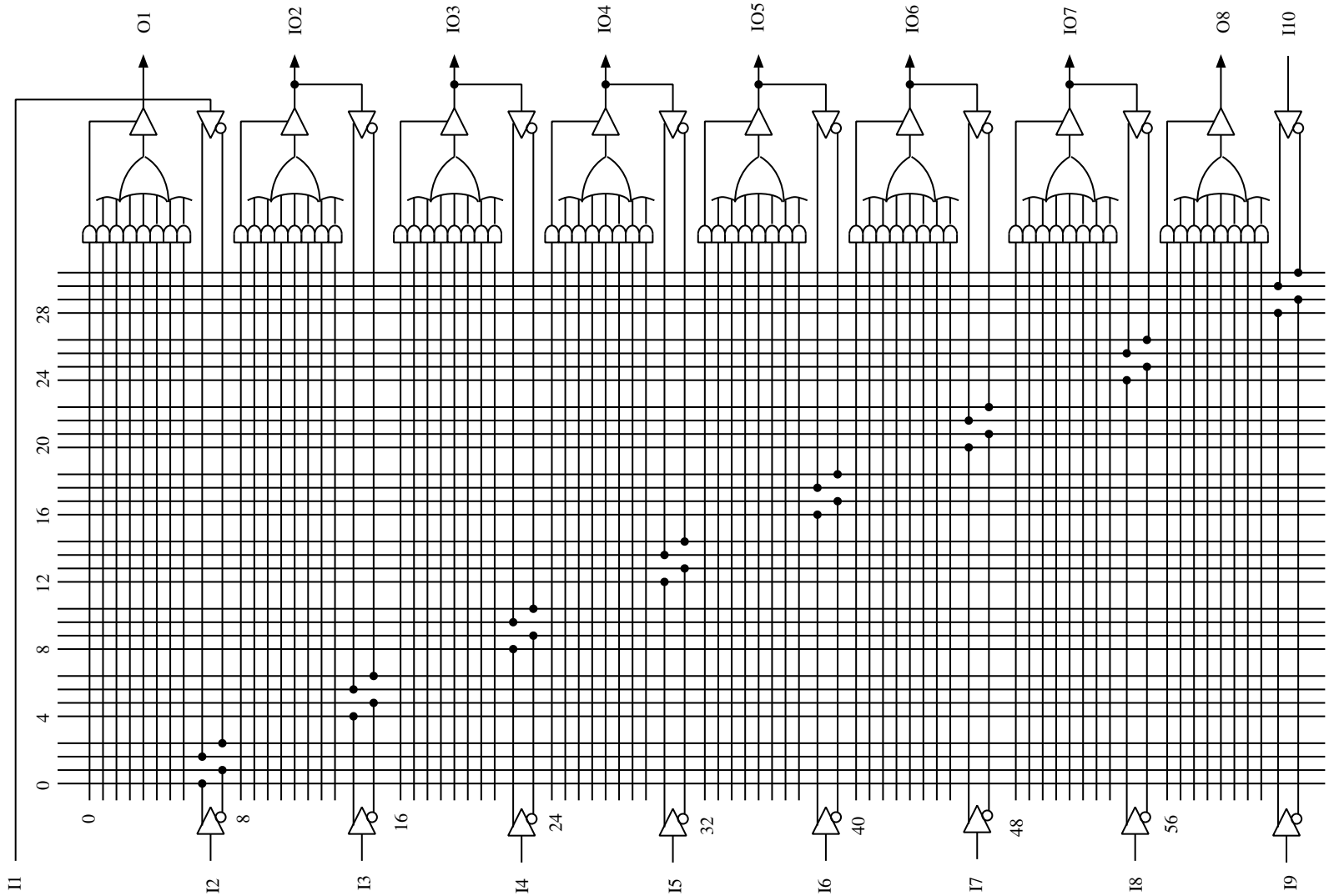

Figure 5.21: 16-INPUT, 8-OUTPUT PAL(P16H8)